



Light Segment A - Connect DIP leg 7 to the resistor connected to Vdd while leg 3 is connected to Vss.

Light Segment B - Connect DIP leg 6 to the resistor connected to Vdd while leg 3 is connected to Vss.

Light Segment C - Connect DIP leg 4 to the resistor connected to Vdd while leg 3 is connected to Vss.

Light Segment D - Connect DIP leg 2 to the resistor connected to Vdd while leg 3 is connected to Vss.

Light Segment E - Connect DIP leg 1 to the resistor connected to Vdd while leg 3 is connected to Vss.

Light Segment F - Connect DIP leg 9 to the resistor connected to Vdd while leg 3 is connected to Vss.

Light Segment G - Connect DIP leg 10 to the resistor connected to Vdd while leg 3 is connected to Vss.

Light Segment DP - Connect DIP leg 5 to the resistor connected to Vdd while leg 3 is connected to Vss.