



# *Photodiode Amplifiers*

**Changing Light to Electricity**

# Paul Rako

---


Strategic Applications Engineer  
Amplifier Group




# *The Photodiode:*

---

**Simple?**

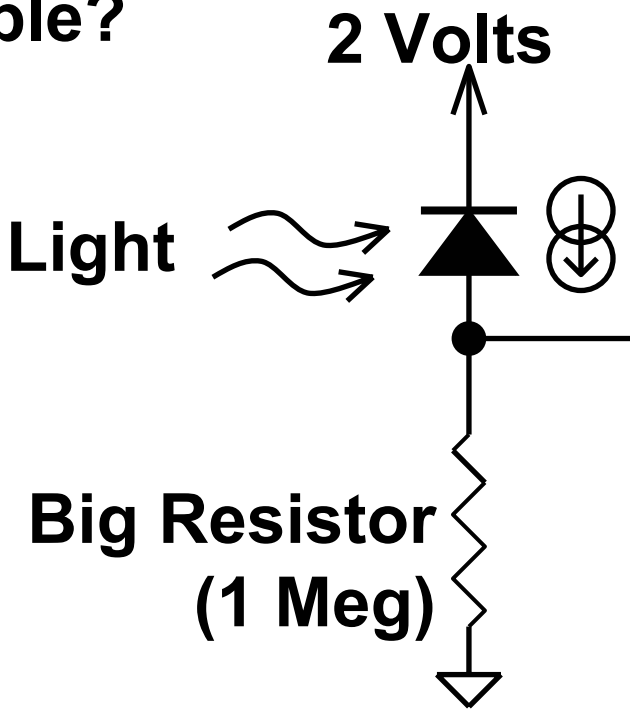

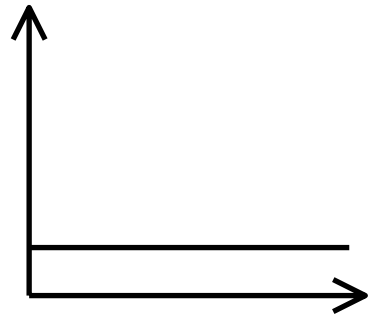**Tiny current flows here (10 nanoAmperes)**




**Makes about a 10 millivolts here**




# *The Photodiode:*

**No, not really 2 Volts  
simple:**

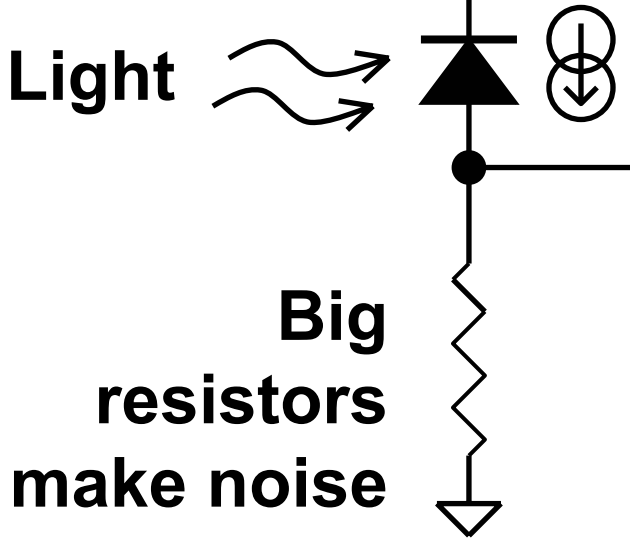

**Big  
resistors  
make noise**

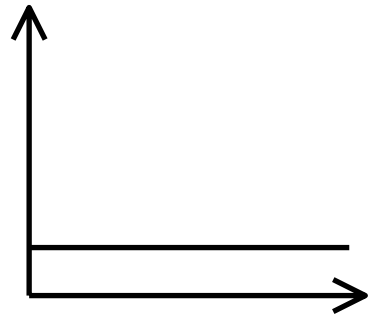**Dark Current  
(diode leakage)  
flows too and is  
worse with temp.**



**10 millivolts is  
not very useful.**



# *The Photodiode:*


---

**Worse yet:**



**2 Volts**

**High impedance point difficult to interface with.**

**Light**

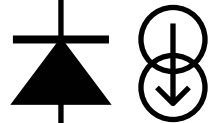

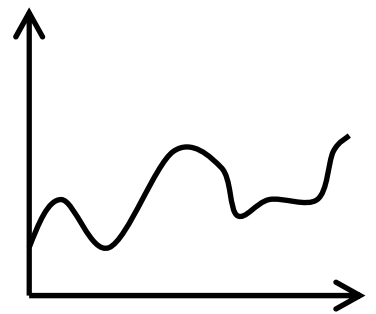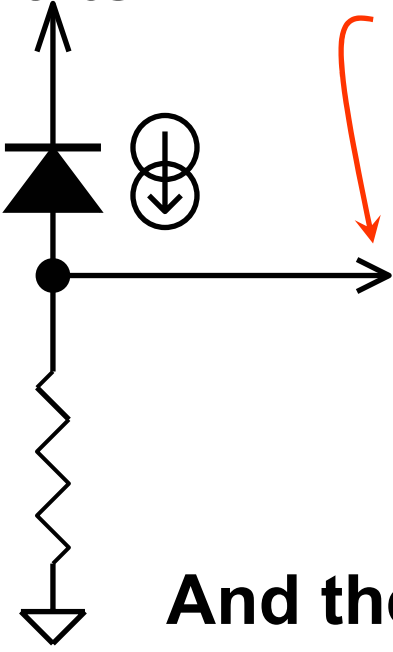**Diodes are capacitors too, so fast signals are difficult.**



**And the capacitance changes with voltage across the diode.**




# *The Photodiode:*

---

**Still Worse:**

**2 Volts**

**Light**

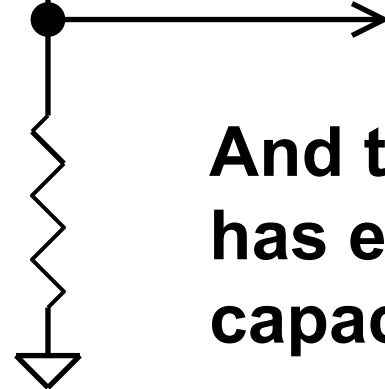

**To make the diode more sensitive to light you make the P-N junction big.**

**And that big junction has even more capacitance.**




## *Inside the Photodiode:*

---

**A cap and a current source:**

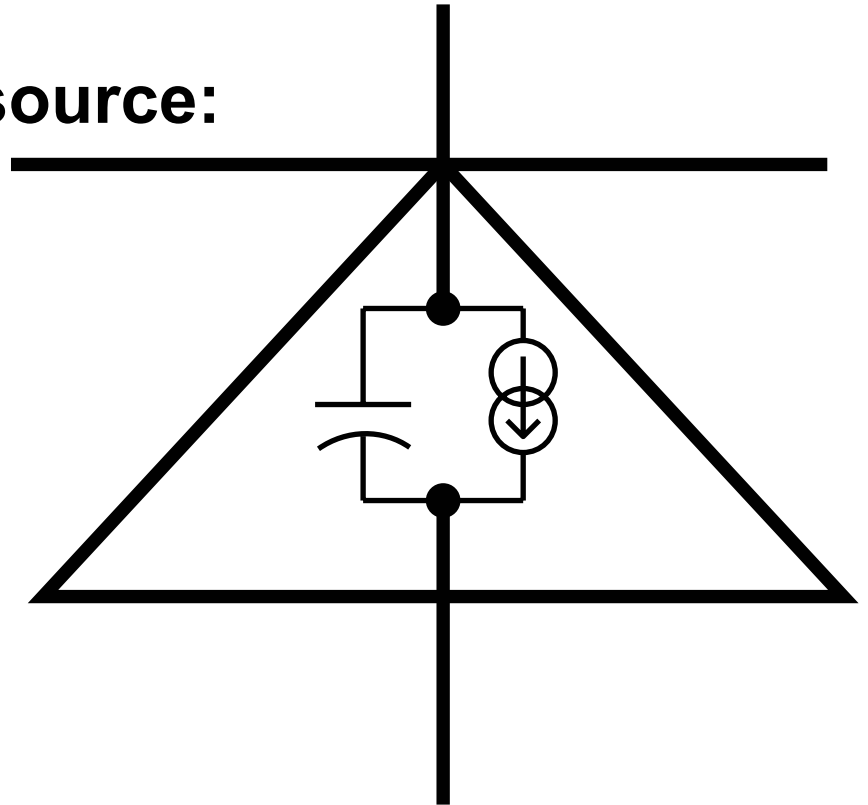**The bigger the voltage across the diode the further the junction boundaries are pushed apart and the lower the capacitance.**






## *Inside the Photodiode:*

---

**(And a really big resistor)**

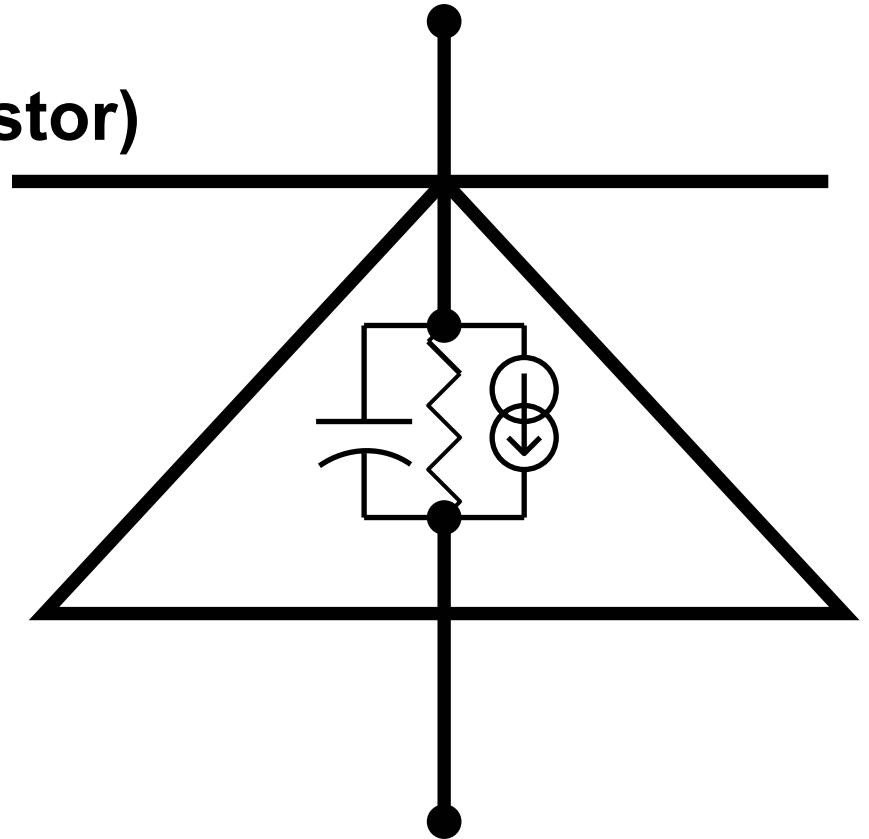**There is also a bulk resistivity to the diode but it is usually very high (100 M $\Omega$ ). This represents the “Dark Current”.**








# Photodiode Amplifier Types:

**Two ways to use the diode:**

**1) The Photovoltaic Mode:**

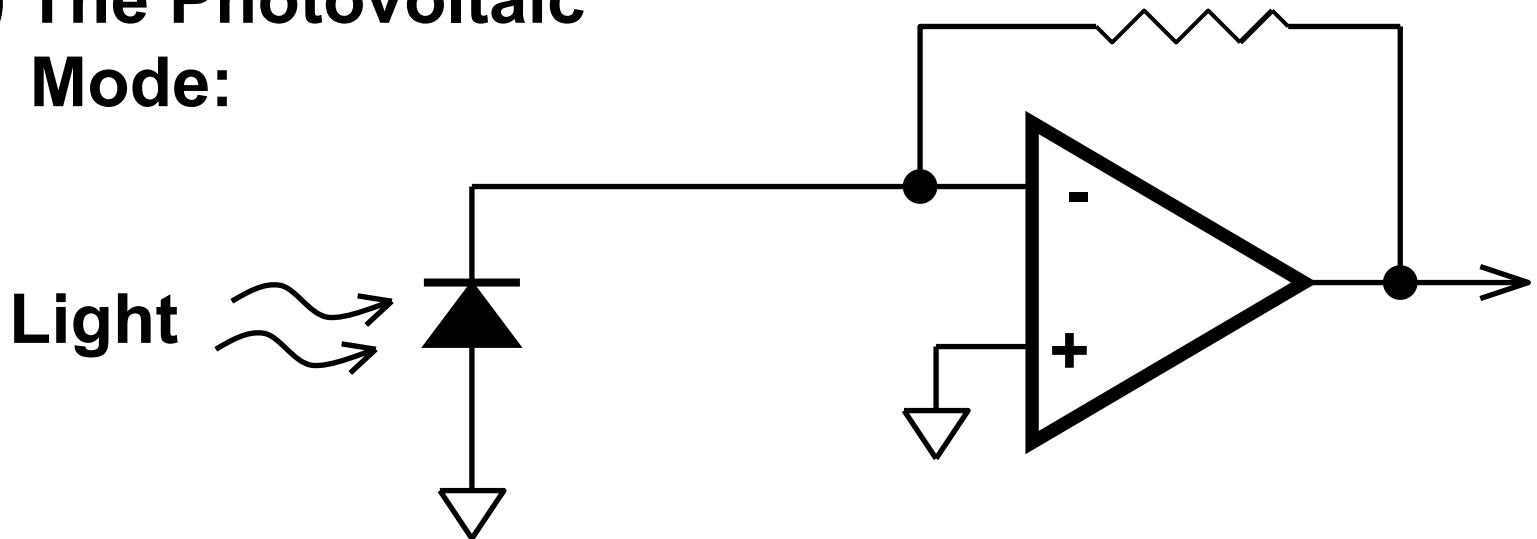

**Note ground— no voltage across diode.**



## *Photodiode Amplifier Types:*

---

### **The Photovoltaic Mode:**

**No voltage across diode means no current though the big resistor ~**

- **No dark current.**

**Also:**

- **Linear output**
- **Low Noise**



## *Photodiode Amplifier Types:*

---

### **Use Photovoltaic Mode:**


- **Where precision is more important than speed.**

**The lack of dark current removes an entire error term. The lower noise makes smaller measurements possible. The linear output makes calculations trivial.**



## Photodiode Amplifier Types:

### The Photoconductive Mode:

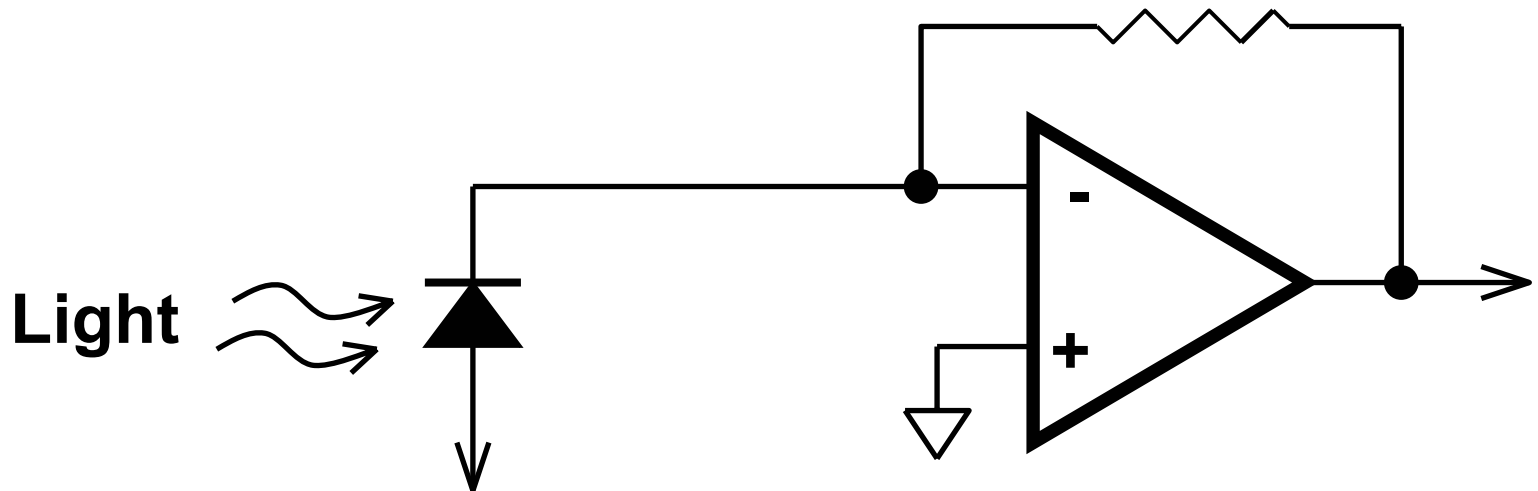

**- 10V, there is voltage  
across the diode.**



## *Photodiode Amplifier Types:*

---

### **Use Photoconductive Mode:**

- **Where speed is more important than precision.**

**The voltage across the diode lowers its capacitance. This allows faster amplifiers:**

- **Less capacitance allows a faster amplifier while maintaining stability.**




## *Biasing the Photodiode:*

---

- **Apply a big voltage (that doesn't change):**

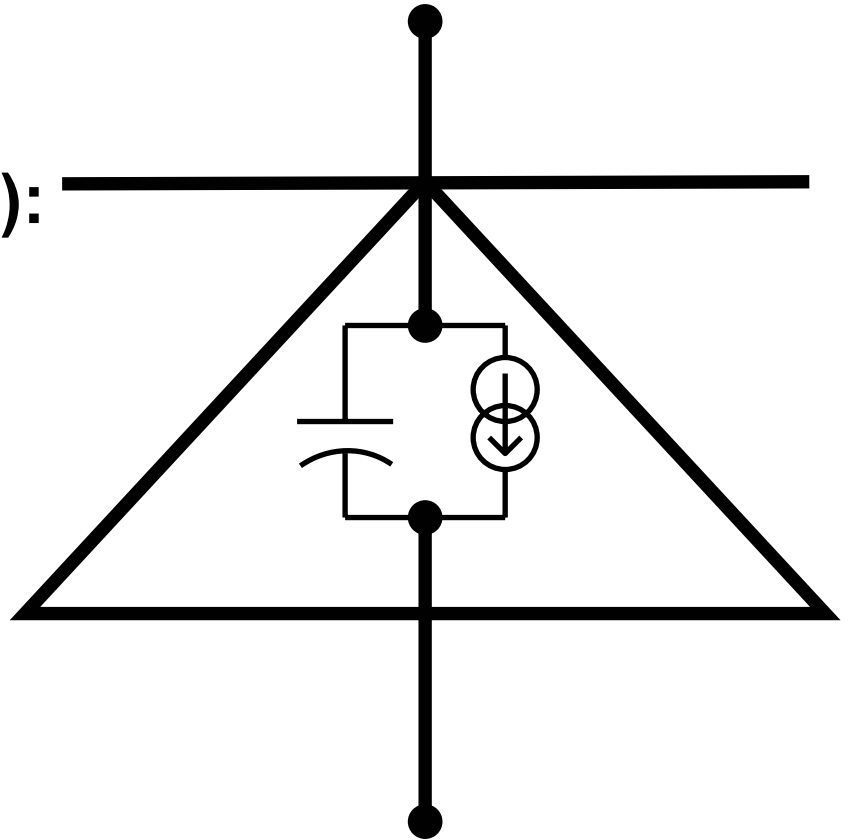
**We want a low capacitance so put a big voltage across the diode. We want fast response so don't let the voltage ever change. How?**





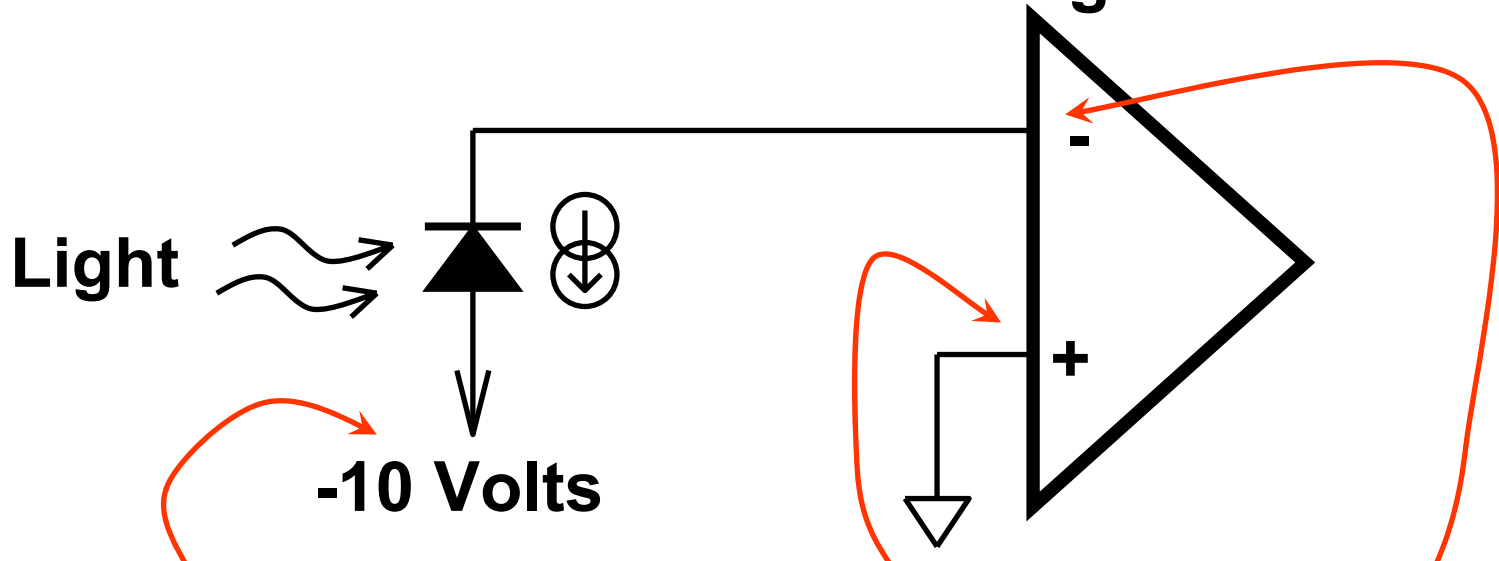
# *The Photodiode Amplifier:*

- **Connect the diode to a virtual ground:**



**Light**

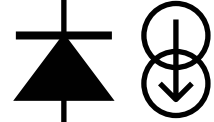

**-10 Volts**

**As much reverse voltage as the diode can stand.**


**If this pin is at ground so must this pin be at ground.**



# *The Photodiode Amplifier:*

- Oh yeah, add some feedback:

Light

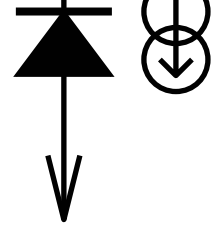

-10 Volts

This current makes positive voltage here


This pin stays at ground so output goes more positive with more light.




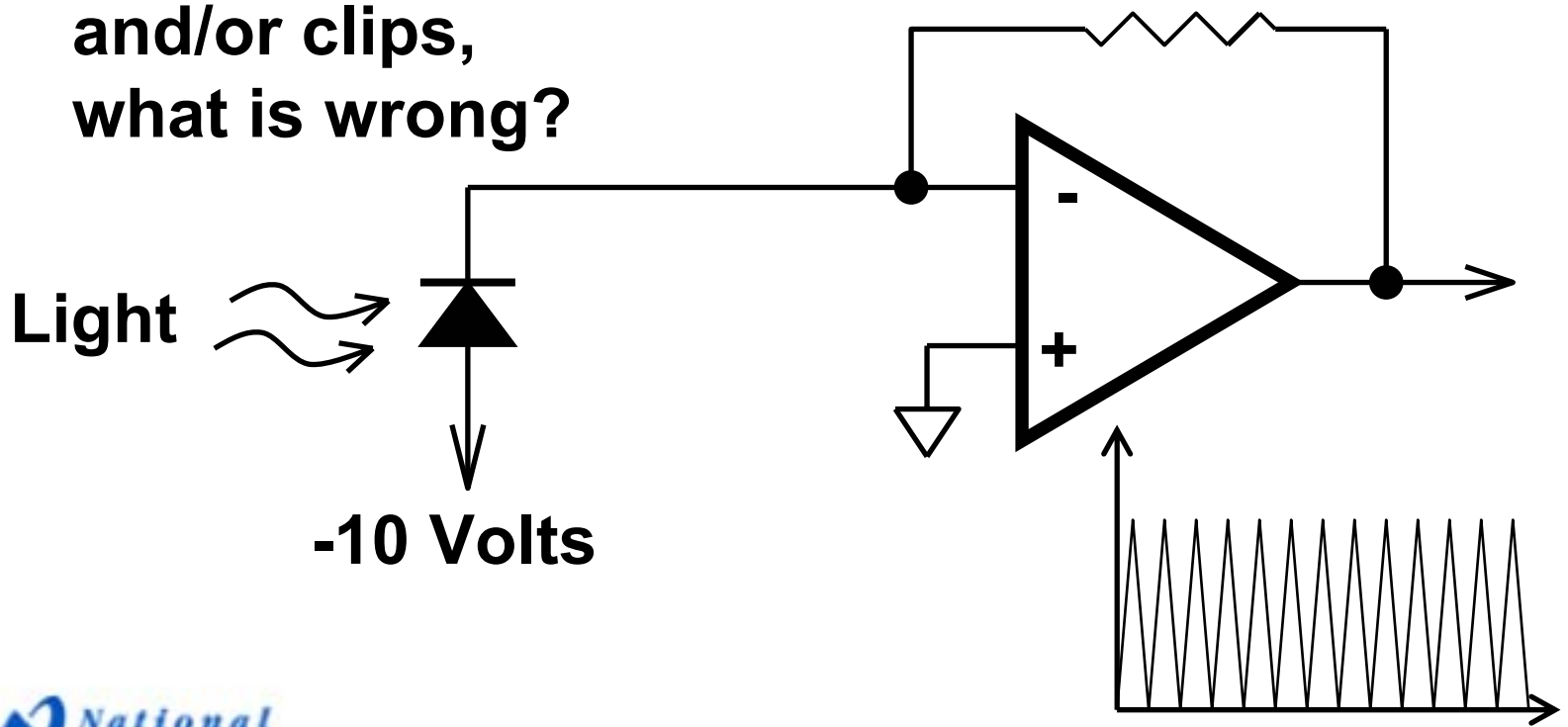
# *The Photodiode Amplifier:*

- **So it oscillates and/or clips, what is wrong?**






# Amplifier Stability:

- **Oscillations caused by capacitive diode on input.**

**Photodiode looks like cap to amp**

**-10 Volts**

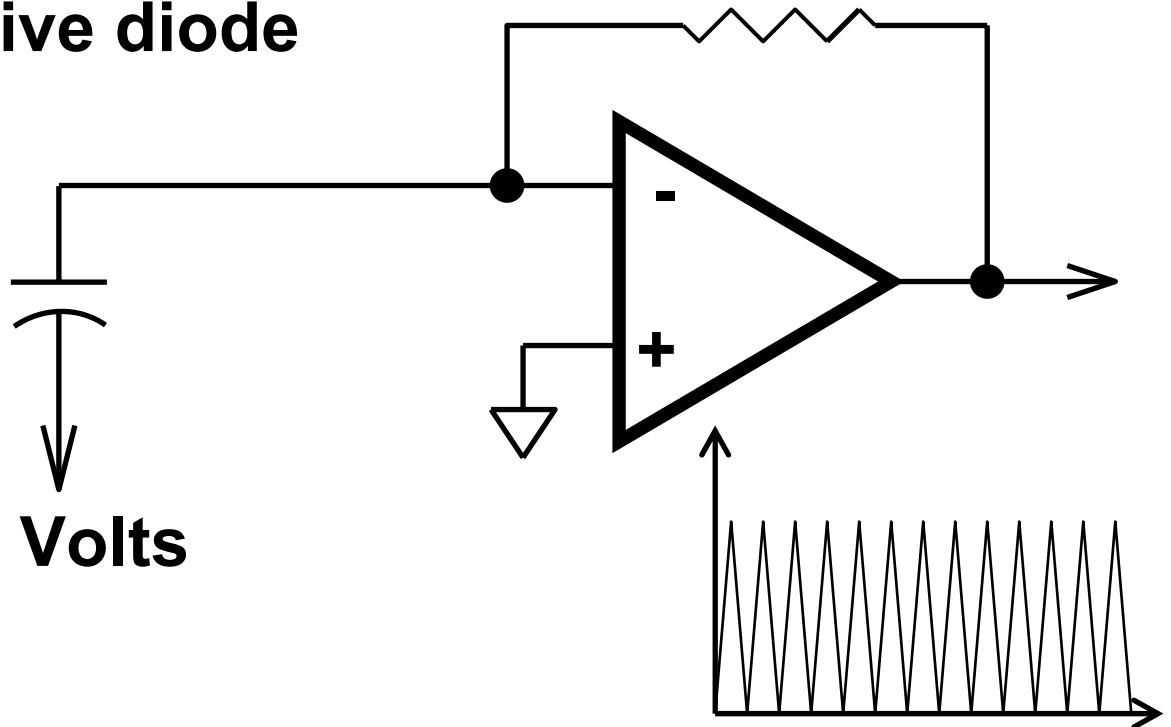




# Amplifier Stability:

- **Input pole (freq domain) or feedback lag (time domain) is bad.**

**Photodiode current source causes output to change.**

**-10 Volts**

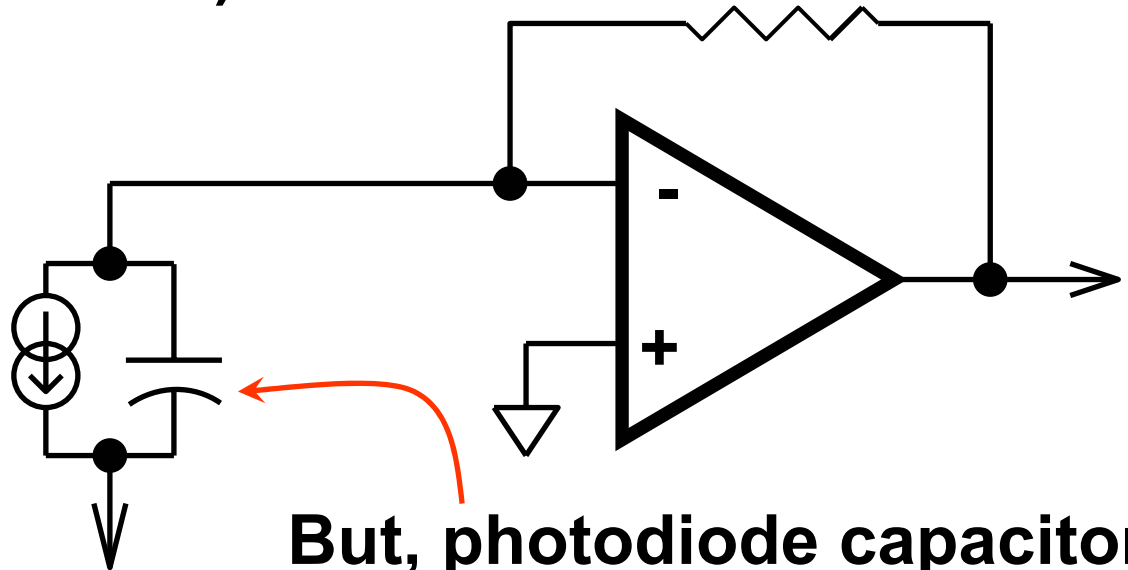

**But, photodiode capacitor means feedback signal will lag the actual output change.**



## *Mechanical Analogy:*


---

- **A gear and rack mechanical servo.**

**This gear is the  
amp output stage.**

**You are the amplifier  
front-end trying to keep  
the pointers the same.**

**This gear is the  
feedback.**

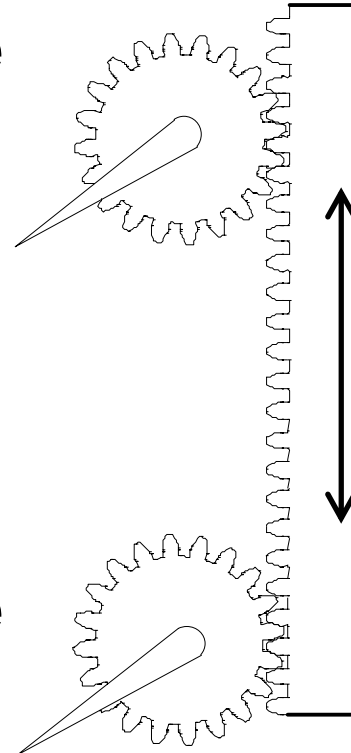

**This  
rack is  
the  
output  
voltage.**




## *Mechanical Analogy:*

---

- **Input cap is like backlash in feedback mechanism.**

**Backlash here is a lag in the feedback.**


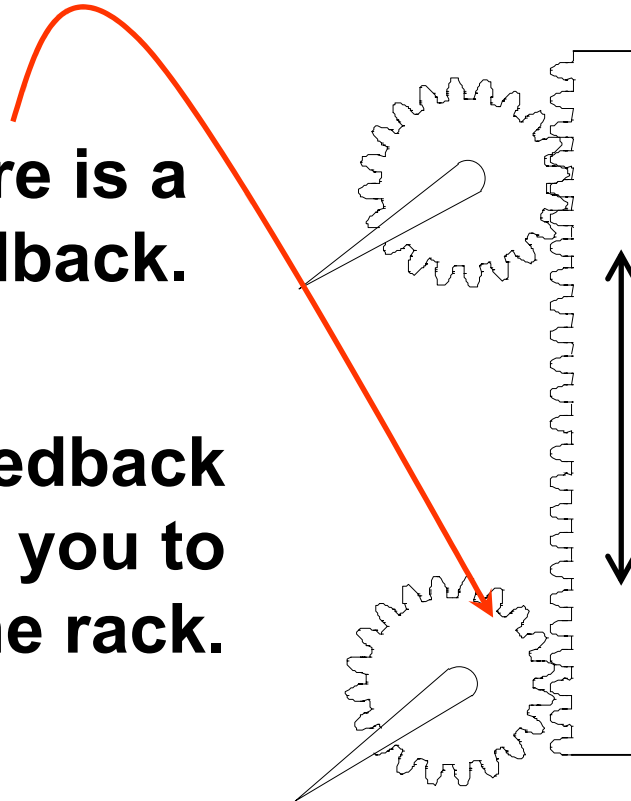
**The lag in your feedback pointer will cause you to oscillate the rack.**




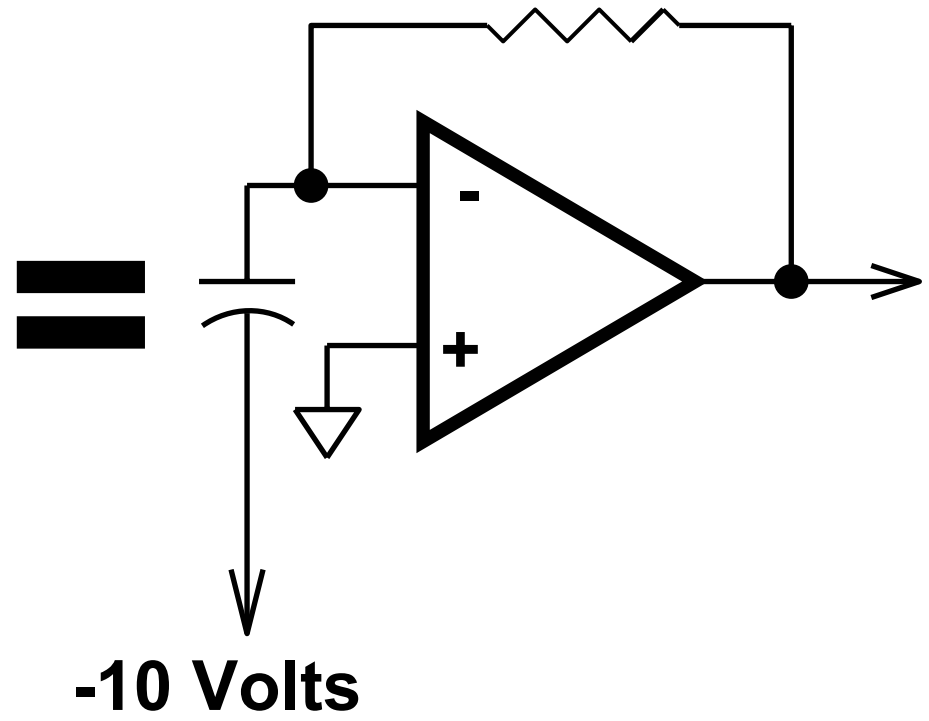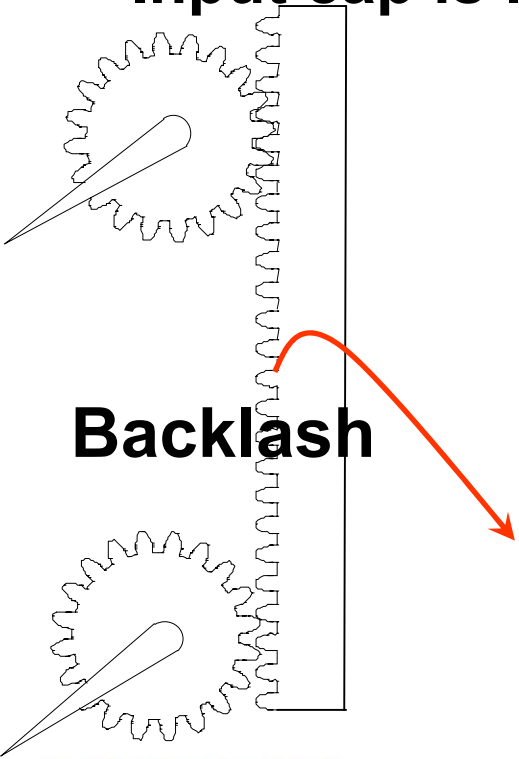
# Mechanical Analogy:


- **Input cap is like backlash in feedback mechanism.**




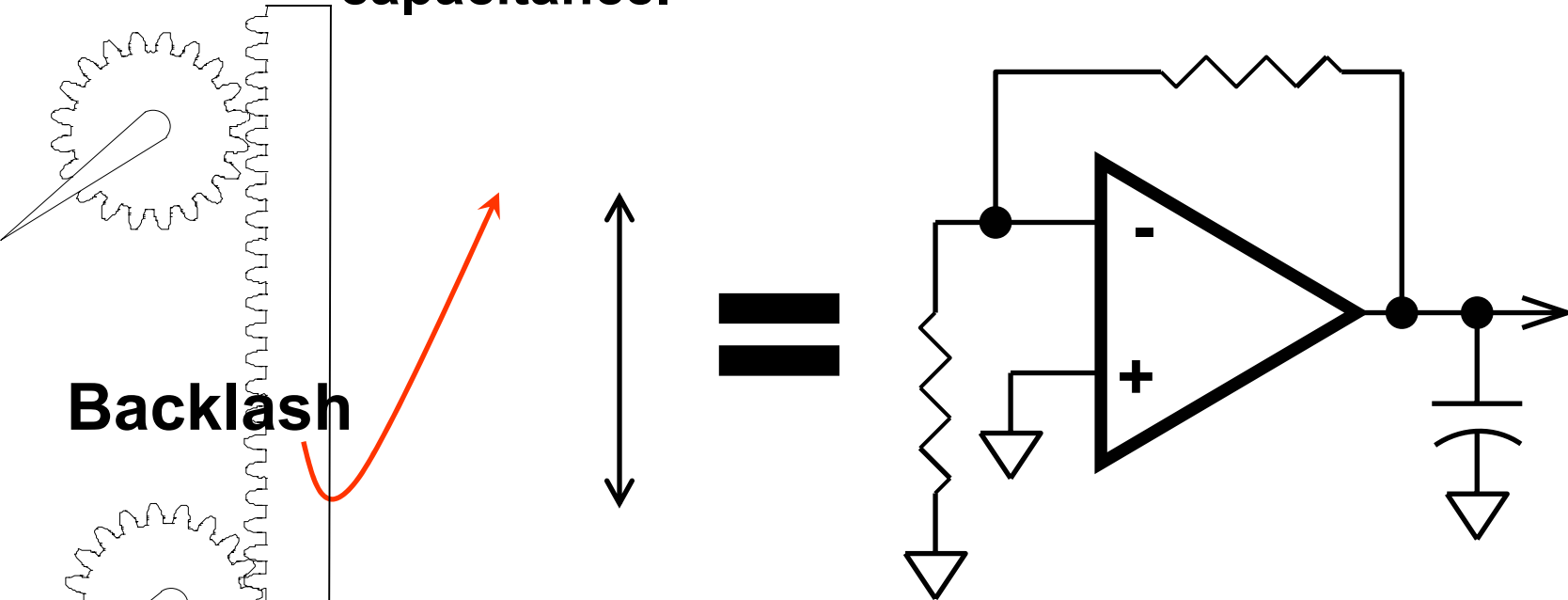
## Mechanical Analogy:

- **Interesting note: Driver backlash is like output capacitance.**




**Without compensation  
either cap will cause  
oscillations.**



## Compensated Amplifier:

- **Add a feedback cap to compensate.**

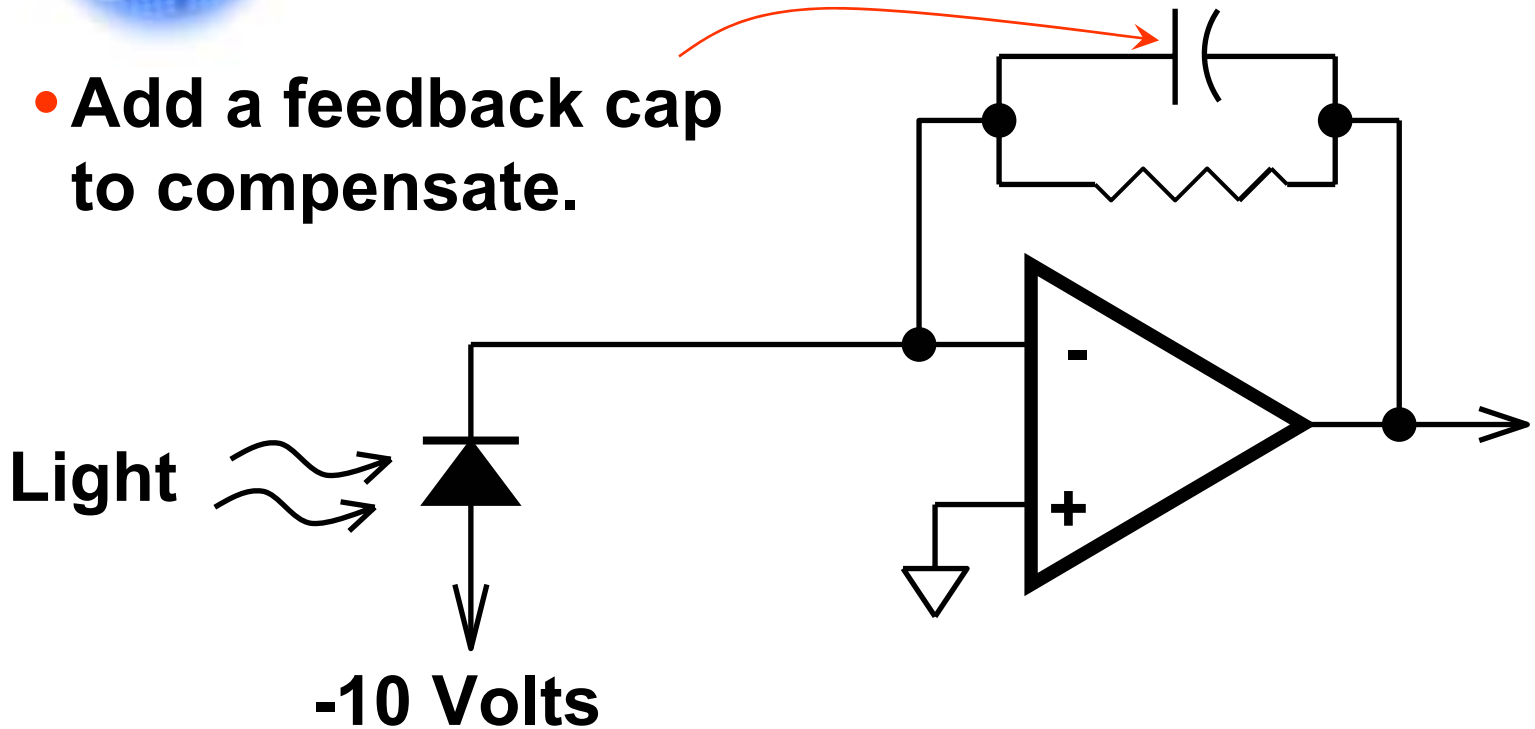





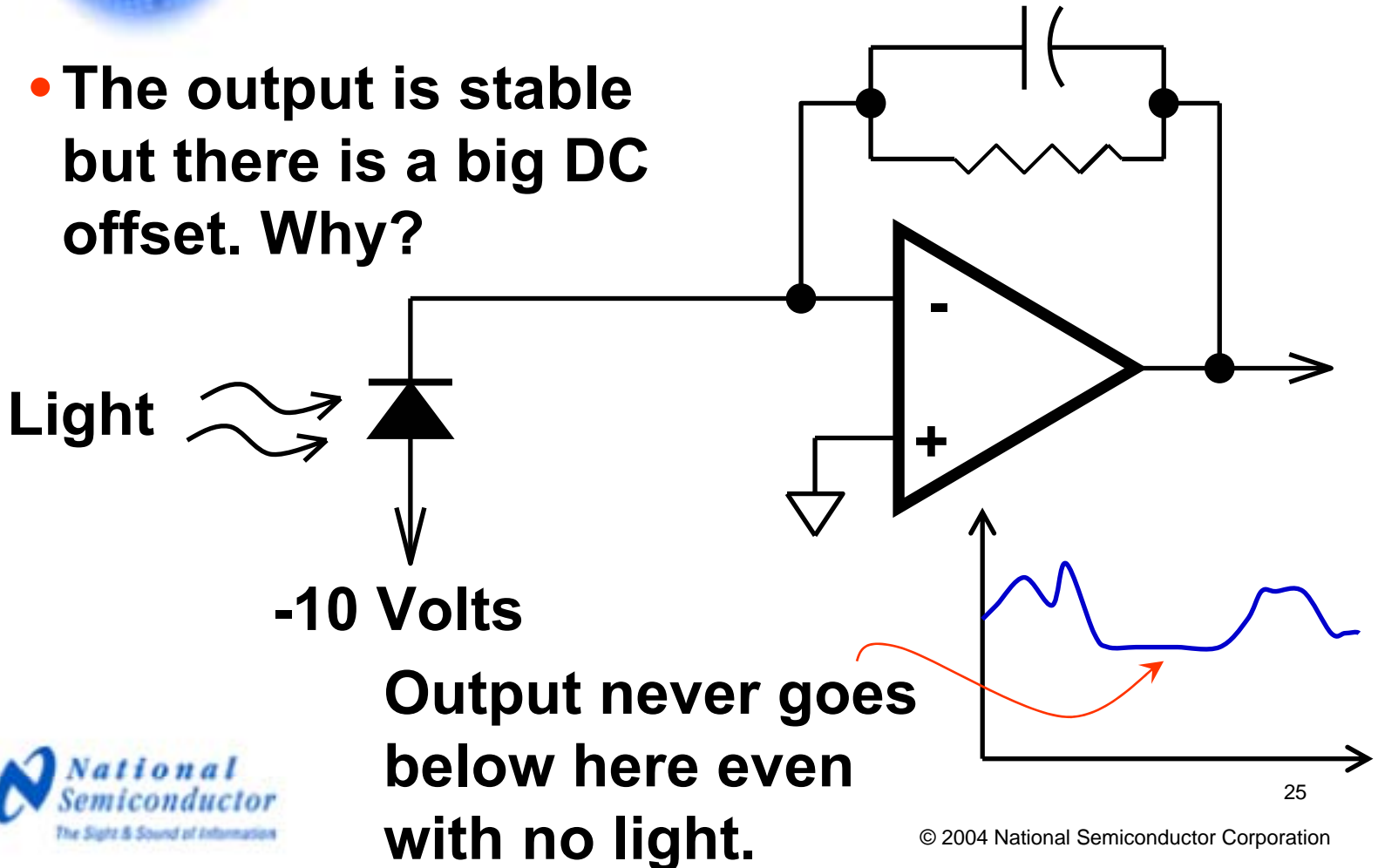
## Biassing the Amplifier:


- **The output is stable but there is a big DC offset. Why?**




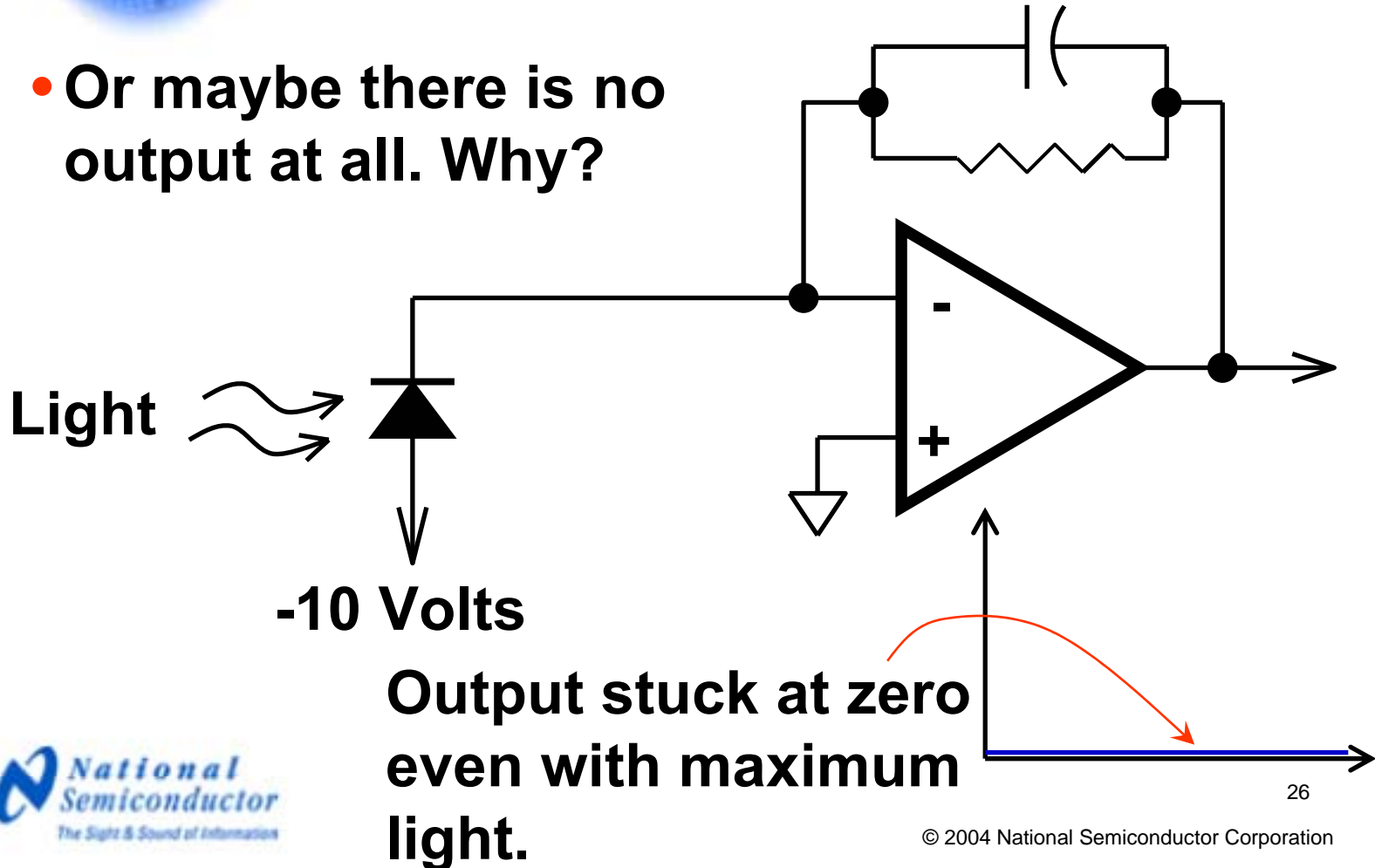
## Biassing the Amplifier:


- Or maybe there is no output at all. Why?





## Biassing the Amplifier:


- **Answer: Input bias current.**

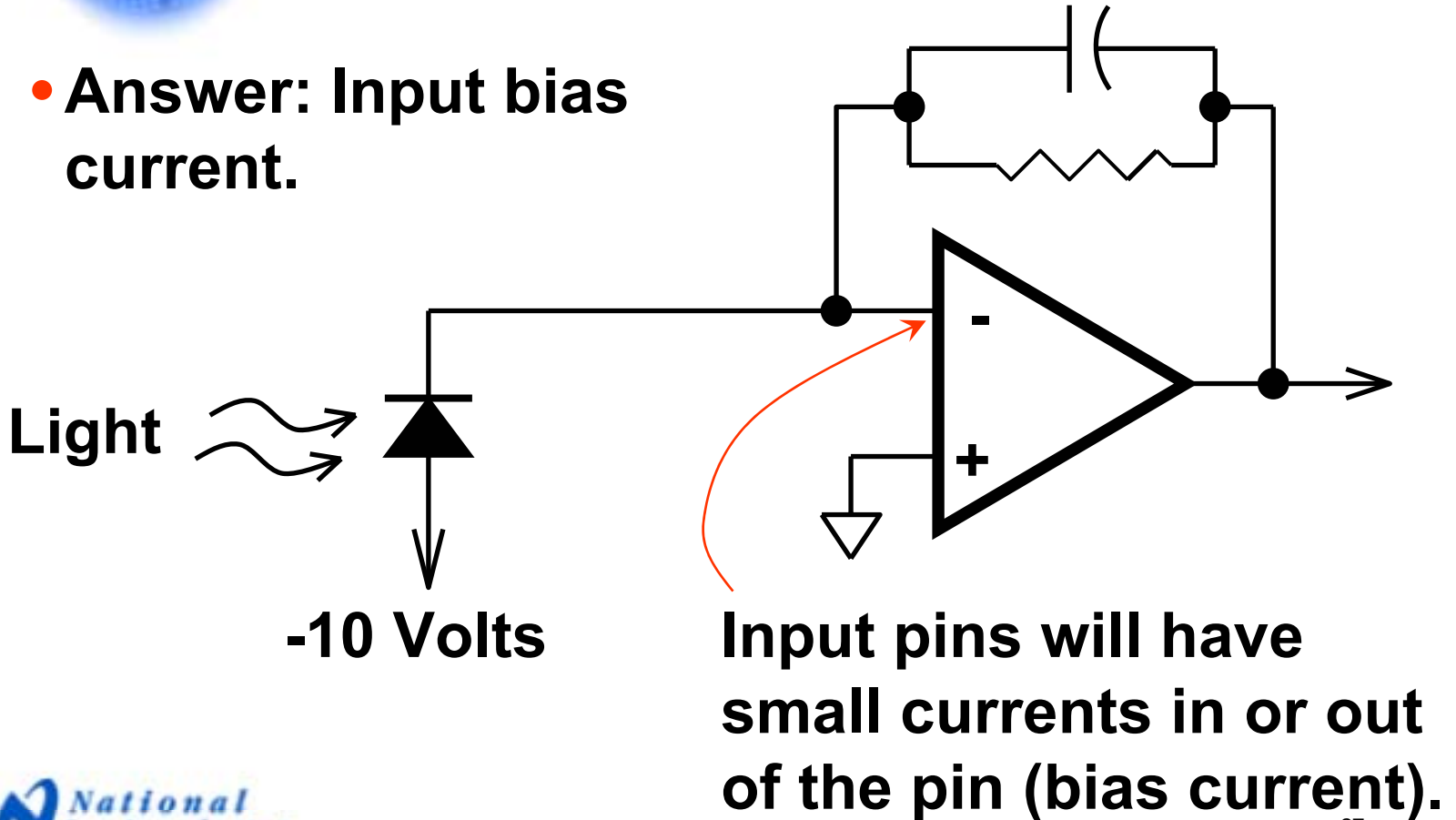


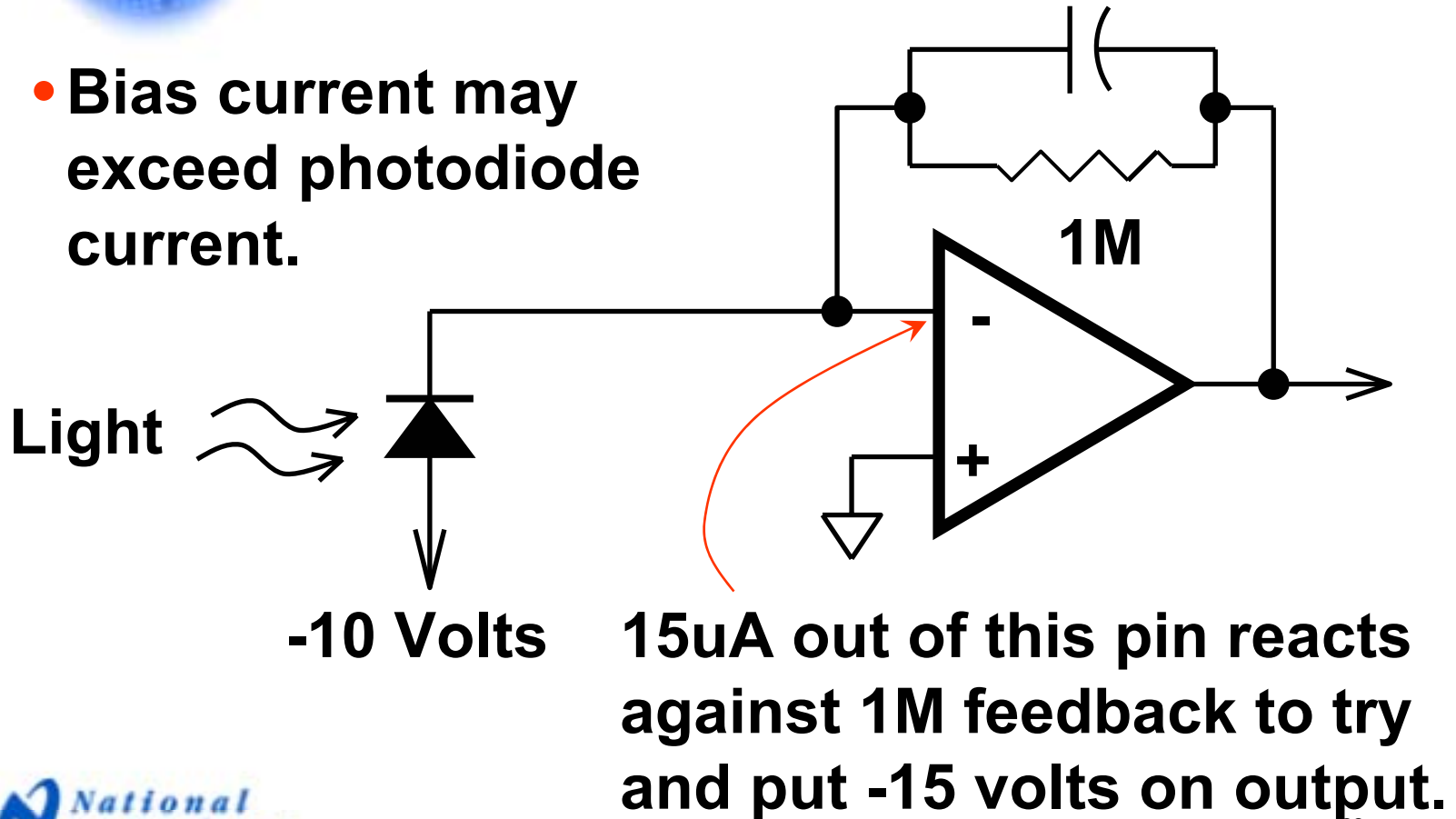
## Biassing the Amplifier:


- Bias current may exceed photodiode current.





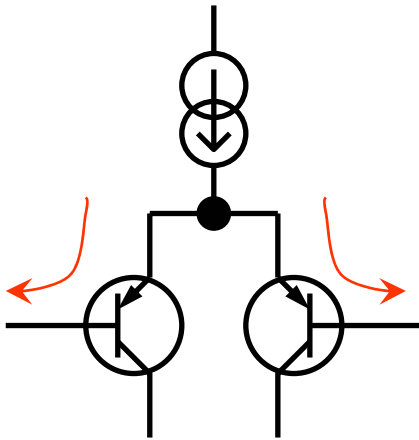
## Amplifier Input Stage:

- **Input transistors have base current.**



**PNP  
Input  
Stage**

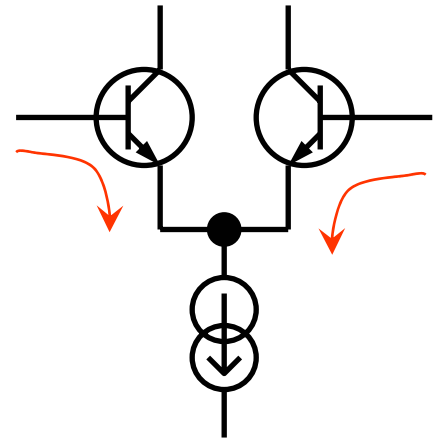**Input bias  
current may  
be 15  $\mu\text{A}$ , but  
won't vary  
much over  
temperature.**




**NPN  
Input  
Stage**



## Amplifier Input Stage:

- **Input JFETs have large drift.**

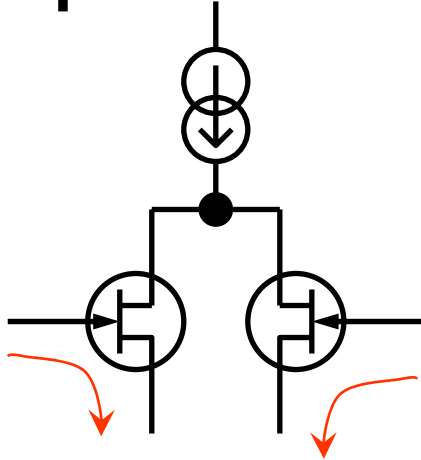

**JFET  
Input  
Stage**


**Input bias  
current may  
be 15 pA, but  
will double  
every 10°C.**



## Amplifier Input Stage:

- CMOS parts have ESD diodes.

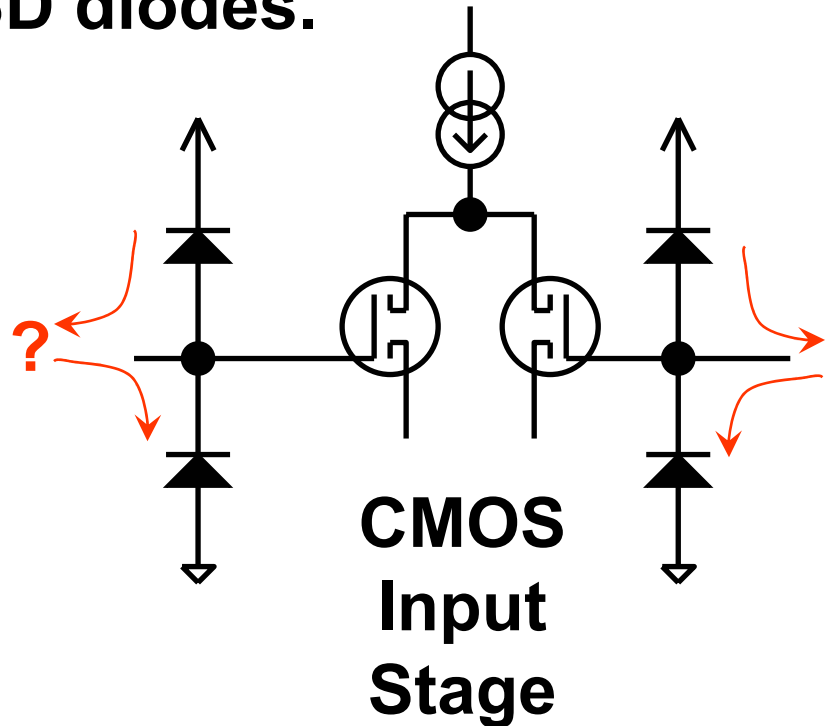
**MOSFET has no DC bias current but mis-match in ESD diodes causes bias current to flow in (or out) of pin.**





# Correcting DC Bias

- Use resistor.

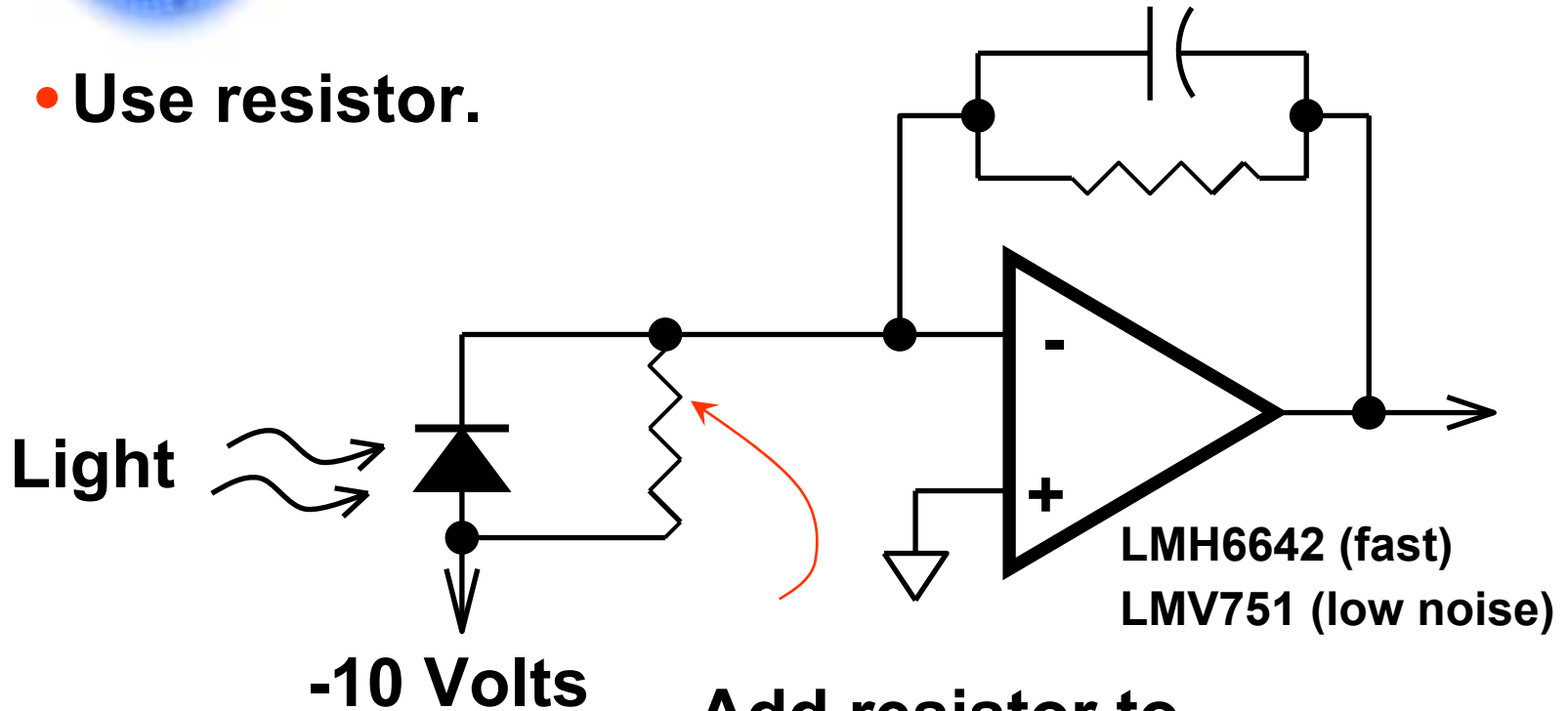






# Correcting DC Bias

- Servo out the error.

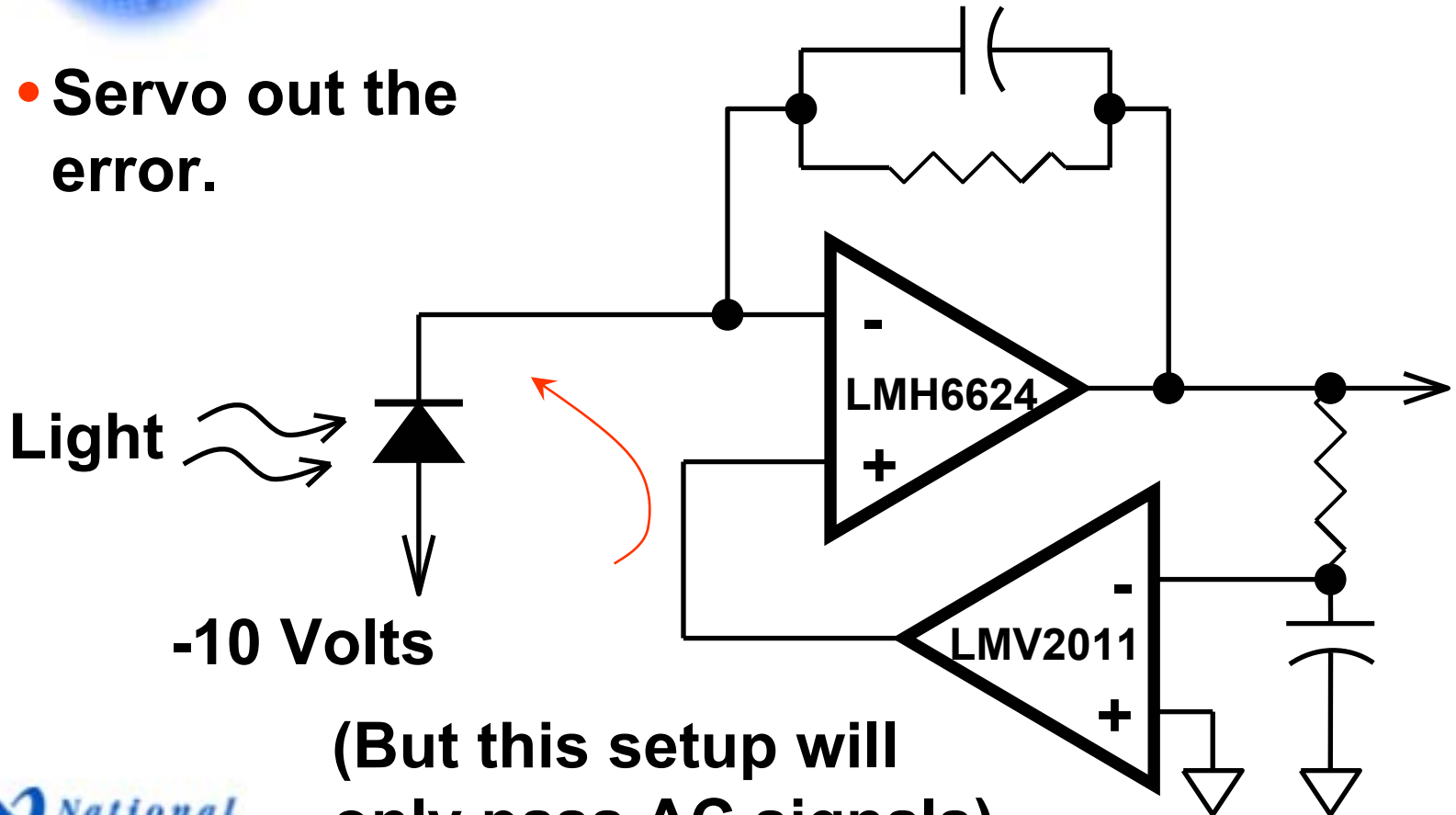


-10 Volts

(But this setup will only pass AC signals)


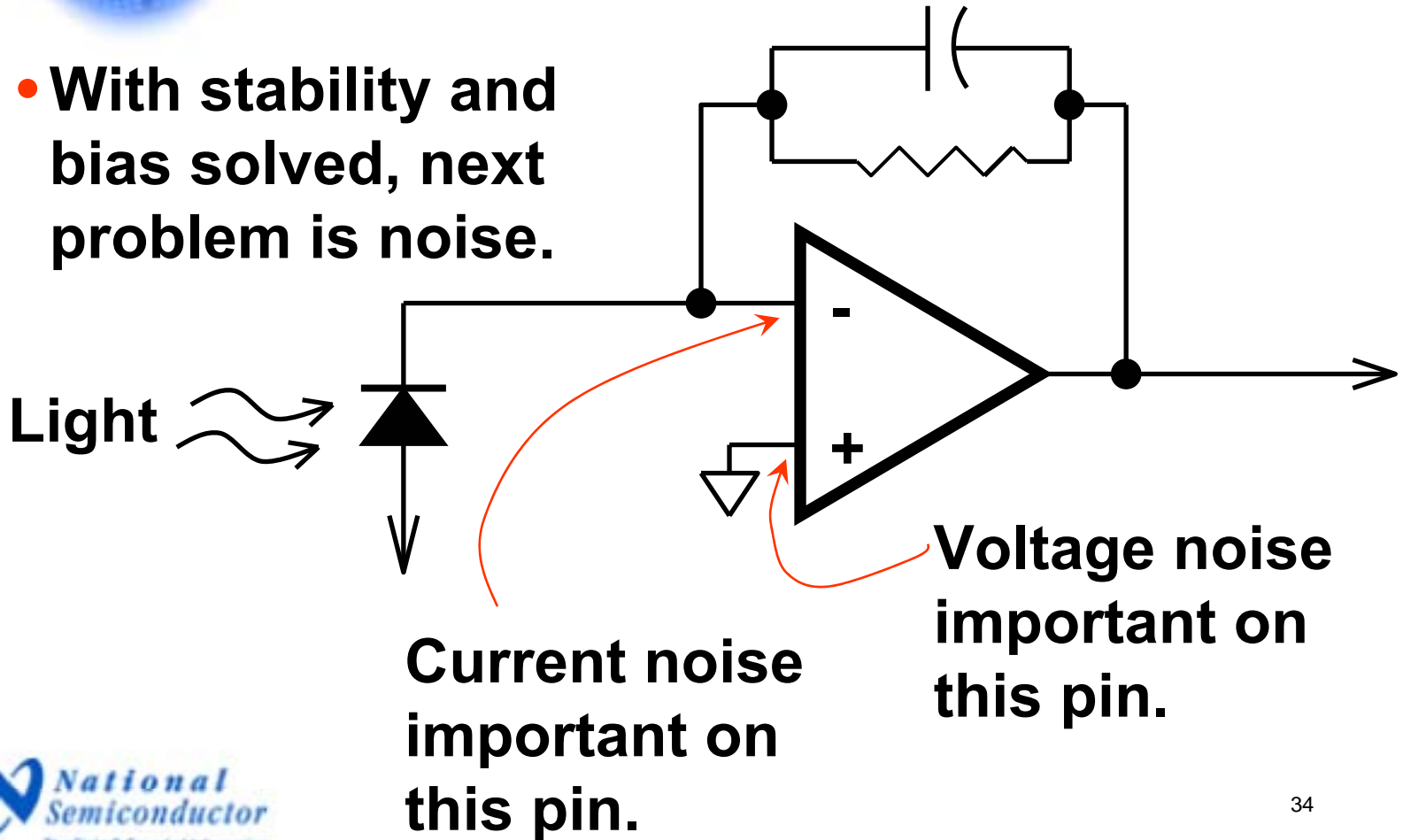
## Amplifier noise:

- **With stability and bias solved, next problem is noise.**





## *Amplifier noise:*

---


- **Low current and low voltage noise in the same part is hard.**
- **JFET amplifiers have low current noise.**
- **Bipolar amplifiers have low voltage noise.**
- **Choppers can cause problems.**


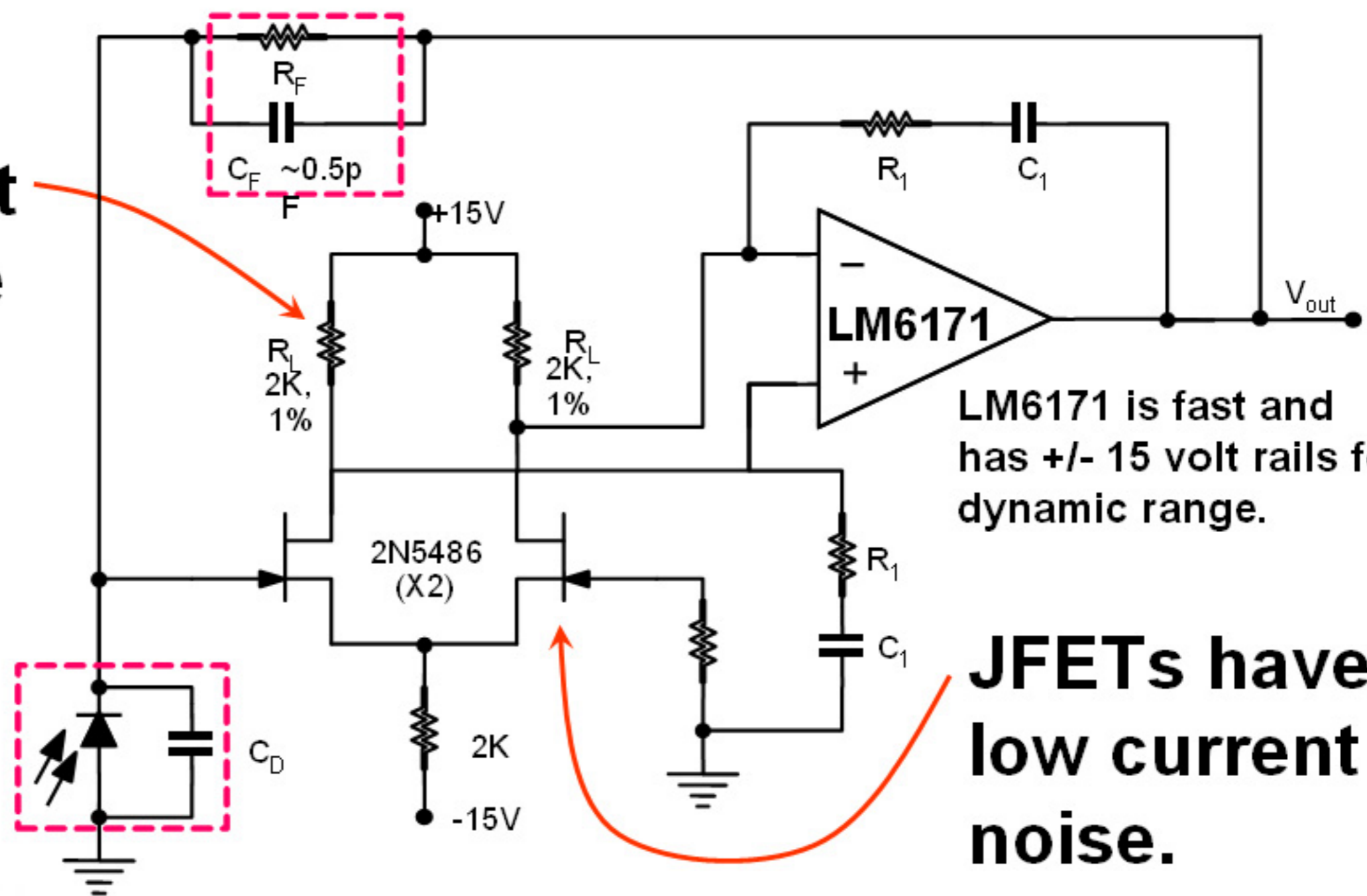
# A Composite Amplifier:

- One solution: a compound amp.

Run a lot of current to reduce the voltage noise.



LM6171 is fast and has +/- 15 volt rails for dynamic range.

JFETs have low current noise.



## *Some Potential Parts:*

---

Device	Input Noise Voltage (nV/RtHz)	Input Noise Current (pA/RtHz)	Input Capacitance (pF)	I <sub>bias</sub> (max)	GBWP (MHz)	GBWP/C <sub>in</sub> (MHz/pF)
LMH6628	2	2	1.5	20μA	200	133
LMH6626*	1.0	1.8	0.9	20μA	500	556
LMH6624*	0.92	2.3	0.9	20μA	500	556
LMH6622	1.6	1.5	0.9	10μA	200	222
LMH6654 /6655	4.5	1.7	1.8	12μA	150	83
LMH6672	4.5	1.7	2	14μA	100	50
LF411A	25	0.01	4	200pA	4	1
LMV751	7	0.005	5	100pA	5	1
LMC662	22	0.0002	4	0.01pA (typical)	1.4	0.3
LMV771	8	0.001	4	100pA	4	1



## *Conclusions:*

---

- **Photodiode amplifiers are tricky.**
- **The design should be tailored for the application, DC, Data, etc.**
- **The design requires a lot of trial and error.**
- **Be prepared to do a lot of study.**
- **National Applications Engineering is here to help you.**



## *Resources:*

---

- **AN-1244: Photo-Diode Current-to-Voltage Converters.**
- **Amplifier WEBENCH®– On-line simulation of amplifier performance**
- **Photodiode Amplifiers: OP AMP Solutions by Jerald Graeme**
- **Photodetection and Measurement: Maximizing Performance in Optical Systems by Mark Johnson**
- **Photodetectors: Devices, Circuits and Applications by Silvano Donati**



## *Thank You!*

---

- If you have questions for our presenter, please send them to our customer response center at [new.feedback@nsc.com](mailto:new.feedback@nsc.com).
- The online technical journal National Edge is available at <http://www.national.com/nationaledge/>.
- Sign up for National's monthly newsletter, [News@National](mailto:News@National) by updating your online profile at [http://www.national.com/profile/user\\_info.cgi](http://www.national.com/profile/user_info.cgi)