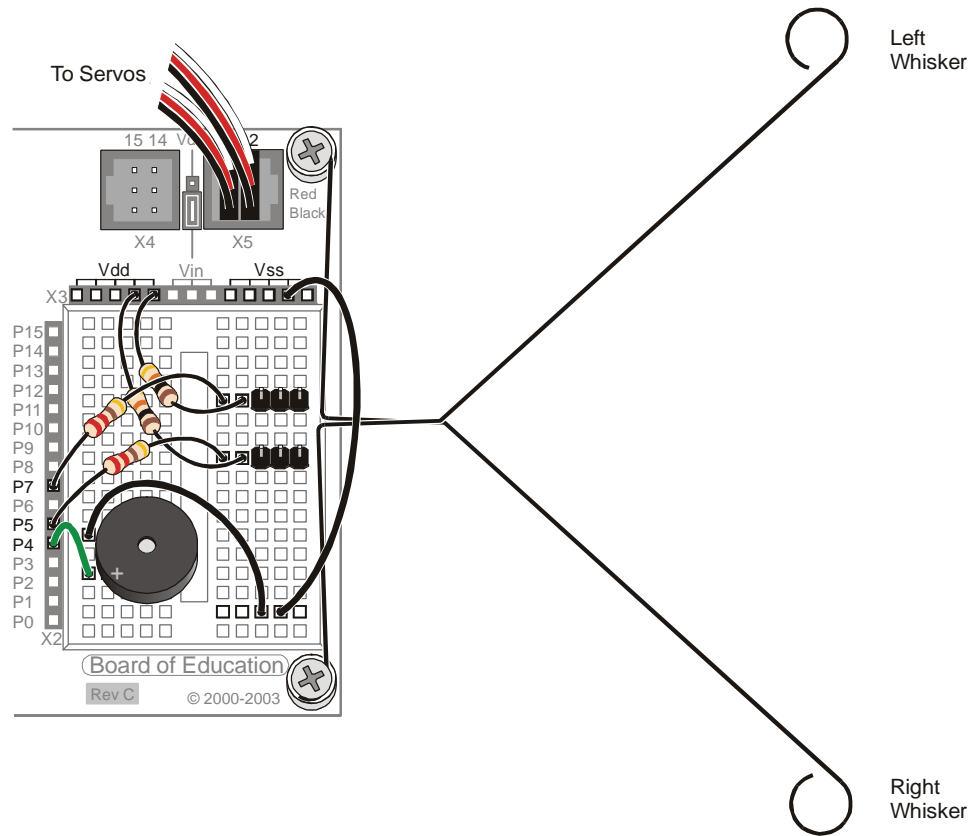


Figure 5-5: Whisker Wiring Diagram for the Board of Education



5

! Use the 220 Ω resistors (red-red-brown color codes) to connect P5 and P7 to their corresponding 3-pin headers. Use the 10 kΩ resistors (brown-black-orange color codes) to connect Vdd to each 3-pin header.