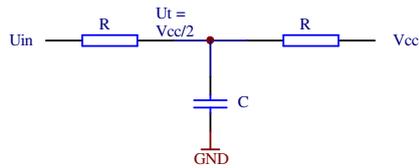


calculations to find real Umin and Umax



First, C needs to be charged until $U_t > V_{cc}/2$

$$U_t(t) = (U_{in}/2 + V_{cc}/2) * (1 - e^{-t/(C*R/2)})$$

$$t = m * T_i$$

$$K = T_i / (C * R/2)$$

$$U_t(m) = (U_{in}/2 + V_{cc}/2) * (1 - e^{-mK}) \quad m = 0, 1, 2, \dots$$

$$(U_{in}/2 + V_{cc}/2) * (1 - e^{-mK}) > V_{cc}/2$$


$$e^{mK} > 1 + V_{cc}/U_{in}$$

$$m > \ln(1 + V_{cc}/U_{in}) / K$$

$$M = \text{INT}(1 + \ln(1 + V_{cc}/U_{in}) / K)$$

$$U_{max} = (U_{in}/2 + V_{cc}/2) * (1 - e^{-MK})$$

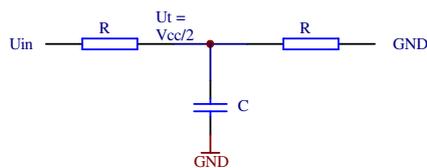at $t = M * T_i$ the discharge starts and this takes one T_i



$$U_{min} = U_{max} * e^{-K} + (U_{in}/2) * (1 - e^{-K})$$

EXAMPLES

$$T_i = 4.34 \mu, R=10k, C=0.1 \mu$$

$$K = T_i / (C * R/2) = 0.00868$$

$$U_{in} = V_{cc}/10, V_{cc}=5$$

$$M = \text{INT}(1 + \ln(11) / 0.00868) = \text{INT}(1 + 276.25) = 277$$

$$e^{-MK} = 0.090323$$

$$U_{max} = 0.500322 * V_{cc}$$

$$e^{-K} = 0.991358$$

$$U_{min} = 0.496430 * V_{cc}$$

$$U_{ripple} = U_{max} - U_{min} = 0.003892 * V_{cc} = 19.46 \text{mV}$$

Checking with formulae:

$$U_{ripple} = (V_{cc}/2) * (1 - e^{-K}) / (1 + e^{-K}) = 0.002170 * V_{cc} = 10.85 \text{mV}$$

$$U_{max} = U_{in}/2 + (V_{cc}/2) / (1 + e^{-K}) = 0.301085 * V_{cc}$$

$$U_{min} = U_{in}/2 + (V_{cc}/2) * (e^{-K}) / (1 + e^{-K}) = 0.298915 * V_{cc}$$

So the M correction is required to find the real Umin and Umax

The formulae apparently are only correct when $U_{in} = V_{cc}/2$

$$T_i = 4.34 \mu, R=10k, C=0.1 \mu$$

$$K = 0.00868$$

$$U_{in} = V_{cc}/2, V_{cc}=5$$

$$M = 127$$

$$e^{-MK} = 0.332086$$

$$U_{max} = 0.500936 * V_{cc}$$

$$e^{-K} = 0.991358$$

$$U_{min} = 0.498767 * V_{cc}$$

$$U_{ripple} = 0.002169 * V_{cc} = 10.85 \text{mV}$$

$$U_{max} = 0.501085 * V_{cc}$$

$$U_{min} = 0.498915 * V_{cc}$$