



Design Equations

$$U_{inmax} = \frac{V_{dd}}{2} * \left[1 + \frac{R_1}{R_2} - \frac{R_1}{R_3} + \frac{R_1}{R_4} \right]$$

$$U_{inmin} = \frac{V_{dd}}{2} * \left[1 - \frac{R_1}{R_2} - \frac{R_1}{R_3} + \frac{R_1}{R_4} \right]$$

Step 1

Select U_{inmax} , U_{inmin} and R_1 and calculate R_2

$$U_{inmax} - U_{inmin} = V_{dd} * \frac{R_1}{R_2} \longrightarrow R_2 = \frac{V_{dd}}{U_{inmax} - U_{inmin}} * R_1$$

$$U_{inmax} + U_{inmin} = V_{dd} * \left[1 - \frac{R_1}{R_3} + \frac{R_1}{R_4} \right]$$

Step 2

If $(U_{inmax} + U_{inmin}) > V_{dd}$

$$R_3 = \infty \quad (\text{eg. leave } R_3 \text{ out})$$

$$R_4 = \frac{V_{dd}}{(U_{inmax} + U_{inmin}) - V_{dd}} * R_1$$

If $(U_{inmax} + U_{inmin}) < V_{dd}$

$$R_4 = \infty \quad (\text{eg. leave } R_4 \text{ out})$$

$$R_3 = \frac{V_{dd}}{V_{dd} - (U_{inmax} + U_{inmin})} * R_1$$

If $(U_{inmax} + U_{inmin}) = V_{dd}$

$$R_3 = \infty \quad (\text{eg. leave } R_3 \text{ out})$$

$$R_4 = \infty \quad (\text{eg. leave } R_4 \text{ out})$$

Step 3

Calculate $1/R_p$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

Step 4

Calculate C_p and C for input bandwidth F_{in}

$$C_p = \frac{1}{2 * \pi * F_{in}} * \frac{1}{R_p}$$

$$C = C_p / 2$$

Step 5

Calculate oversample frequency for given bit resolution N

$$F_s = \frac{2^{N-2}}{C_p * R_p}$$

Calculate total conversion time

$$T_c = \frac{2^N}{F_s} = 4 * C_p * R_p$$