



Design Equations

$$U_{inmax} = \frac{V_{dd}}{2} * \left[1 + \frac{R_1}{R_2} - \frac{R_1}{R_3} + \frac{R_1}{R_4} \right]$$

$$U_{inmin} = \frac{V_{dd}}{2} * \left[1 - \frac{R_1}{R_2} - \frac{R_1}{R_3} + \frac{R_1}{R_4} \right]$$

Step 1

Select U_{inmax} , U_{inmin} and R_1 and calculate R_2

$$U_{inmax} - U_{inmin} = V_{dd} * \frac{R_1}{R_2} \longrightarrow R_2 = \frac{V_{dd}}{U_{inmax} - U_{inmin}} * R_1$$

$$U_{inmax} + U_{inmin} = V_{dd} * \left[1 - \frac{R_1}{R_3} + \frac{R_1}{R_4} \right]$$

Step 2

If $(U_{inmax} + U_{inmin}) > V_{dd}$

$R_3 = \infty$ (eg. leave R_3 out)

$$R_4 = \frac{V_{dd}}{(U_{inmax} + U_{inmin}) - V_{dd}} * R_1$$

$$R_p = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4}} = \frac{V_{dd}}{2 * U_{inmax}} * R_1$$

Step 3

Check U_{inmax} and U_{inmin} for bit resolution N

U_{inmax} must comply to :

$$U_{inmax} < 2^{N-1} * (U_{inmax} - U_{inmin})$$

U_{inmin} must comply to :

$$U_{inmin} > V_{dd} - 2^{N-1} * (U_{inmax} - U_{inmin})$$

If $(U_{inmax} + U_{inmin}) < V_{dd}$

$R_4 = \infty$ (eg. leave R_4 out)

$$R_3 = \frac{V_{dd}}{V_{dd} - (U_{inmax} + U_{inmin})} * R_1$$

$$R_p = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{V_{dd}}{2 * V_{dd} - 2 * U_{inmin}} * R_1$$

Step 4

Calculate C for sample frequency F_s and bit resolution N

$$C = \frac{2^N}{4 * R_2 * F_s} * \frac{1}{1 + \frac{1}{3} * k^2}$$

$$k = \frac{R_2}{2^N * R_p} \quad (\text{note: } k < 1 \text{ if step 3 succeeded})$$

If $(U_{inmax} + U_{inmin}) = V_{dd}$

$R_3 = \infty$ (eg. leave R_3 out)

$R_4 = \infty$ (eg. leave R_4 out)

$$R_p = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{V_{dd}}{V_{dd} + U_{inmax} - U_{inmin}} * R_1 = \frac{V_{dd}}{2 * U_{inmax}} * R_1$$

Step 5

Calculate total conversion time T_c

$$T_c = \frac{2^N}{F_s}$$