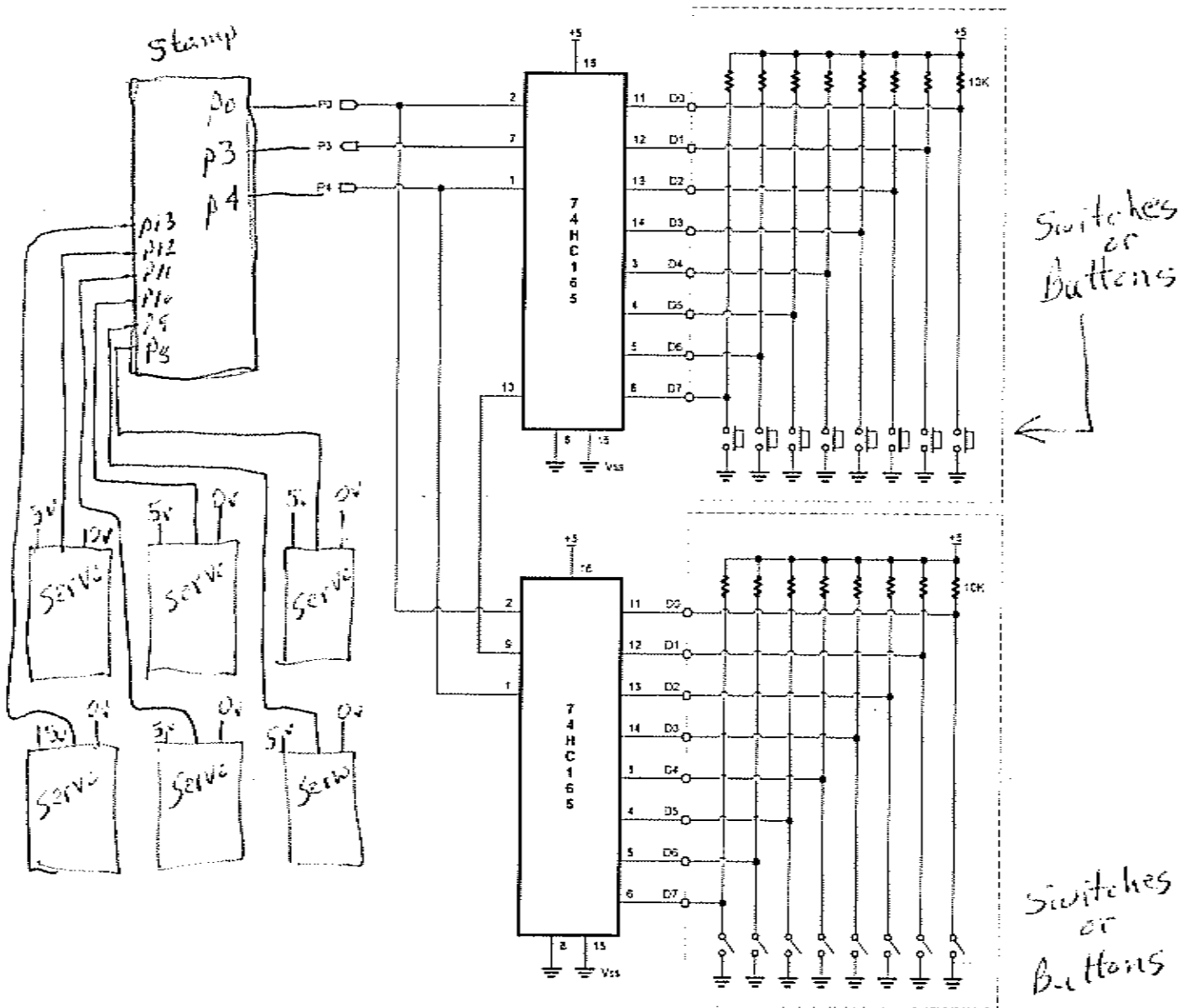


Experiment #24b: Expanded Inputs

Building The Circuit (Note that schematic is NOT chip-centric)



total of 16 switch inputs
and 6 servo outputs.