

# TLC5924 Precharge FET Eliminates Ghosting in Time-Multiplexed LED Displays

Jatan Naik

PMP - Portable Power

## ABSTRACT

LED drivers are often used in visual applications that require time-multiplexing of numerous LEDs in the display. Time-multiplexing is a scheme that involves connecting the cathodes of multiple LEDs to each OUT pin of the LED driver. A time-multiplexed circuit is advantageous because it uses fewer LED drivers for a given amount of LEDs, which results in lower cost and smaller size. One major drawback to time-multiplexing is a side-effect called *ghosting*. The ghosting phenomenon is caused by stray board capacitance which can force time-multiplexed LEDs to flash when they should be off. This application report discusses the precharge FET feature on the Texas Instruments TLC5924 which eliminates the ghosting effect, allowing for cleaner imagery on the LED display. It should be read by users wishing to evaluate the differences between the TLC5923 and TLC5924 as well as users interested in time-multiplexed LED displays.

## Contents

1	LED Output Topologies .....	1
2	Ghosting Effect.....	4
3	Conclusion.....	6
4	References .....	6


## List of Figures

1	TLC5923 With Single LED per Output.....	2
2	Time-Multiplexing Topology .....	3
3	Time-Multiplexing With the TLC5923 .....	4
4	Time-Multiplexing Waveforms.....	5
5	TLC5924 Precharge FET .....	6

## 1 LED Output Topologies

### 1.1 Single LED per Output

Most LED drivers are used in applications where only one LED is connected to each output of the LED driver. This type of scheme is ideal for applications where size is not a factor and a small number of LEDs are being used. One advantage of this topology is that the code used to program the LED driver can be relatively simple, because it does not have to switch external FETs as in a time-multiplexed system. The TLC5923 is an excellent choice of LED driver for a system using one LED per output. [Figure 1](#) demonstrates a TLC5923 in this topology.

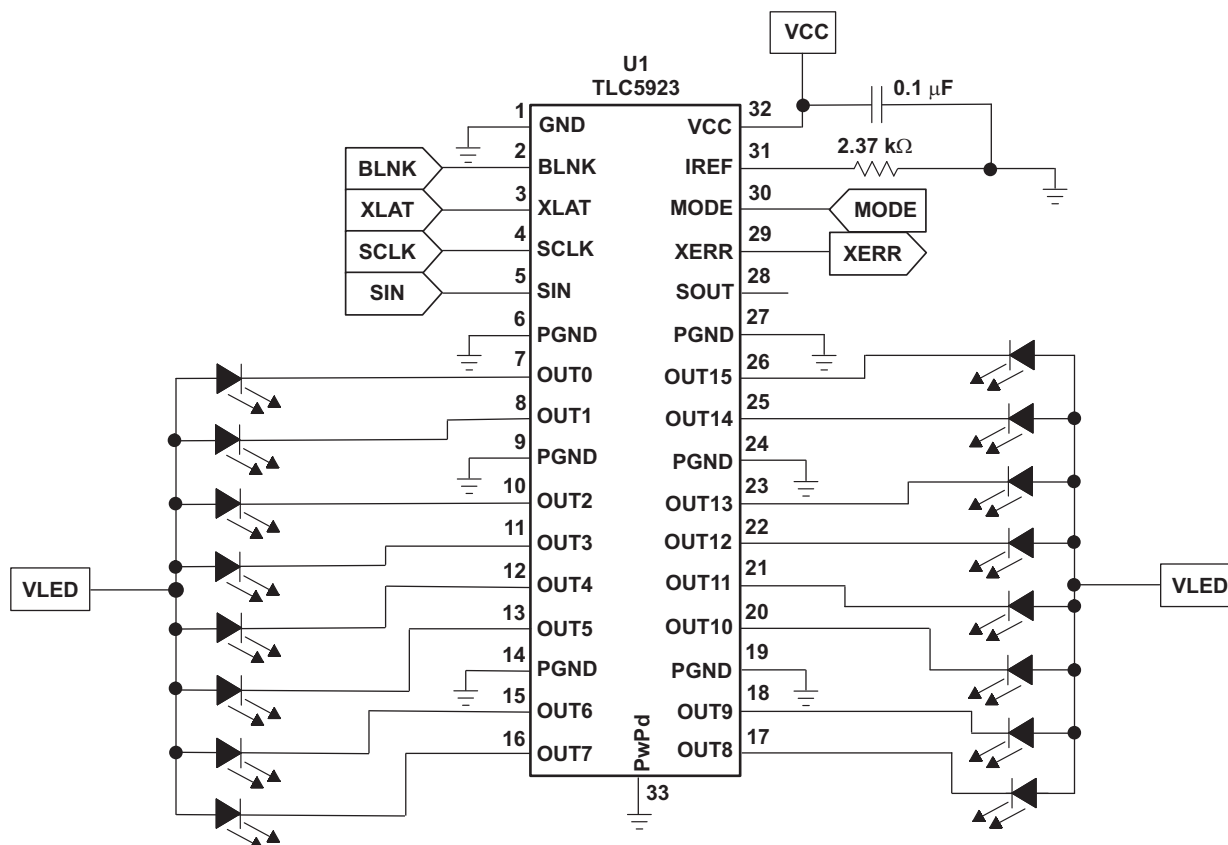


**Figure 1. TLC5923 With Single LED per Output**

As shown in [Figure 1](#), the cathode of each LED is connected to a different output pin on the TLC5923, and the anodes of the LEDs are connected to a single voltage source (VLED). Each TLC5923 output controls the current flowing through each LED and therefore the brightness of all 16 LEDs. The input control pins (BLNK, XLAT, SCLK, SIN, MODE) program the current for each of its 16 outputs. See the TLC5923 data sheet for a more detailed description of its programming.

## 1.2 Time-Multiplexing

Using one LED driver per 16 LEDs may not be a practical solution in display systems that require a large amount of LEDs. Instead, the concept of time-multiplexing can be used so that multiple LEDs are connected to each LED driver's output. [Figure 2](#) demonstrates this concept:

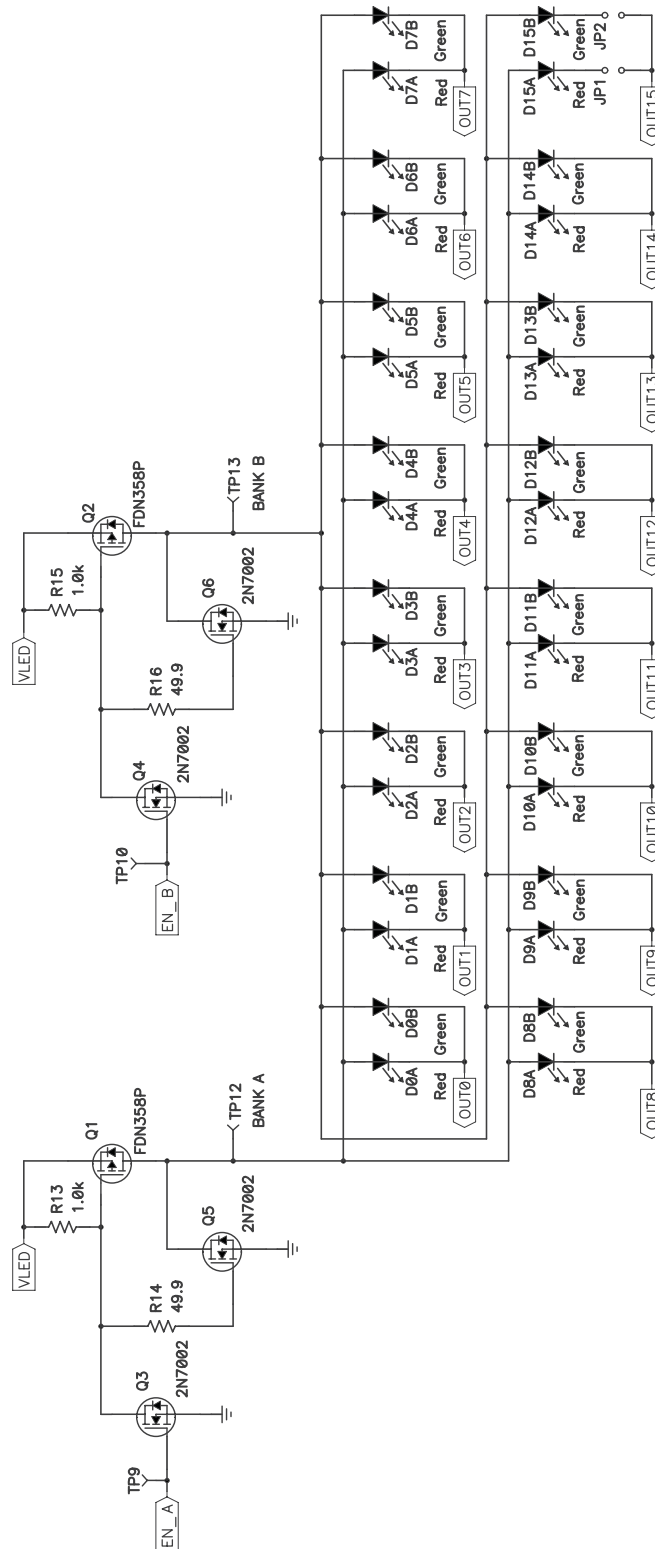


**Figure 2. Time-Multiplexing Topology**

In [Figure 2](#), two LEDs are connected to each LED driver output (the LED driver is not shown in the figure). In this system, a microcontroller controls the EN\_A and EN\_B signals so that the VLED voltage is only applied to one LED on each output. Because EN\_A and EN\_B are never active at the same time, only the red or green LEDs are controlled by the IC at any given instant. The other set of LEDs are turned off by transistor Q5 or Q6, which ties the anodes of the disabled LEDs to ground. If the LED driver is programmed to multiplex between the two rows of LED fast enough, the user does not see the LEDs turn on and off, resulting in the illusion of both red and green LEDs being on at the same time. Multiplexing between the red and green LEDs faster than 100 Hz is fast enough that the switching is not visible. If a single LED per output topology had been used to drive the 32 LEDs in [Figure 2](#), then two LED drivers would have been necessary instead of only one. In an application where hundreds or thousands of LEDs are required, time-multiplexing offers obvious benefits, because the time-multiplexed topology is cheaper and smaller than a nontime-multiplexed topology where each LED requires a separate driver output. However, a time-multiplexed topology requires more complicated programming of the LED driver, as well as additional external parts such as the switching MOSFETs.

## 2 Ghosting Effect


### 2.1 Description

A time-multiplexed topology has another disadvantage called the *ghosting effect* if the proper LED driver is not selected for the application. This ghosting phenomenon causes time-multiplexed LEDs to emit a brief flash of light when they should be off. In display applications, the images on the display appear illuminated at improper times, resulting in poor image quality. This phenomenon is caused by several factors, mainly the differences in the forward voltage drops of the LEDs coupled with the stray capacitance on the PCB and cabling. [Figure 3](#) illustrates this parasitic capacitance.

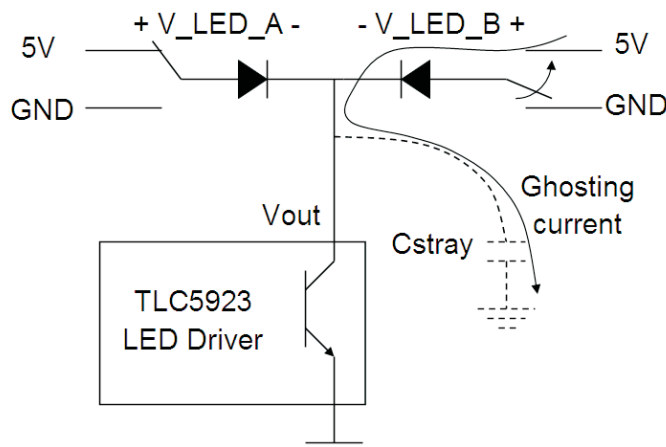

**Figure 3. Time-Multiplexing With the TLC5923**

For simplification, only one output pin and two LEDs are shown in the [Figure 3](#). Additionally, the six transistors in [Figure 2](#) are replaced with two switches that serve the same function. The value of VLED in [Figure 2](#) is assumed to be 5 V in [Figure 3](#). [Figure 4](#) illustrates the timing waveforms and highlights the ghosting effect.

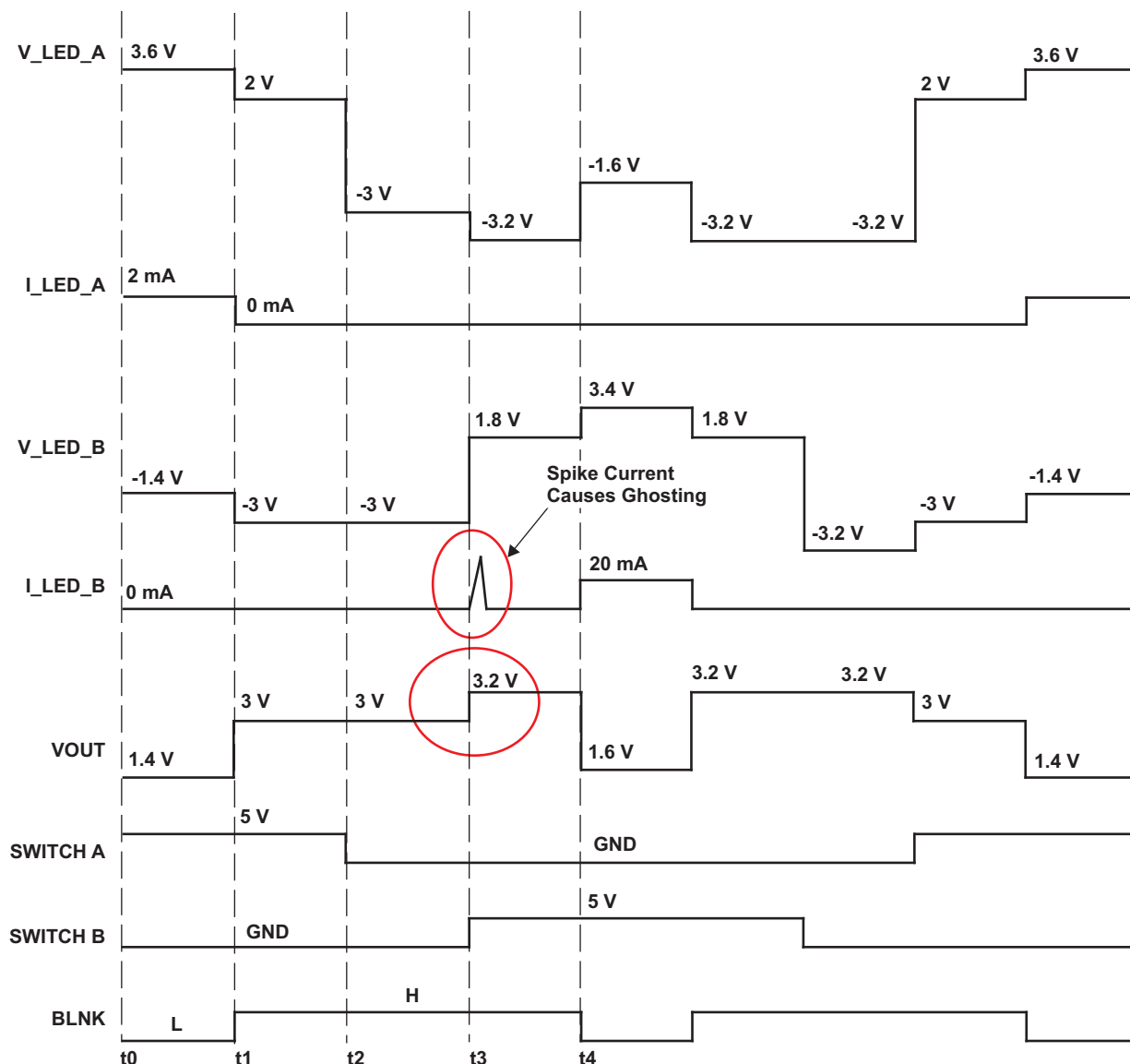

**Figure 4. Time-Multiplexing Waveforms**

The following assumptions were made for [Figure 4](#).

- LEDA has a forward voltage drop of 3.6 V at approximately 20 mA.
- LEDA has a forward voltage drop of 2 V when OUT is open drain (no current flowing through LEDA).
- LEDB has a forward voltage drop of 3.4 V at approximately 20 mA.
- LEDB has a forward voltage drop of 1.8 V when OUT is open drain (no current flowing through LEDB).


At time  $t_0$ , switch A is tied to 5 V so that current flows through LEDA (switch B is tied to GND). BLNK is high at  $t_1$ , forcing the LEDs off. The voltage on VOUT rises to 3 V because  $V_{LED\_A}$  equals 2 V at 0 mA. At  $t_2$ , switch A is tied to GND, forcing  $V_{LED\_A}$  to -3 V. At time  $t_3$ , switch B turns on while the BLNK signal is high. This causes the voltage on VOUT to jump from 3 V to 3.2 V, because the forward voltage drop of LEDB is 1.8 V and the anode of LEDB is switched to 5 V. Because the OUT pin is open drain as a result of BLNK being asserted, the voltage on VOUT can only be raised to 3.2 V by the charging of the stray capacitance. In order for this to happen, current must flow into the stray capacitance, and the only path available for this current is through LEDB. Therefore, LEDB flashes briefly (even though BLNK is asserted). This flash is the unwanted ghosting effect. The red circles in [Figure 4](#) highlight the moment at which the ghosting effect occurs.

## Conclusion

To summarize, the ghosting effect occurs when VOUT transitions from a lower voltage to a higher voltage while BLNK is asserted. The exact amplitude, duration, and timing of the ghost current spike in LEDB depends on the amount of stray capacitance in the circuit, the forward voltage characteristics of the LEDs, and the timing characteristics of the second switch.

## 2.2 Solution

The Texas Instruments TLC5924 contains an innovative precharge FET feature which eliminates the ghosting effect from multiplexed LED displays. Figure 5 illustrates this feature.

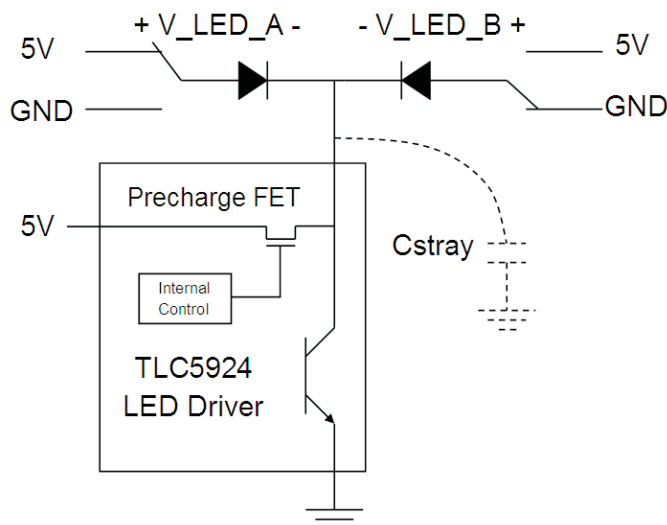

**Figure 5. TLC5924 Precharge FET**

Each output pin of the TLC5924 is connected to an external voltage source (VUP) through its own internal precharge FET. This FET is switched on when BLNK is asserted so that OUT is pulled up to the voltage on the VUP pin. Therefore, the FET provides an alternate path for the current to charge the stray capacitance. Instead of flowing through LEDB, the current flows through the precharge FET from the VUP pin. This prevents the current spike from flowing through LEDB, which eliminates the ghosting effect.

## 3 Conclusion

Time-multiplexing LEDs reduce system level cost and minimize board area by reducing the number of LED drivers in a display. However, it also introduces a problem called ghosting that can degrade video quality. The TLC5924 contains precharge FETs that eliminate ghosting and help maintain high video quality in time-multiplexed systems.

## 4 References

1. Day, Michael, *Time Multiplexed LED Display Architecture—Improving Image Quality by Reducing Ghosting*. The 1<sup>st</sup> International Conference on Display LEDs. February 2007.
2. TLC5924, 16-Channel LED Driver With DOT Correction and Pre-Charge FET data sheet ([SLVS626](#)).
3. TLC5923, 16-Channel LED Driver With DOT Correction data sheet ([SLVS550](#))

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

<b>Products</b>		<b>Applications</b>	
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>	Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>	Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>	Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>	Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>	Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>	Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>	Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>	Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Low Power Wireless	<a href="http://www.ti.com/lpw">www.ti.com/lpw</a>	Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
		Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2007, Texas Instruments Incorporated