



Notes: when existing ± 5 volt signal is + on top,
 D1 conducts and pulls in Rly1.
 Rly1-NO closes, Rly1-NC opens and motor
 runs in one direction.
 when existing \pm volt signal reverses (- on top).
 Rly2 pulls in, Rly2-NO closes, Rly2-NC opens
 and motor runs in opposite direction.