

DESIGN 1 ALTERNATIVE TRANSISTORS

This design uses 4 transistors. Both inputs must **NEVER** be HIGH (this will create a short-circuit and damage the transistors). However this circuit is a good design. The voltage on the H-Bridge can be any voltage and the control voltage just needs to be higher than 1v. The circuit provides OFF feature when both inputs are LOW but does not provide BRAKE feature.

