
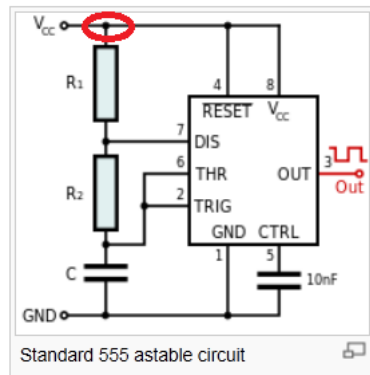


ADC w/Propeller & 555 timer

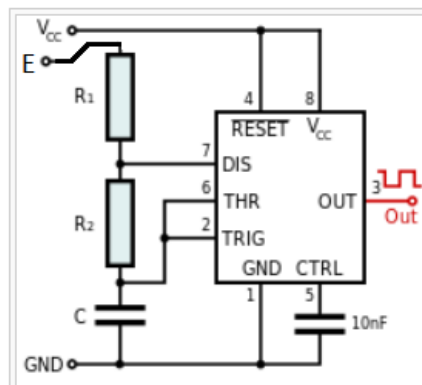If we take the standard 555 *a-stable circuit* and modify it by removing R_1 from V_{cc} (red circle in figure)



You end up with this circuit (see figure below) able to detect voltages greater the V_{cc} when connect to the terminal labeled E .




VCO using 555

When constructed with $R_1=470K\text{-ohm}$ and $R_2=10K\text{-ohm}$ and $C=.1\ \mu\text{F}$ you should get similar results, if $V_{cc} = 5\text{v}$. Connect *output pin 3* through a $10K\text{-ohm}$ resistor to any pin on your *propeller*, should you decide to follow along.

Proving the ‘change’ of behavior takes a little bit of math, and I hope I got it right. I use to have a book named *555 timer cook book* (don’t recall authors name), that gave a great break down of the timer operation and its math. And now, I don’t. It was tossed out by accident as a relative was ‘doing a charitable deed’.

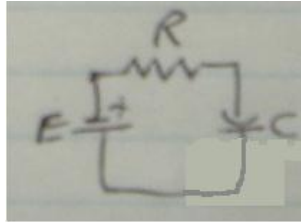So, this was a good excuse for me to dig out my physics book and stretch that area of the brain again. Given a circuit such as shown here:



RC circuit

$$E = IR + V_C$$

Eq-1

But when rewritten with 'charge' q instead:

$$I = \frac{dq}{dt}$$

and

$$V_C = \frac{q}{C}$$

This yields the following expression:

$$E = \frac{dq}{dt} R + \frac{q}{C}$$

$$\frac{dq}{dt} = \frac{E - \frac{q}{C}}{R}$$

or

$$\frac{dq}{dt} = \frac{EC - q}{RC}$$

And finally

$$\frac{dq}{EC - q} = \frac{dt}{RC}$$

(eq-2)

And this last step I hadn't done in a while! Now the expression in eq-2 can be integrated.

$$\int_{q_1}^{q_2} \frac{1}{EC - q} dq = \frac{1}{RC} \int_0^t dt$$

Here, because of the 555 and a V_{cc} of $5v$, we have two *fixed* charges for q_1 and q_2 .

$$q_1 = \frac{5C}{3} \quad \& \quad q_2 = \frac{10C}{3} \quad \text{and will not vary with } E.$$

This leads us two definite integrals:

$$-\ln(EC - q_2) - (-\ln(EC - q_1)) = \frac{t}{RC}$$

Combining log's, yields:

$$\ln\left(\frac{EC - \frac{5C}{3}}{EC - \frac{10C}{3}}\right) = \frac{t}{RC}$$

After simplifying:

$$\ln\left(\frac{3E - 5}{3E - 10}\right) = \frac{t}{RC}$$

Which leads to this expression:

$$t = \ln\left(\frac{3E - 5}{3E - 10}\right) RC$$

Now, I should point out that this expression is just the 'charge' time and not the discharge time. In fact, the software I use (and may be attached) reads only the charge time.

Before we get too far ahead of ourselves, let's test this last expression with $E = 5v$. And see what it yields?

$$t = \ln\left(\frac{15 - 5}{15 - 10}\right) RC = \ln(2) RC$$

This last part $\ln(2)RC$ you can look up as the charge time t of an astable timer using the 555.


So the expression:

$$t = \ln\left(\frac{3E - 5}{3E - 10}\right) RC$$


Can be used to predict behavior for $E > 5$ in a table:

E	t/RC	E	t/RC
5	0.693147	15	0.133531
6	0.485508	16	0.123614
7	0.374693	17	0.115069
8	0.305382	18	0.107631
9	0.257829	19	0.101096
10	0.223144	20	0.09531
11	0.19671	21	0.090151
12	0.175891	22	0.085522
13	0.159065	23	0.081346
14	0.145182	24	0.077558

In graph form this appears as:

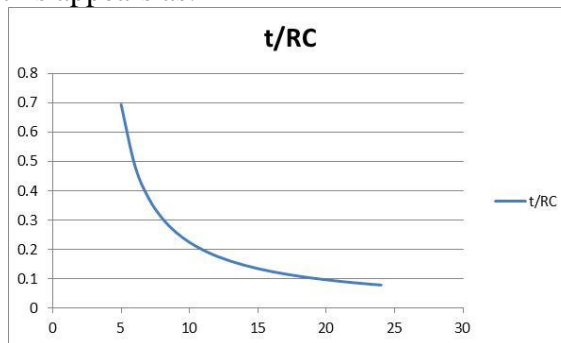

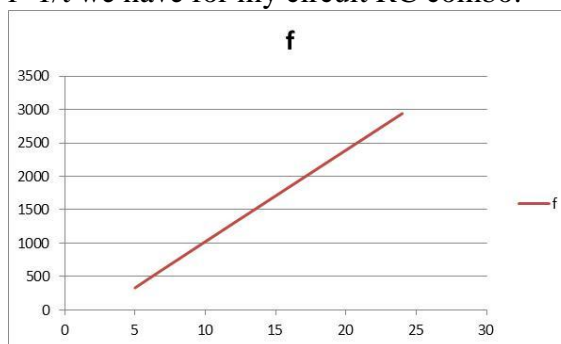When plotting $f=1/t$ we have for my circuit RC combo:



My RC circuit yields $f=320 \text{ Hz}$ @ $E=5\text{v}$. But you should get a linear response exactly as I observed in my circuit.