



K1 is Radio Shack 5V reed relay with 1A contact. The contact resistance is really too high for this application. A higher current relay would be better, but would need a driver for the coil.

Battery cell discharge schematic for use with Stamp 2 Microcontroller