

Keywords: bidirectional, current sense amp, current monitor, battery, charge current, discharge current, amplifier, amplifiers, amps

Mar 25, 2003

APPLICATION NOTE 1949

## Bi-directional Current-Sense with Single Output

*Battery operated devices often need to monitor both charge and discharge currents. A dual current-sense amplifier and differential amplifier are combined to produce a single output voltage that indicates magnitude and direction of battery current.*

Systems such as laptop computers and other devices that have internal charge circuitry require a precise bi-directional current-sense amplifier to monitor accurately the battery's current regardless of polarity. The MAX4377 (a dual low-cost current-sense) can be used to produce a bi-directional current monitor.

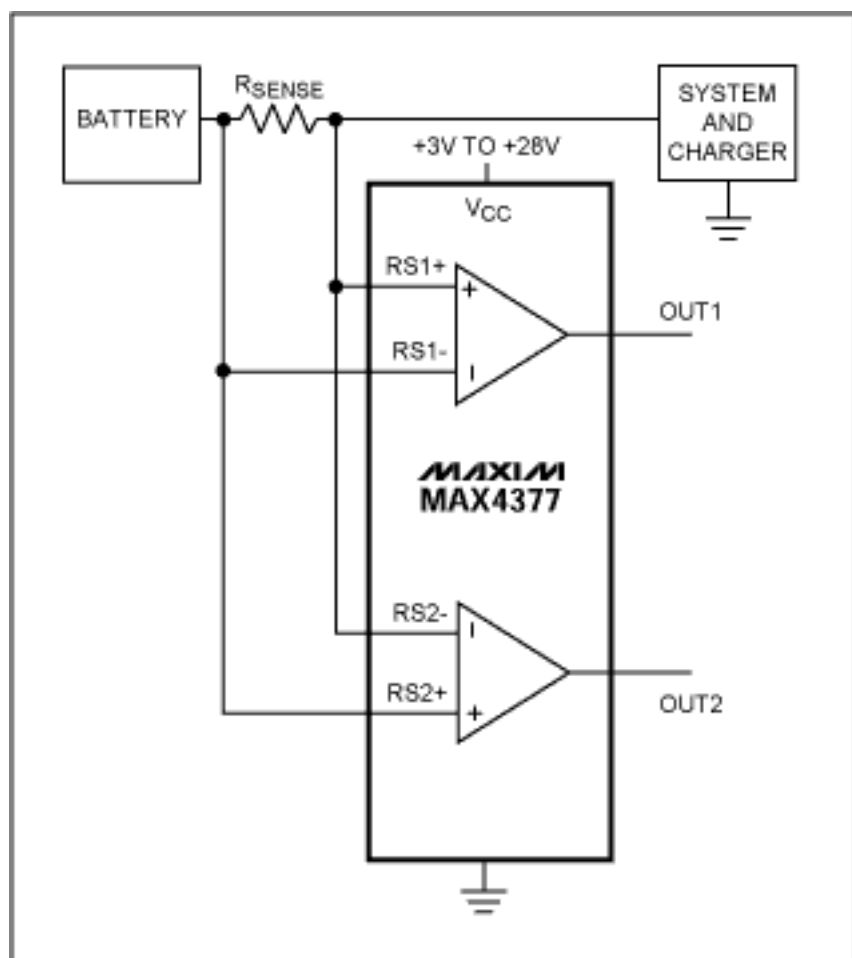


Figure 1.

Output voltage  $OUT_{-}$  is proportional to the magnitude of the sense voltage ( $VRS_{+} - VRS_{-}$ ).  $OUT_{-}$  is approximately zero when  $VRS_{-} > VRS_{+}$ .  
 When  $VRS_{+} > VRS_{-}$ ,  $VOUT = (GAIN)(RSENSE)(ILOAD)$   
 where  $GAIN = 20$  for MAX4377T.

For example,  $R_{SENSE} = 100\text{m}\Omega$  and  $I_{LOAD} = 1\text{A}$  produce, in the case of the MAX4377T, a full-scale output of 2V. However this circuit needs a two channel ADC in order to evaluate the charge and discharge currents. Simply adding a differential amplifier such as the MAX4198 produces a circuit with a single output able to provide the information of charge or discharge current.

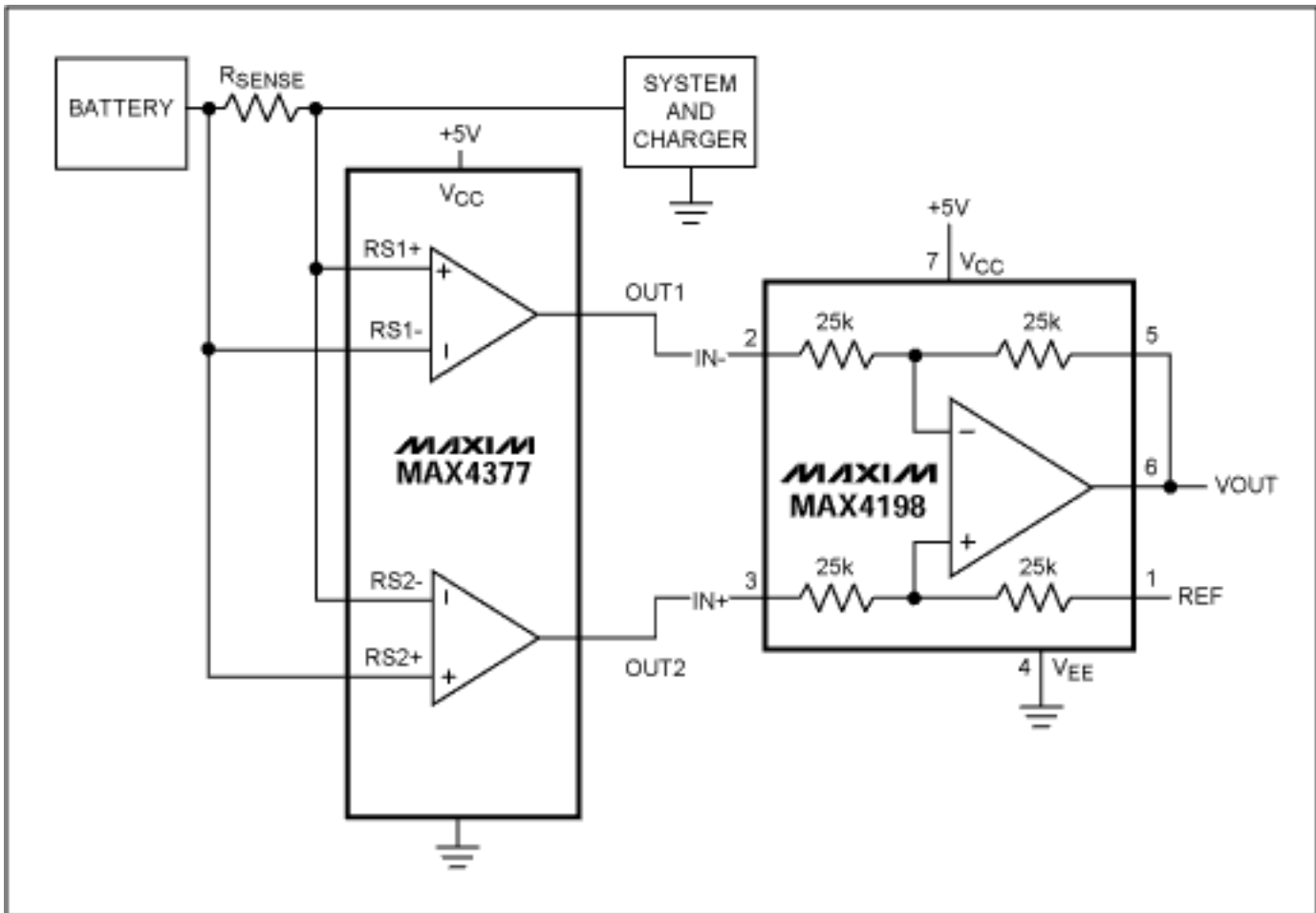


Figure 2.

The output  $V_{out}$  will be  $(OUT2 - OUT1) + REF$ . Using a REF voltage of 2.5V we obtain an output swing from 0.5V to 4.5V (from 2.5V to 4.5V for discharge current and from 2.5V to 0.5V for charge current).

New bi-directional current-sense amplifiers such as the MAX4070, include the differential amplifier and reference on-chip.

A similar version of this article appeared in the September 2, 2002 issue of *Mundo Electronico* magazine.

Application Note 1949: <http://www.maxim-ic.com/an1949>

#### More Information

For technical questions and support: <http://www.maxim-ic.com/support>

For samples: <http://www.maxim-ic.com/samples>

Other questions and comments: <http://www.maxim-ic.com/contact>

#### Related Parts

MAX4070: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX4198: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX4377: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

AN1949, AN 1949, APP1949, Appnote1949, Appnote 1949

Copyright © 2005 by Maxim Integrated Products

Additional legal notices: <http://www.maxim-ic.com/legal>