
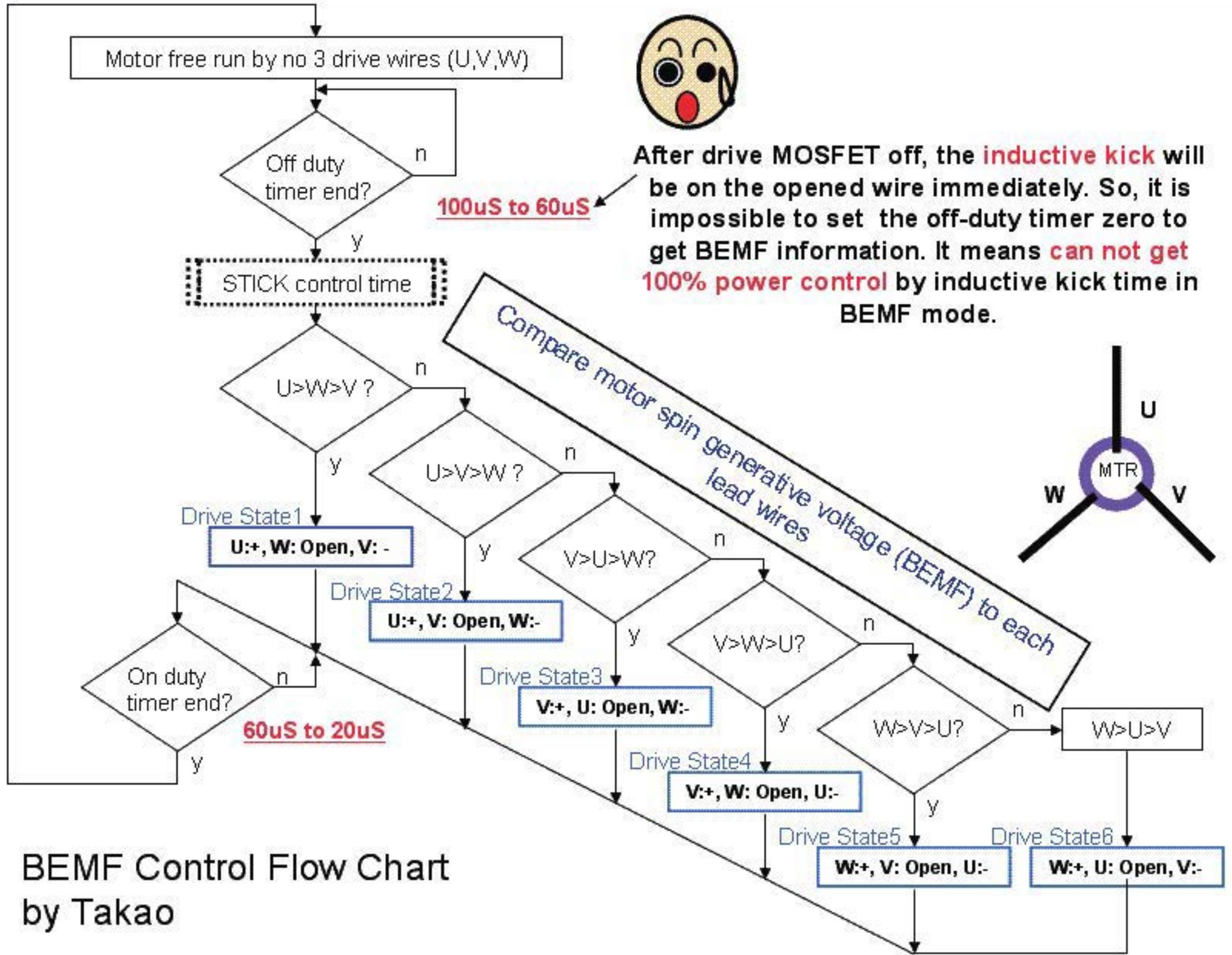


Need the comparator data re-check to get correct data in small signal

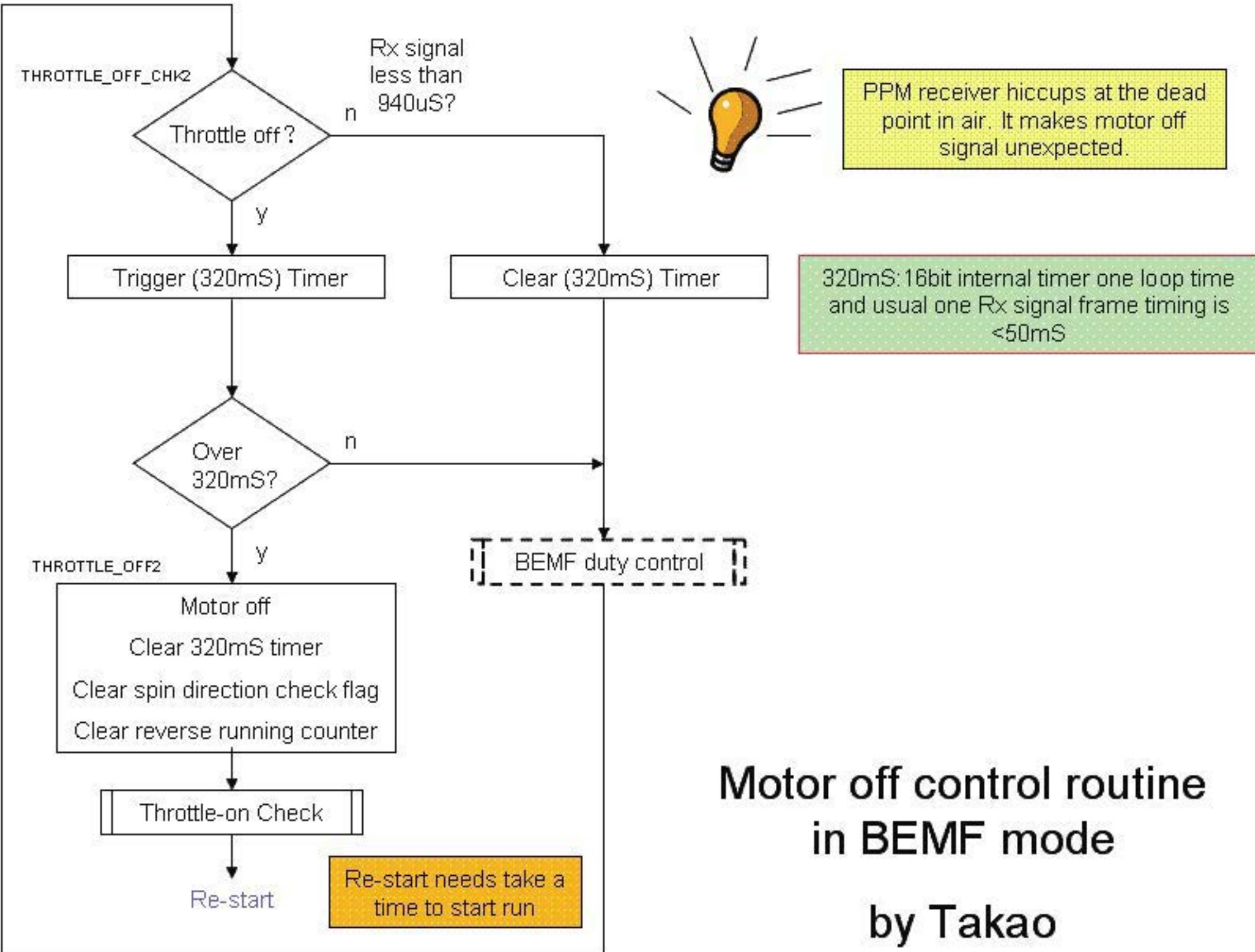
Start sequence for BL-
ESC flow chart by
Takao





Motor off control routine in BEMF mode

by Takao


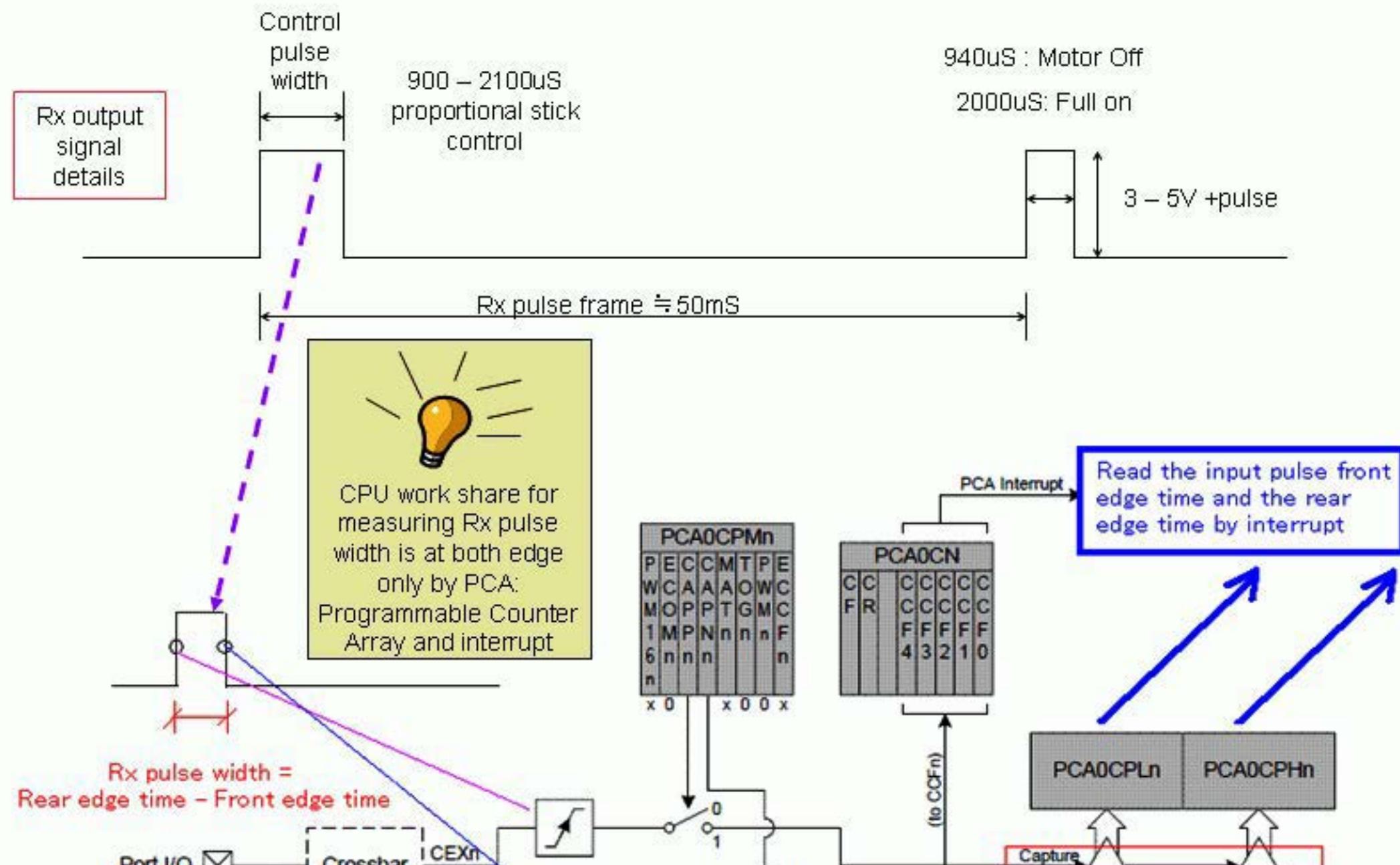


Rx interface details
by Takao

Figure . PCA Capture Mode Diagram


16bit free run 32mS loop counter

Stick Control

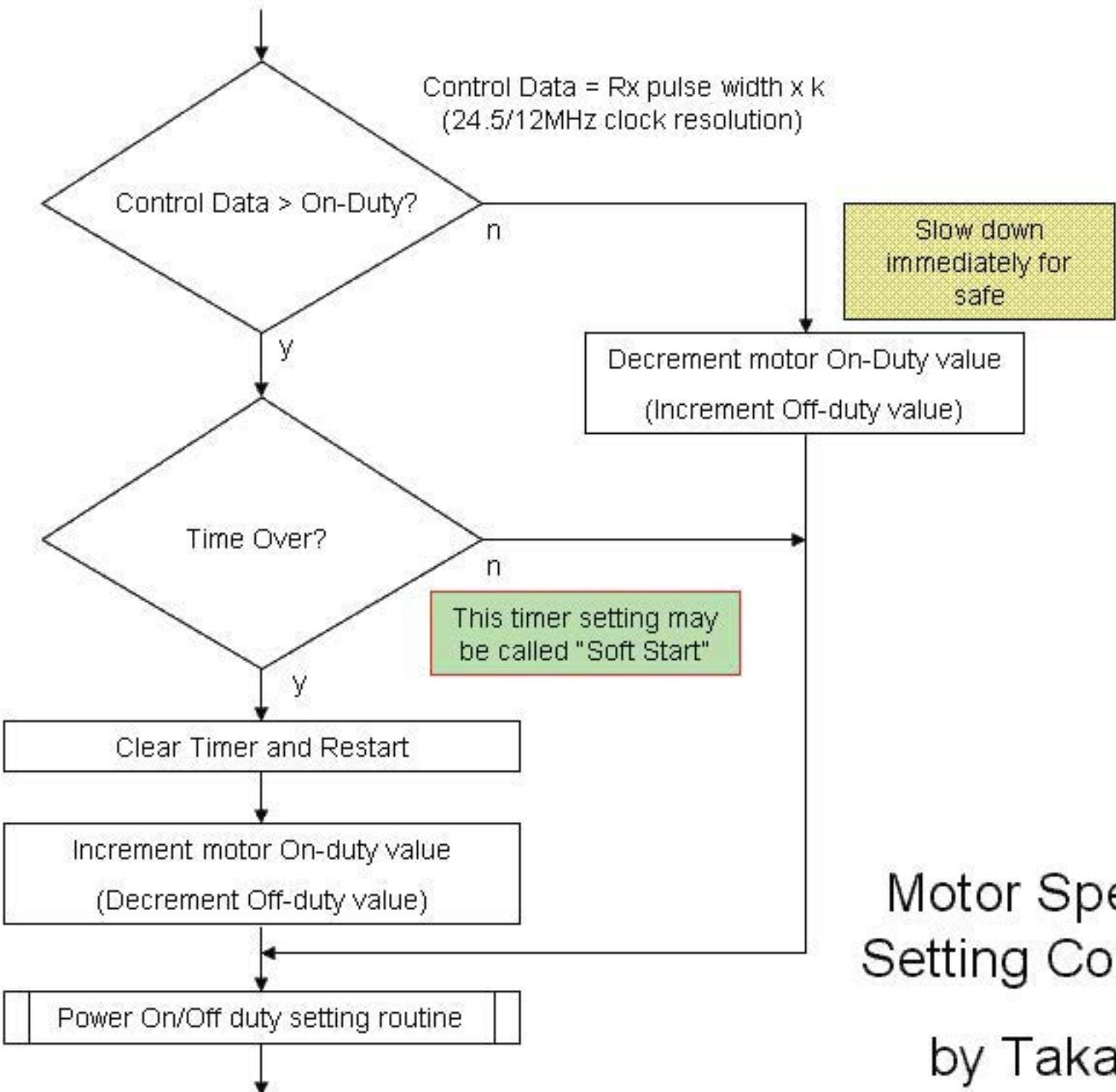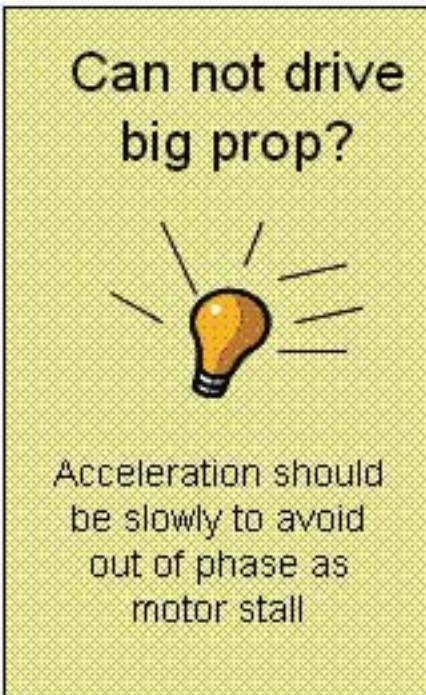

Motor Speed
Setting Control
by Takao

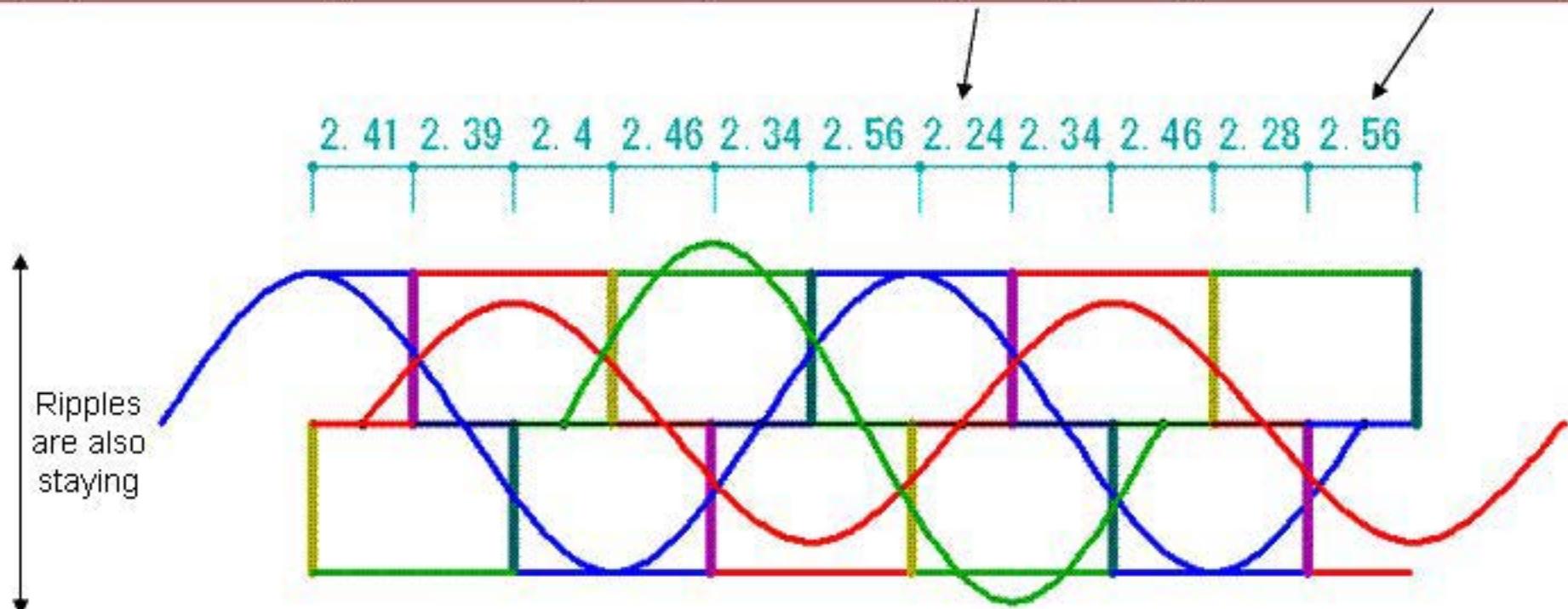
Consider the jitter of each state timing. It is never constant while spinning. Also, mechanical settings as coil turn tolerance, prop balance and magnet force are not precisely constant. Then, you may set ON_DUTY value constant roughly.



The BEMF Sampling time must be less than 1/6 one spin frame time to get drive sync.
I use min. 1/36 by sampling count routine in one frame
(as min. 6 sample counts/state) and adjust sampling frequency automatically by software.



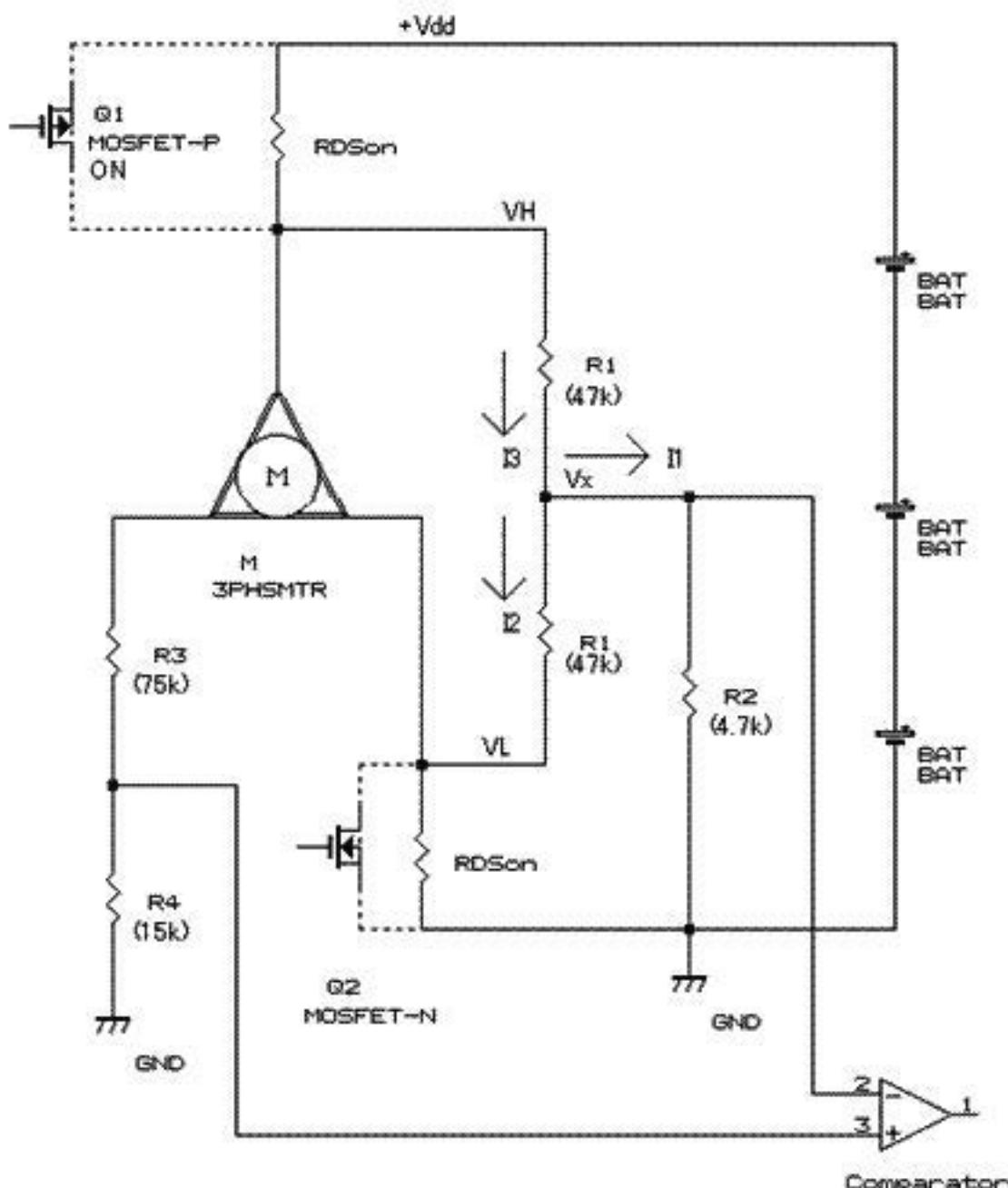Some considerations for spin control by Takao



$$I_3 = (V_H - V_x) / R_1$$

$$I_2 = (V_x - V_L) / R_1$$

$$I_1 = V_x / R_2$$

$$I_3 = I_2 + I_1$$

$$(V_H - V_x) / R_1 = ((V_x - V_L) / R_1) + (V_x / R_2)$$

$$(V_H - V_x) = ((V_x - V_L)) + (V_x \cdot R_1 / R_2)$$

$$V_H + V_L = 2(V_x + V_x \cdot R_1 / R_2)$$

$$\text{Zero Cross Point: } (V_H + V_L) / 2 = V_x(1 + R_1 / 2 \cdot R_2)$$

$$\text{at } R_1 / R_2 : 47k / 4.7k$$

$$\text{Zero Cross Point} = V_x(1 + 10 / 0.2) = 6 \cdot V_x \text{ (= Almost } 1/2 V_{dd})$$

Hence $R_3 : R_4 = 5 : 1$

N and P-channel MOSFET's $R_{ds\text{ on}}(\text{ON})$ Resistance drain-source) should be considered to get precise zero cross point for maximum power control




Precise Zero Cross Point Detection


by Takao

Misfire Check for Zero-Cross Power Control

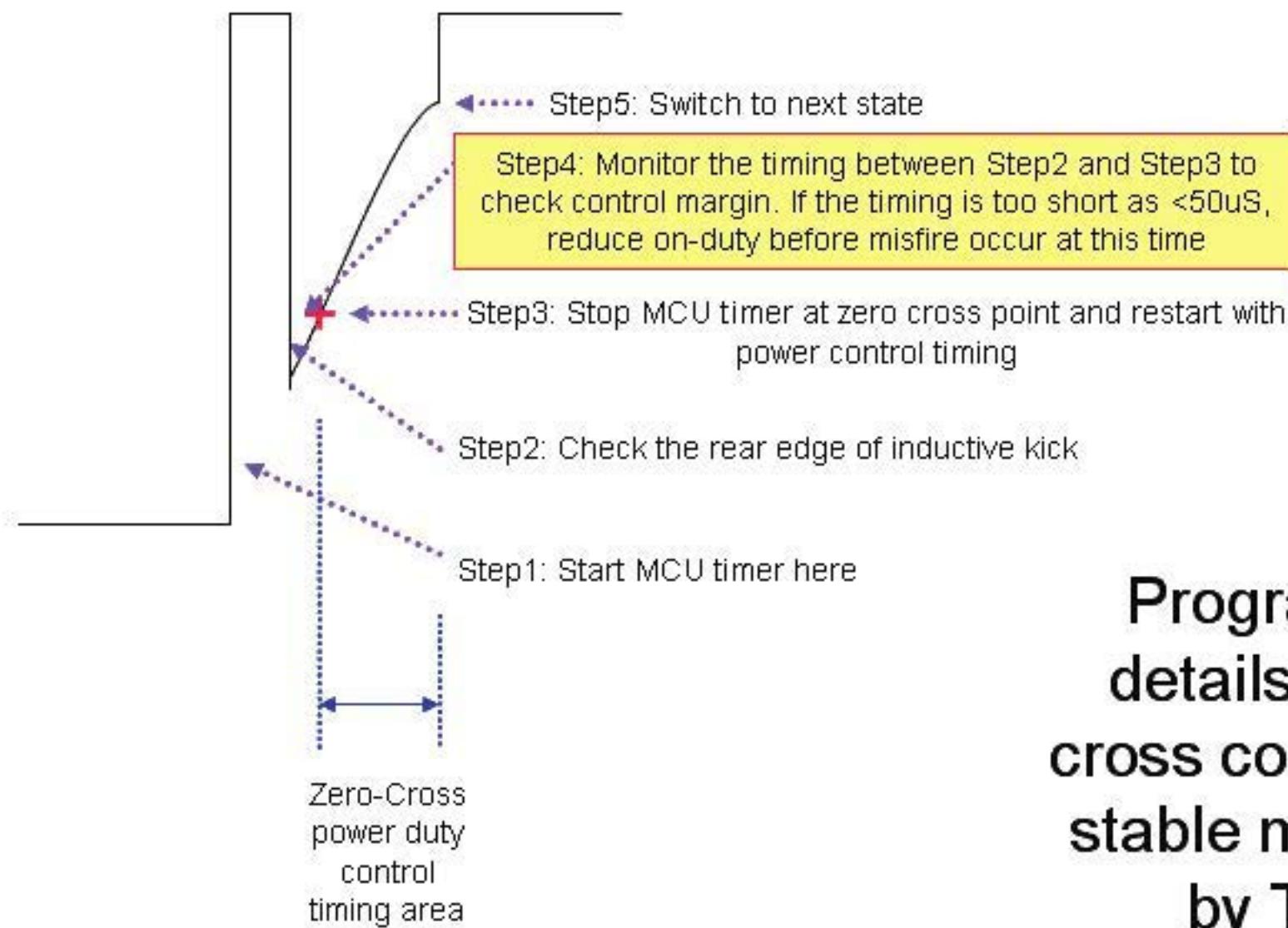The inductive kick is always exist
after MOSFET off




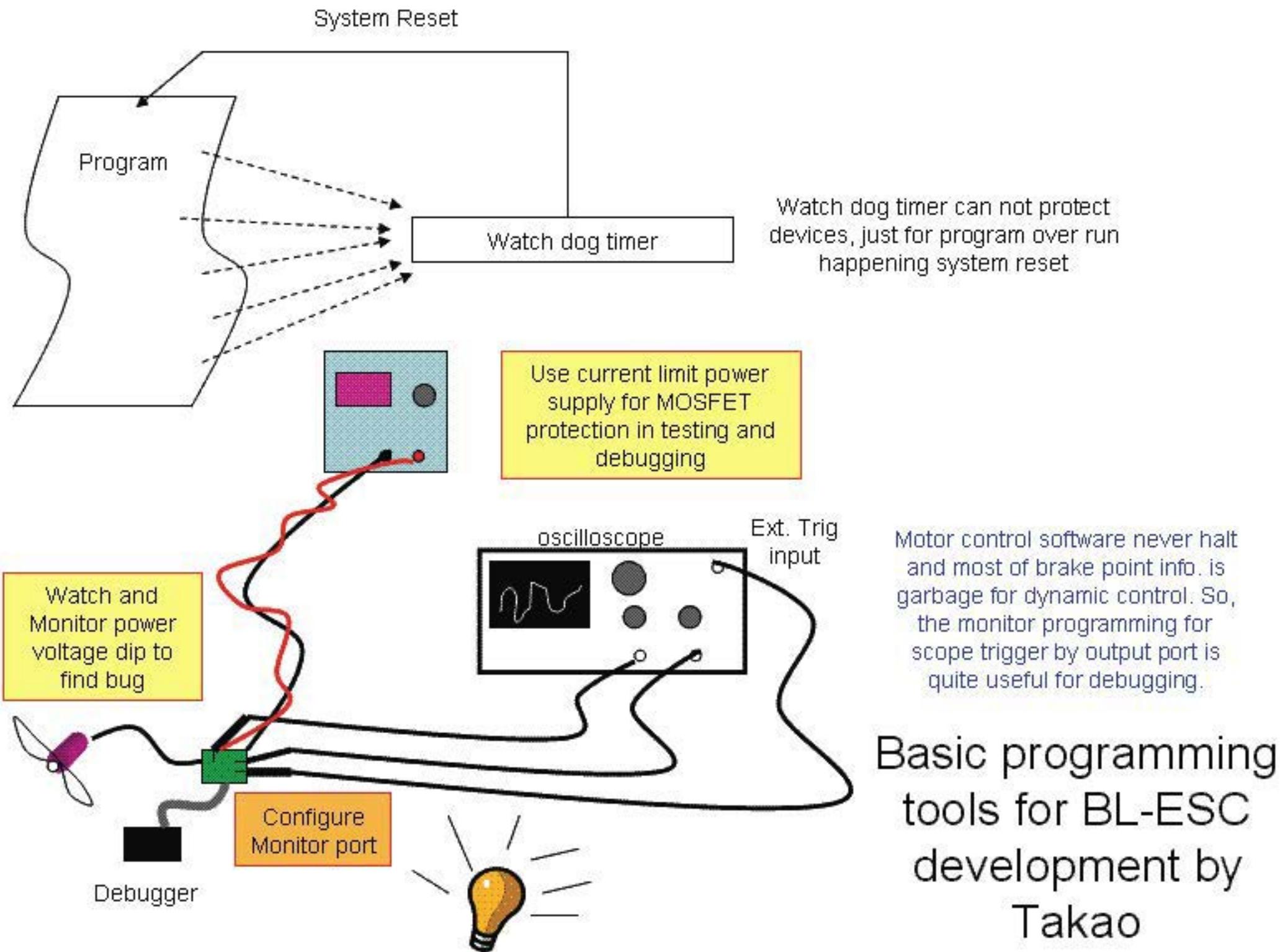**Programming
details for zero
cross control to get
stable max power
by Takao**



Timing Advance in Zero-Cross Power Control

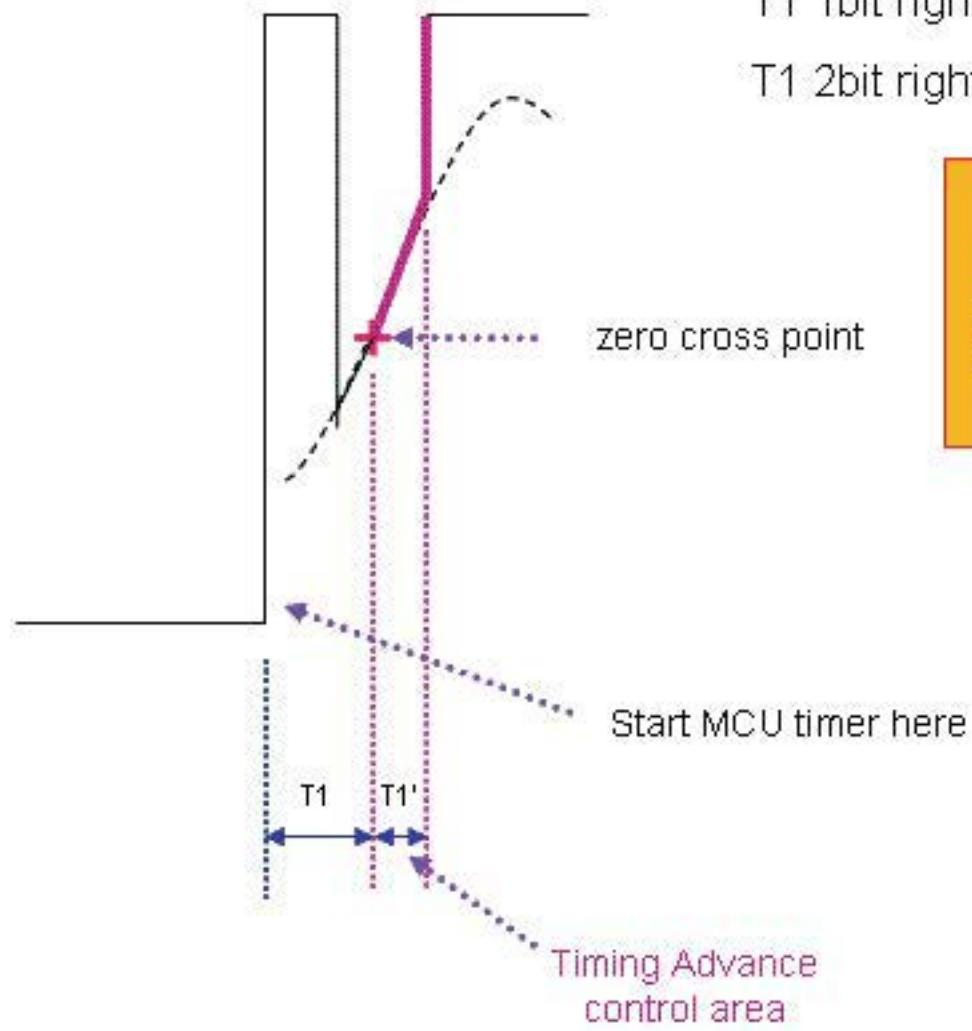The inductive kick is always exist
after MOSFET off



T_1 1bit right shift = T_1' : 25% advance

T_1 2bit right shift = T_1' : 12.5% advance




Timing Advance helps unsymmetrical motor generate sine wave form e.g. magnet field /coil winding tolerance for stable control.


Programming details for Timing Advance control to get stable max power

The battery's internal resistance is very low enough, but the bypass cap on the power line works so great. Why?


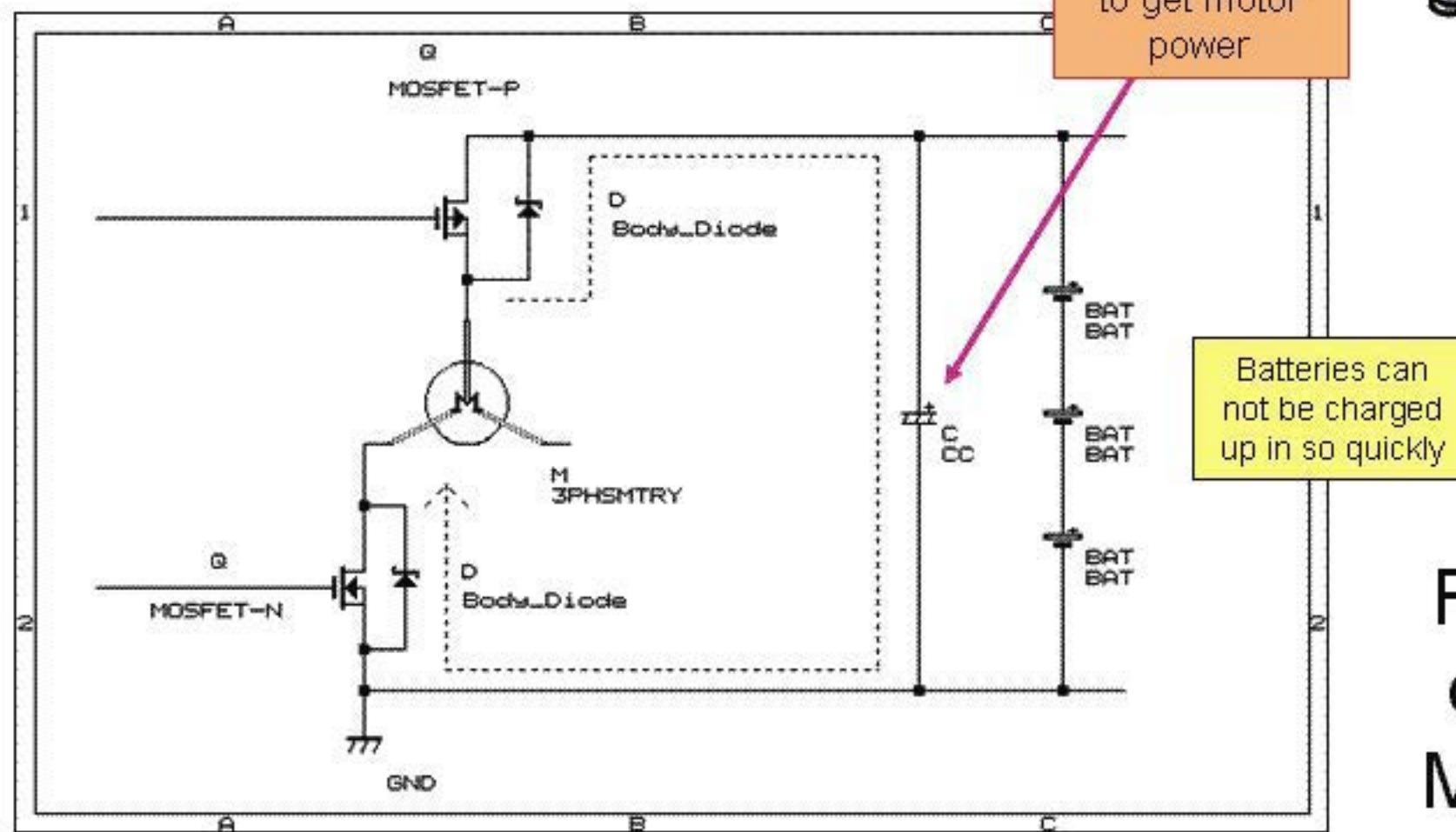
The body avalanche diode as integral reverse p-n diode in MOSFET not only protects MOS device, but also charge-up the capacitor on the power line by inductive power from motor coil.



Flywheel
diode in
MOSFET

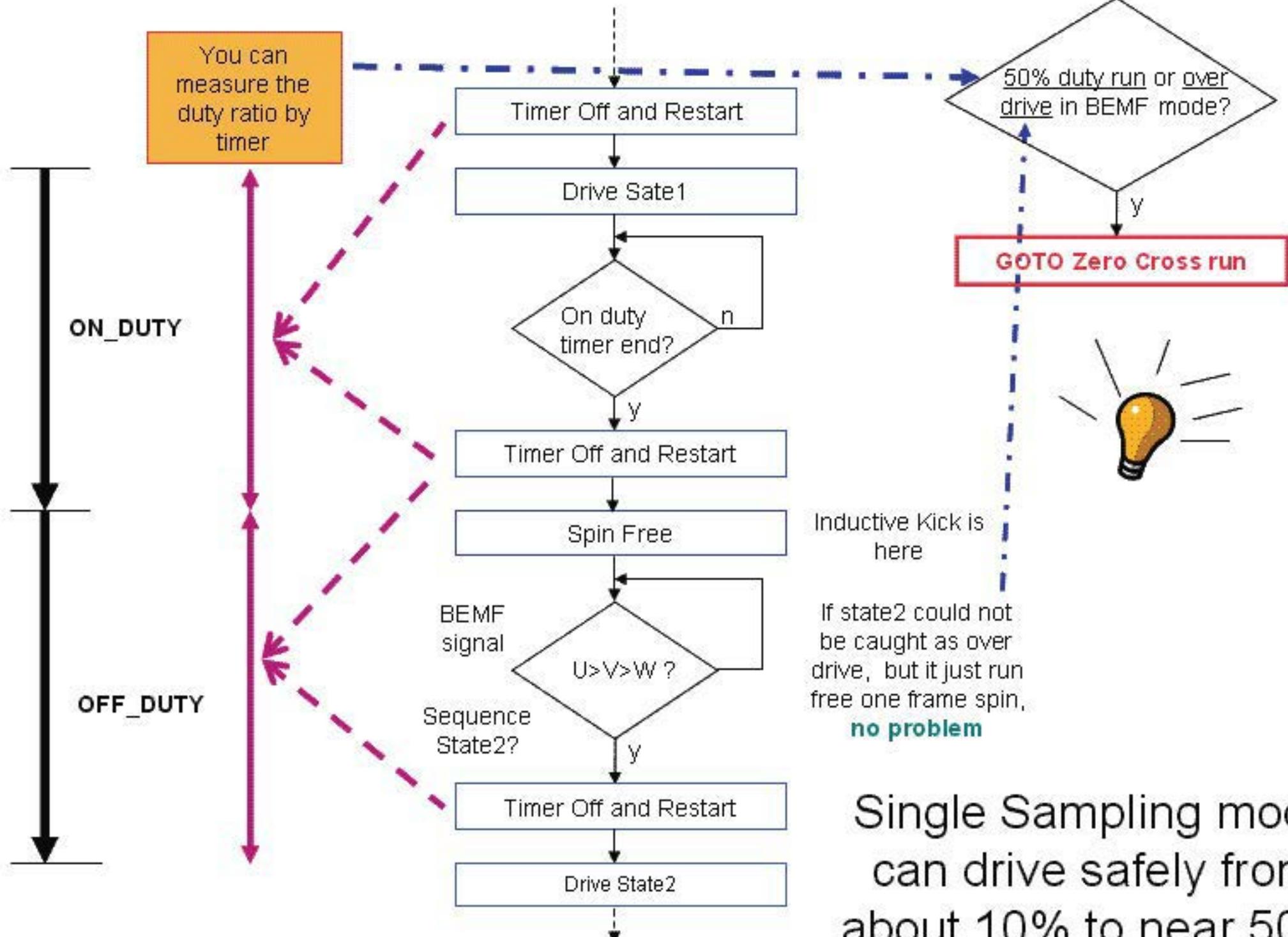


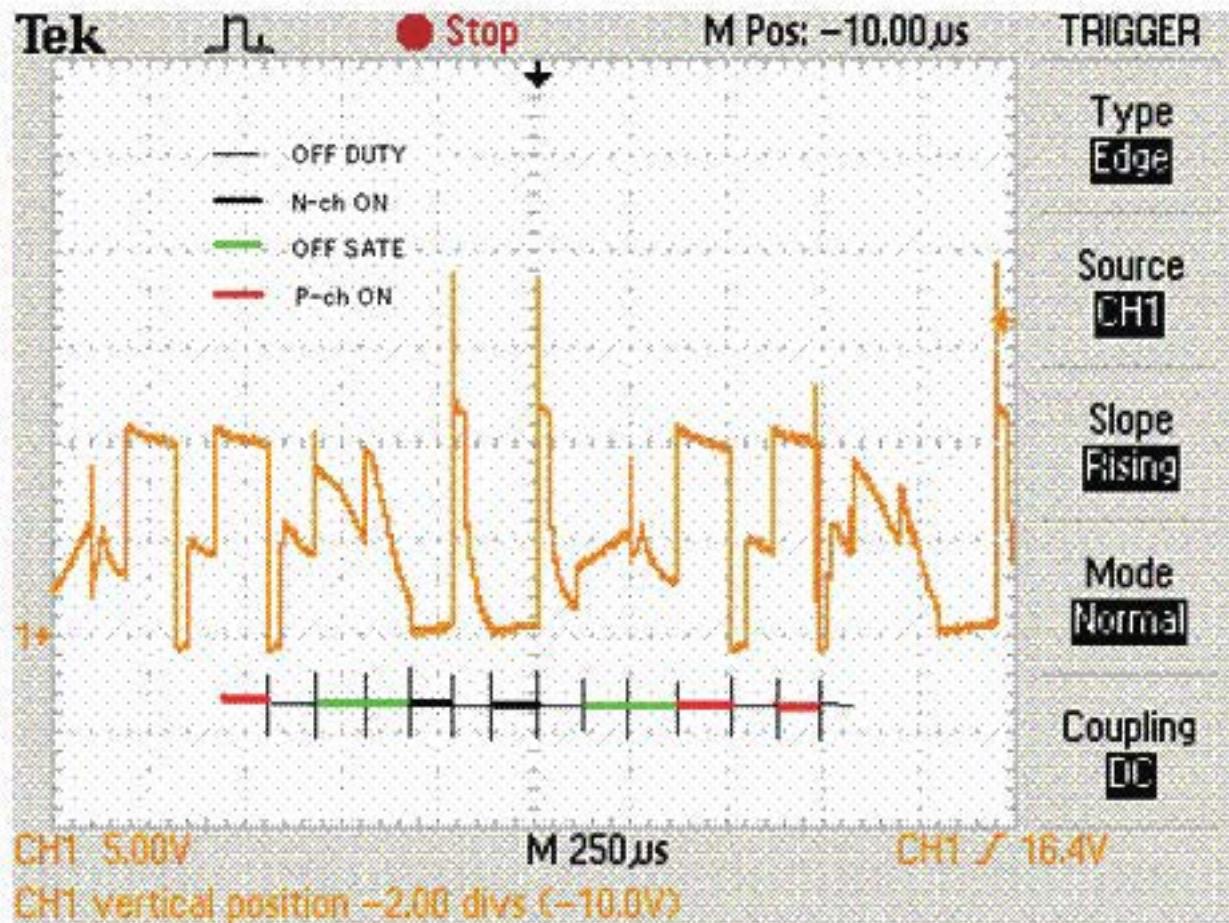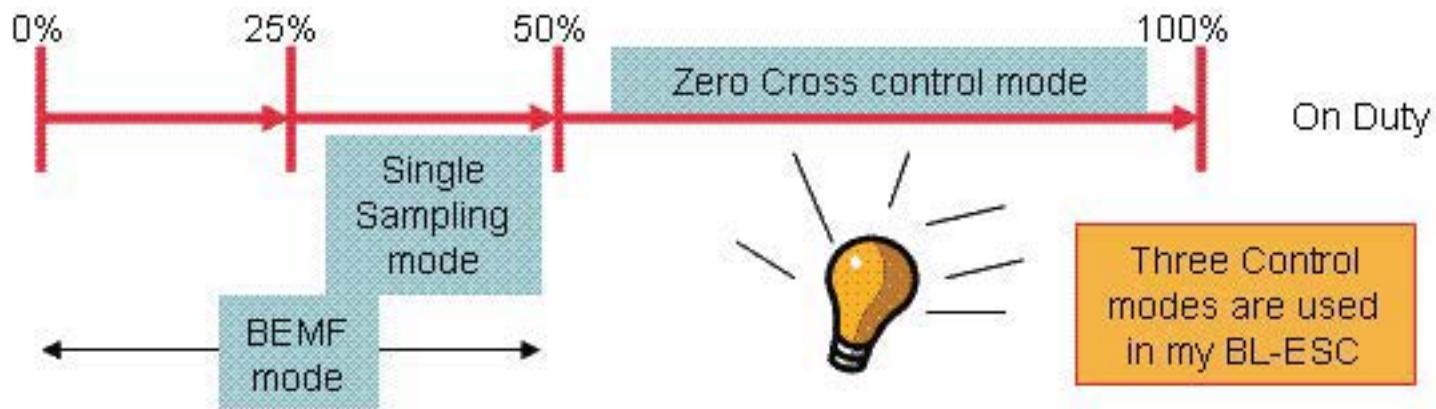Single Sampling mode
can drive safely from
about 10% to near 50%
on-duty




Wave form of Single Sampling mode
by Takao


FMS-FF9

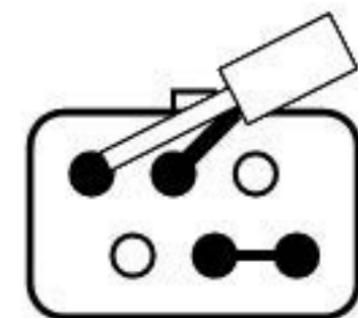


Futaba
FF9 Tx

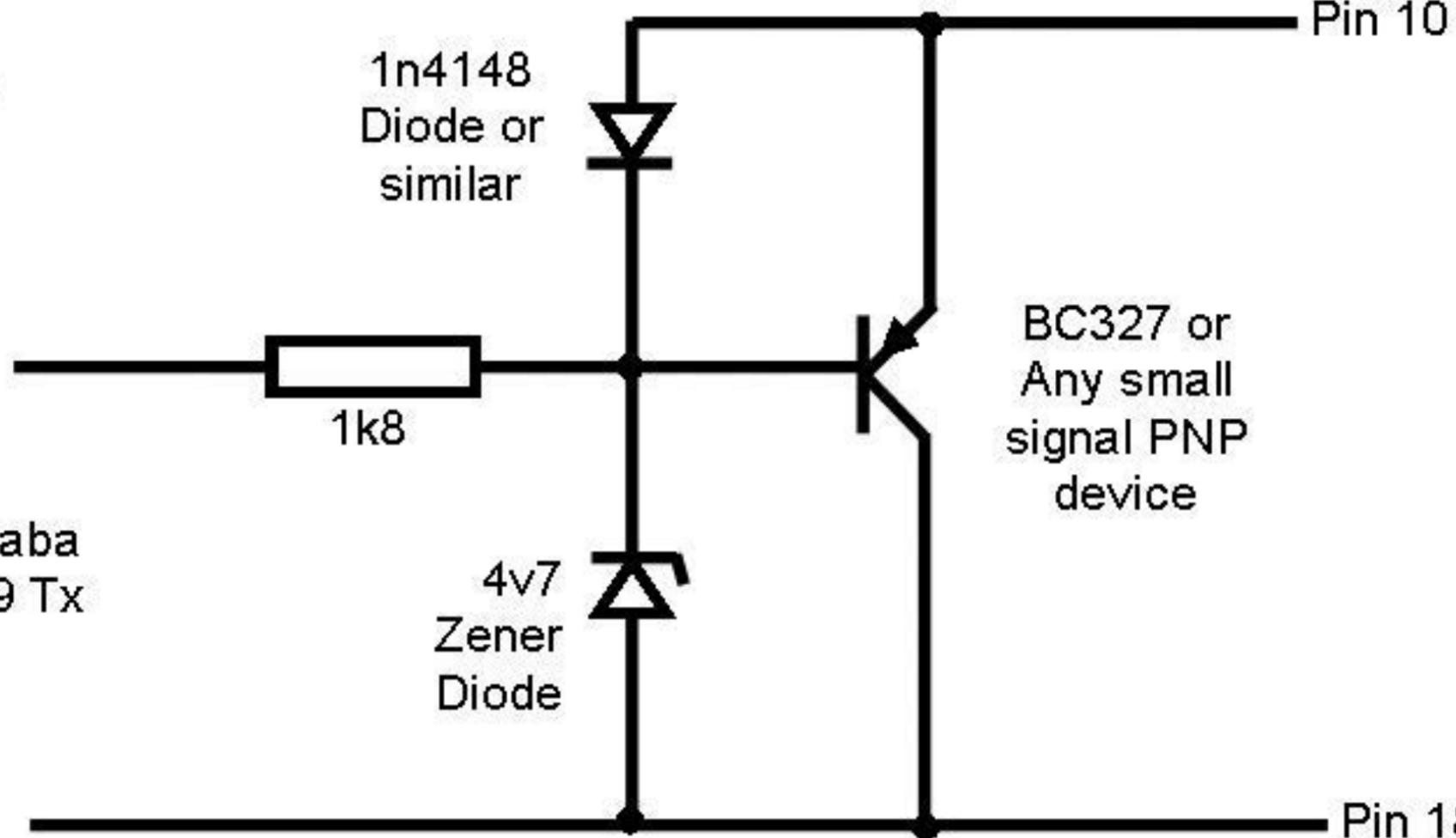



Pin 18

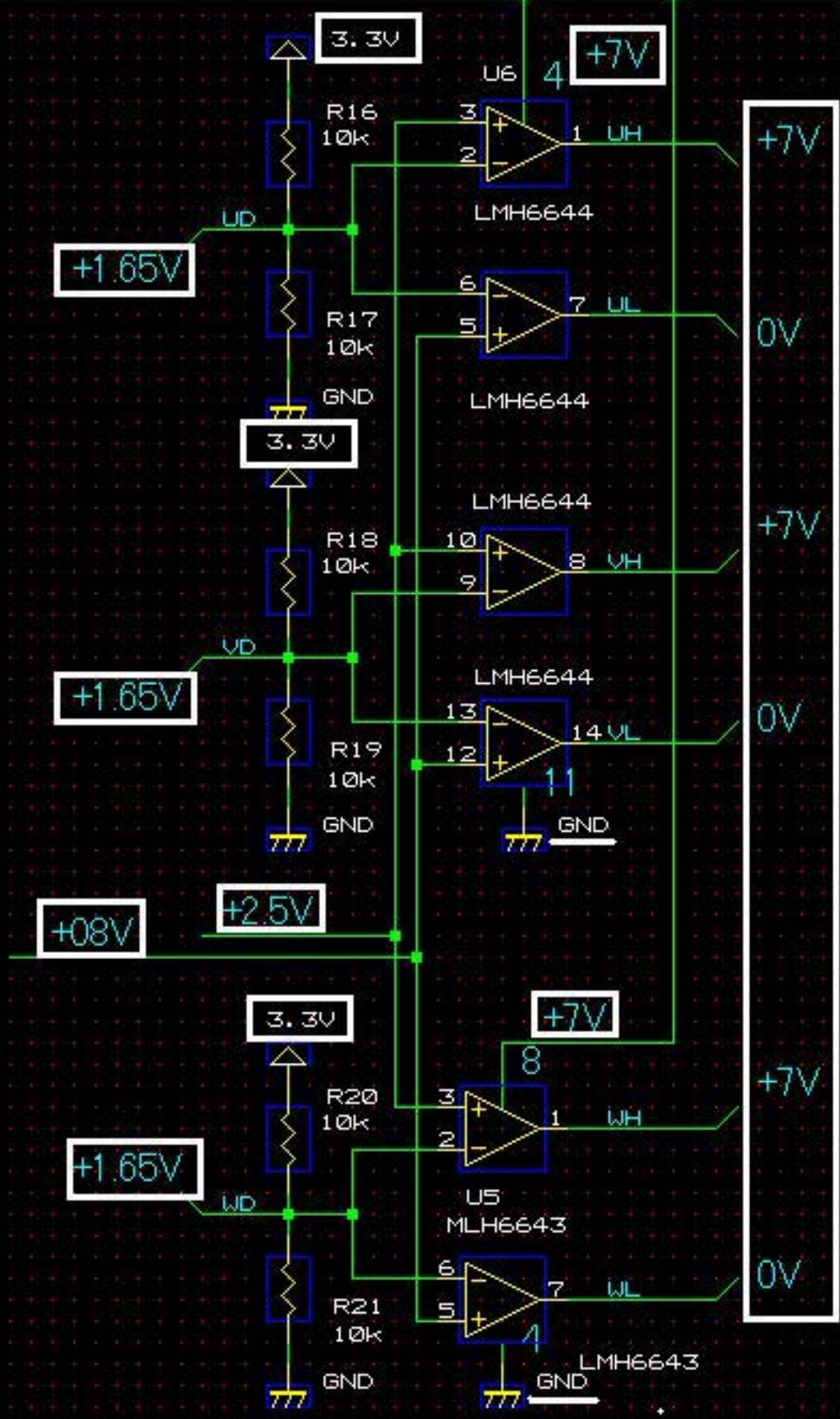

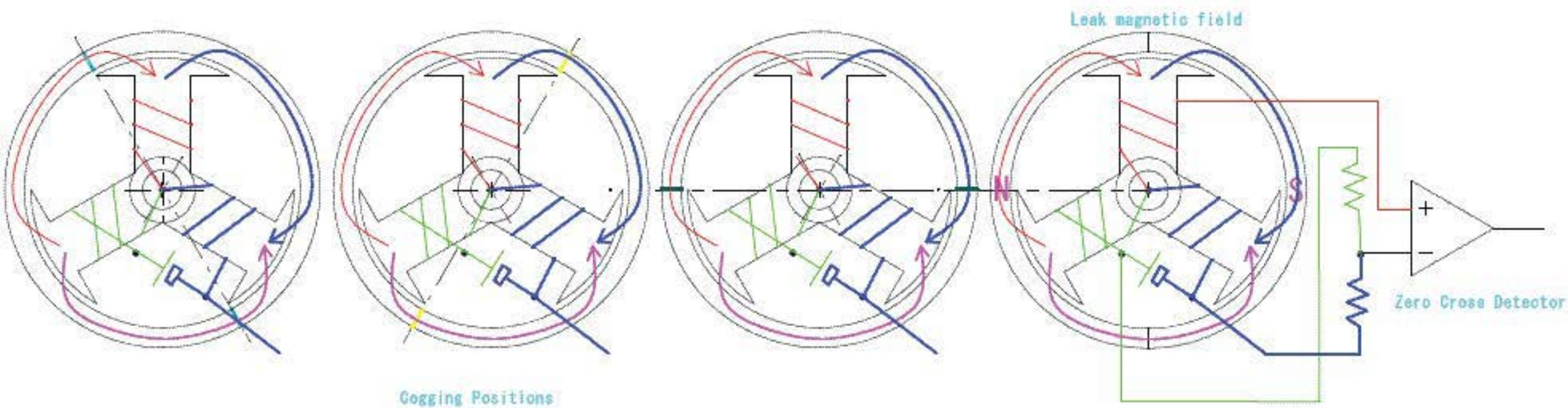
Starting rotar position sensing (shown only one phase impulse drive sensing)



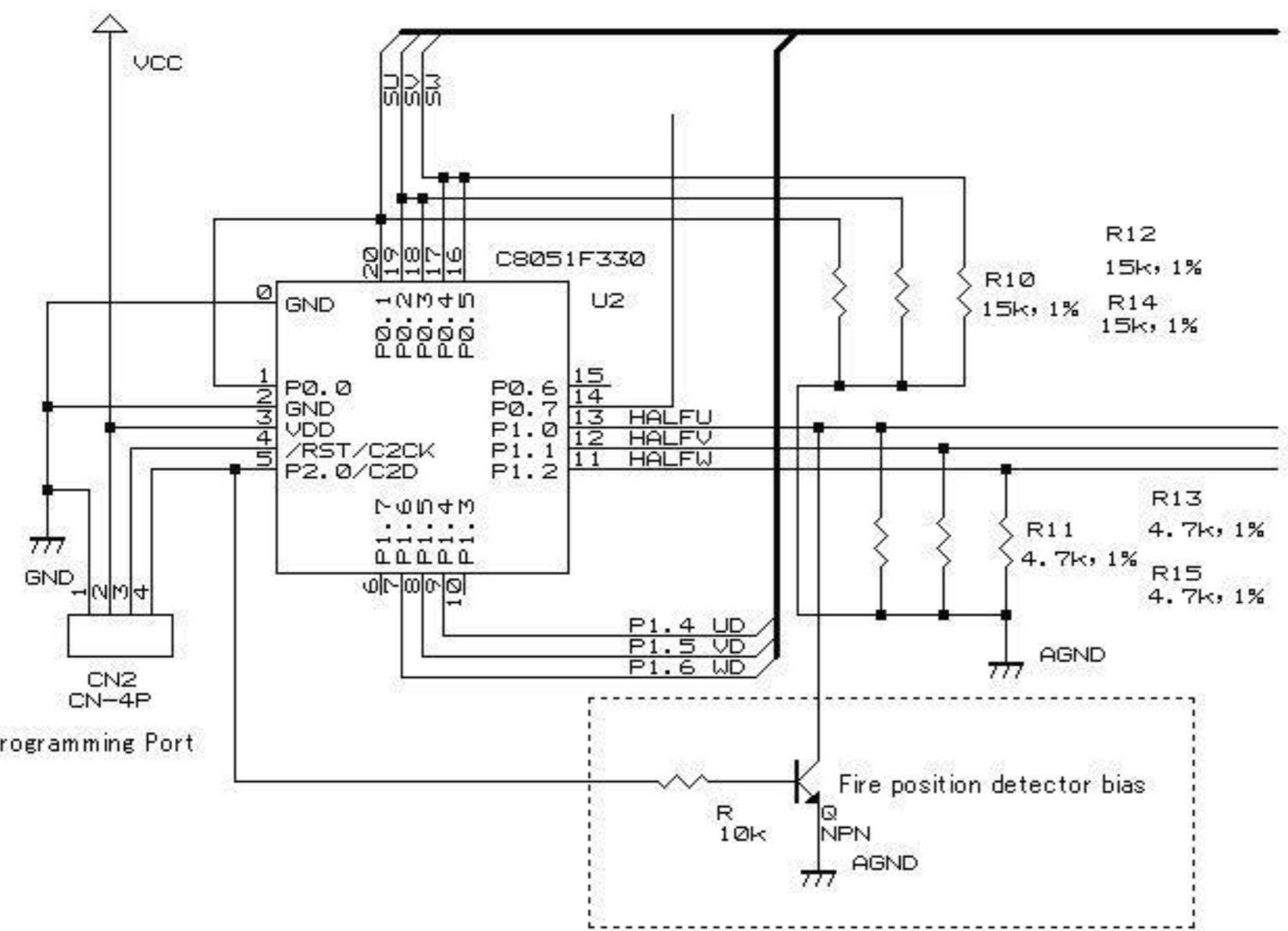


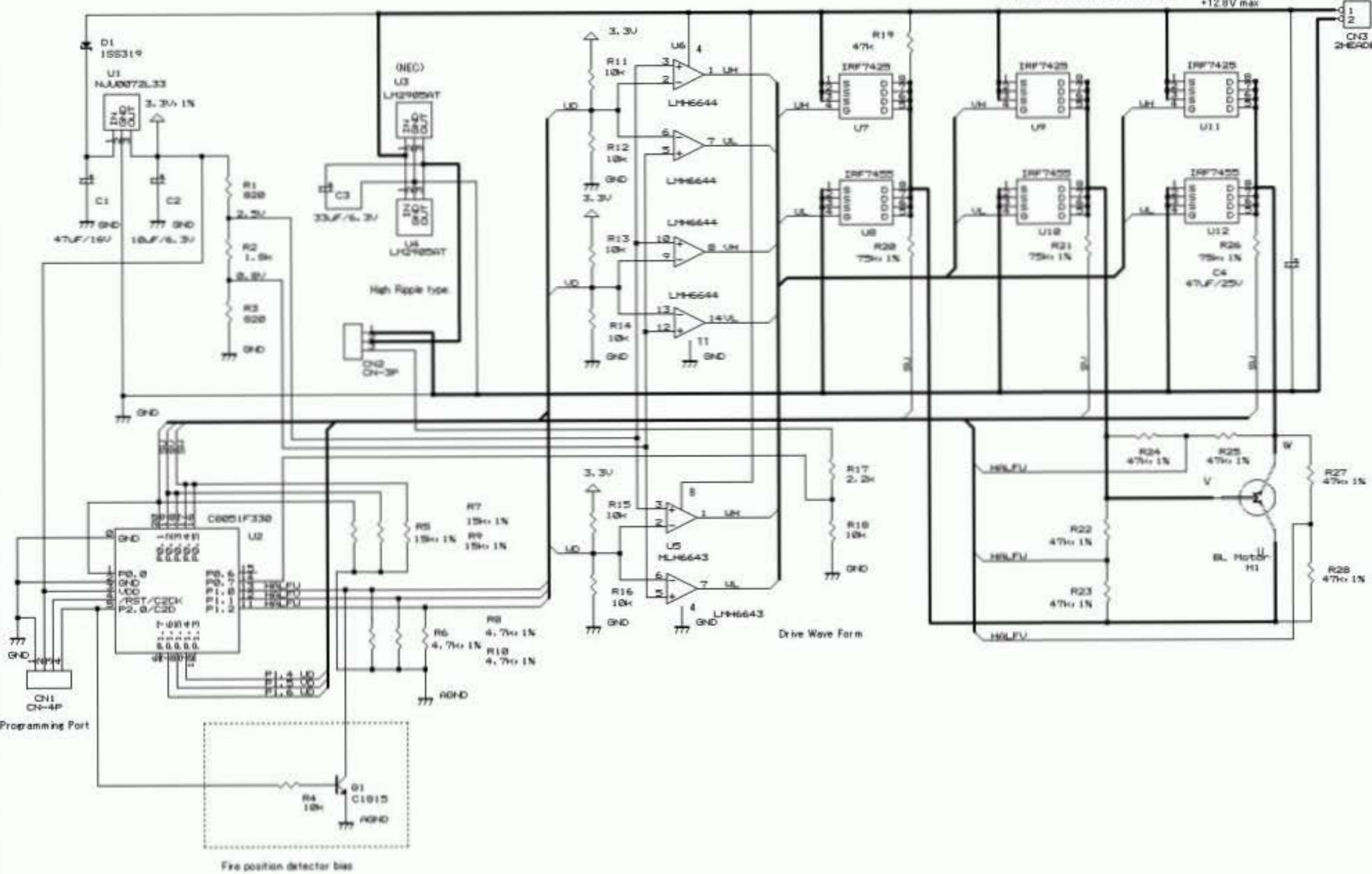


Date	Rev	Designed by	Title	Page
05/08/15	0.5	Takao Shiu Yu	Brushless Sensor-less Electric Speed Controller Schematic	1/1

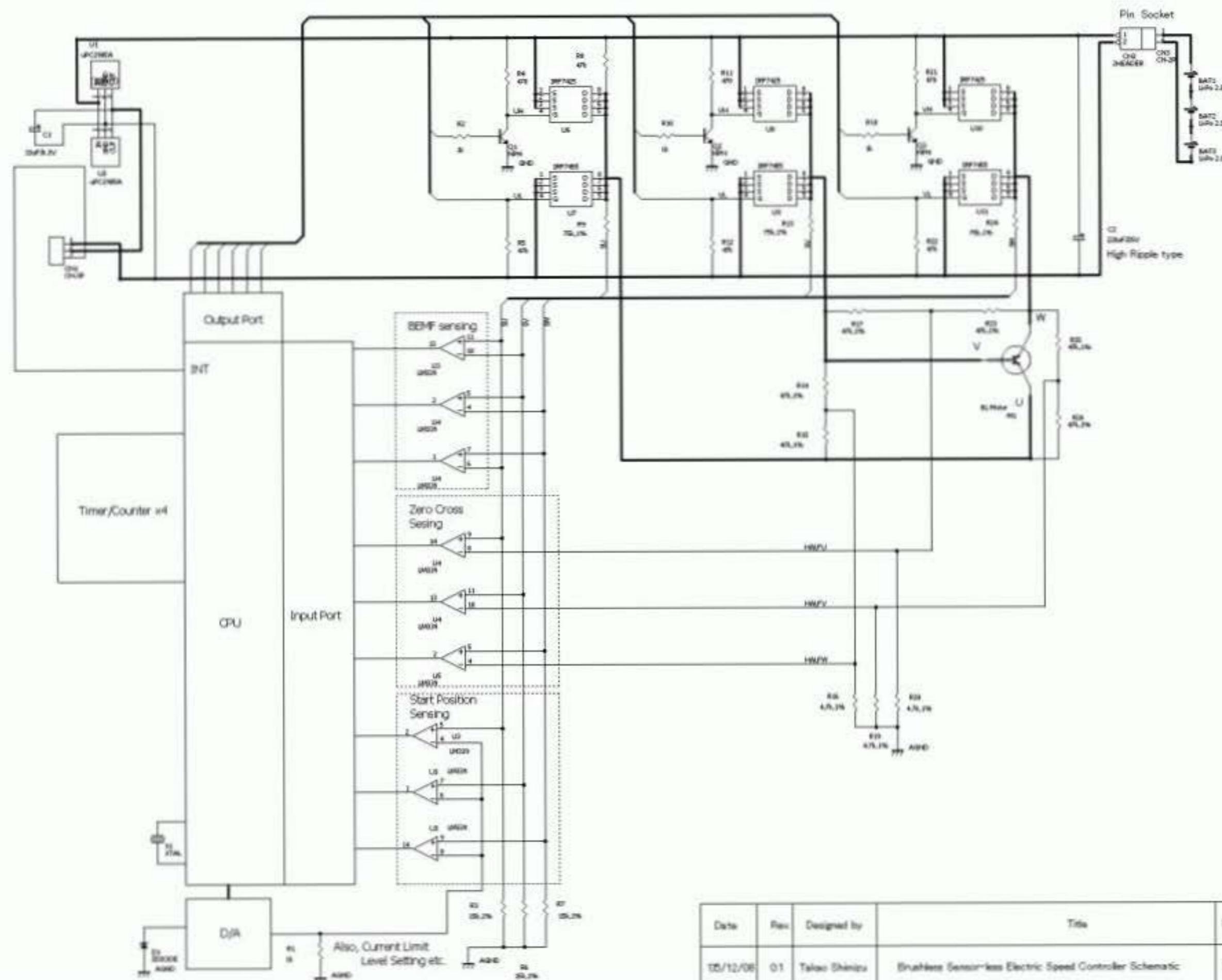


Current Limiter function


Keep the lowest operation voltage

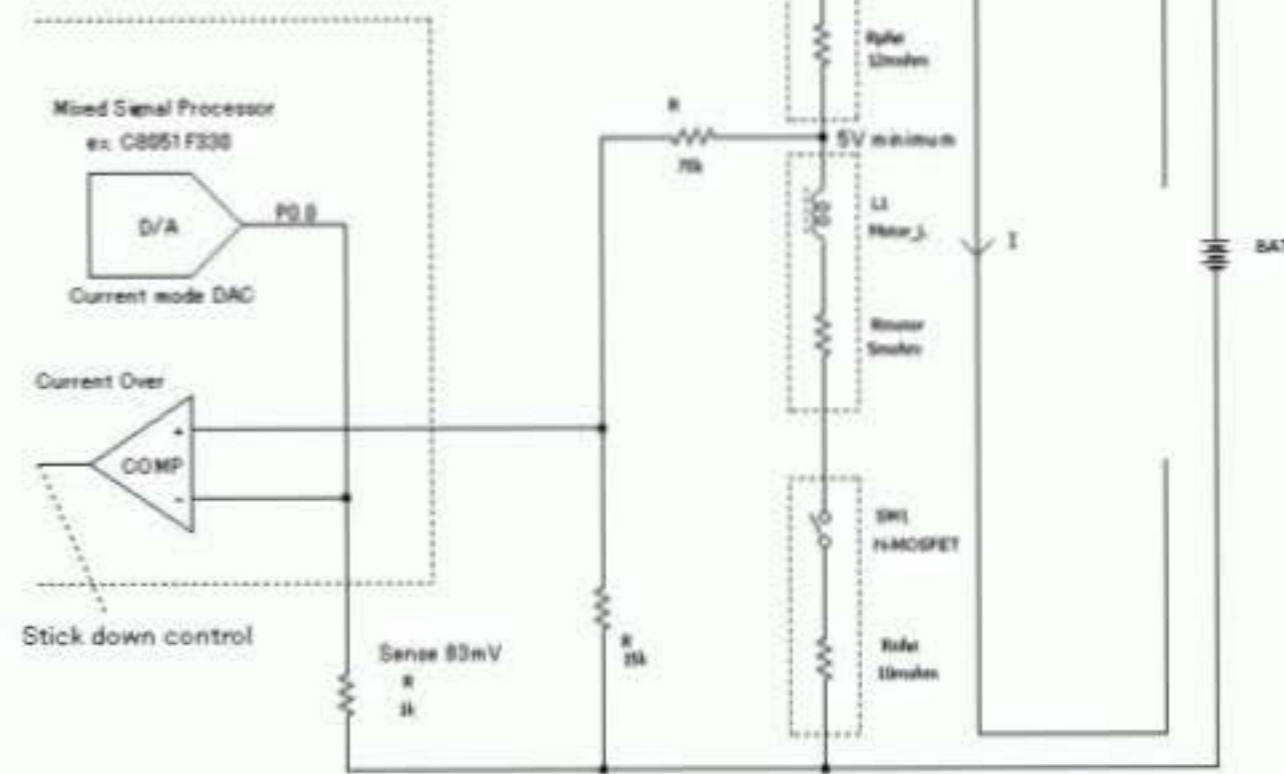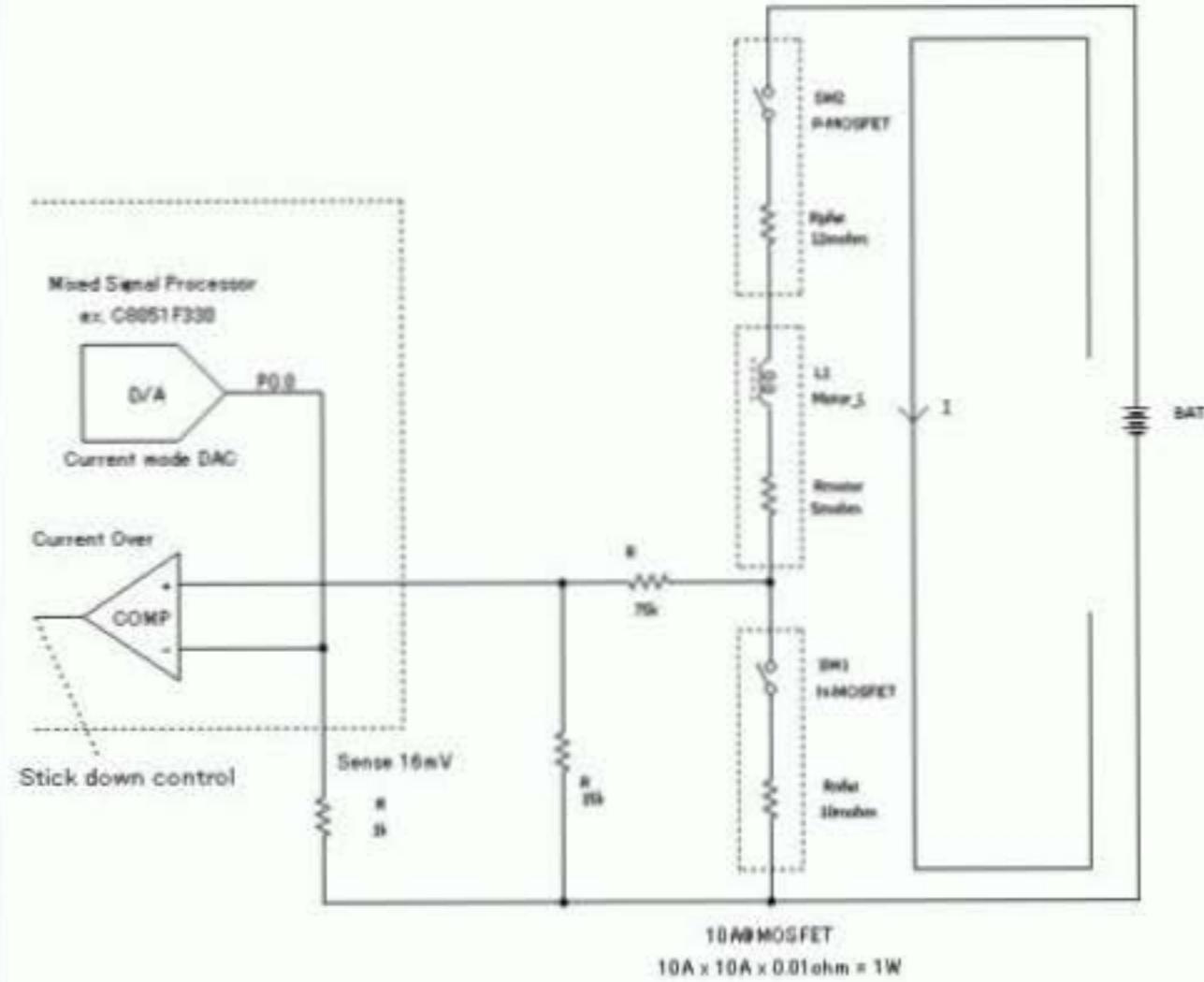

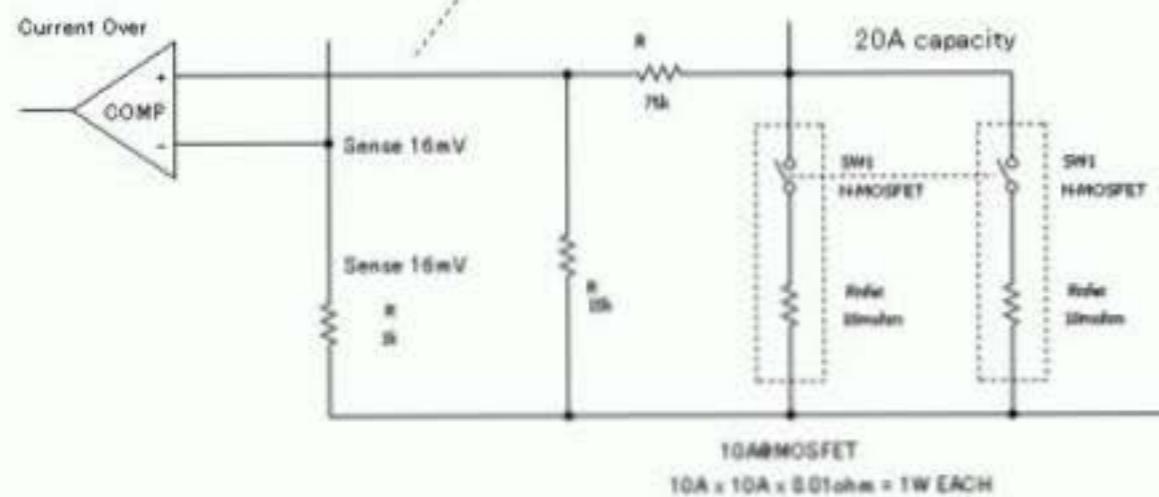
The sensing voltage is same as single MOSFET driver!




Date	Rev	Designed by	Title	Page
10/12/30	2	Takao Shimizu	BL-ESC Protection diagram in MPU	1/1

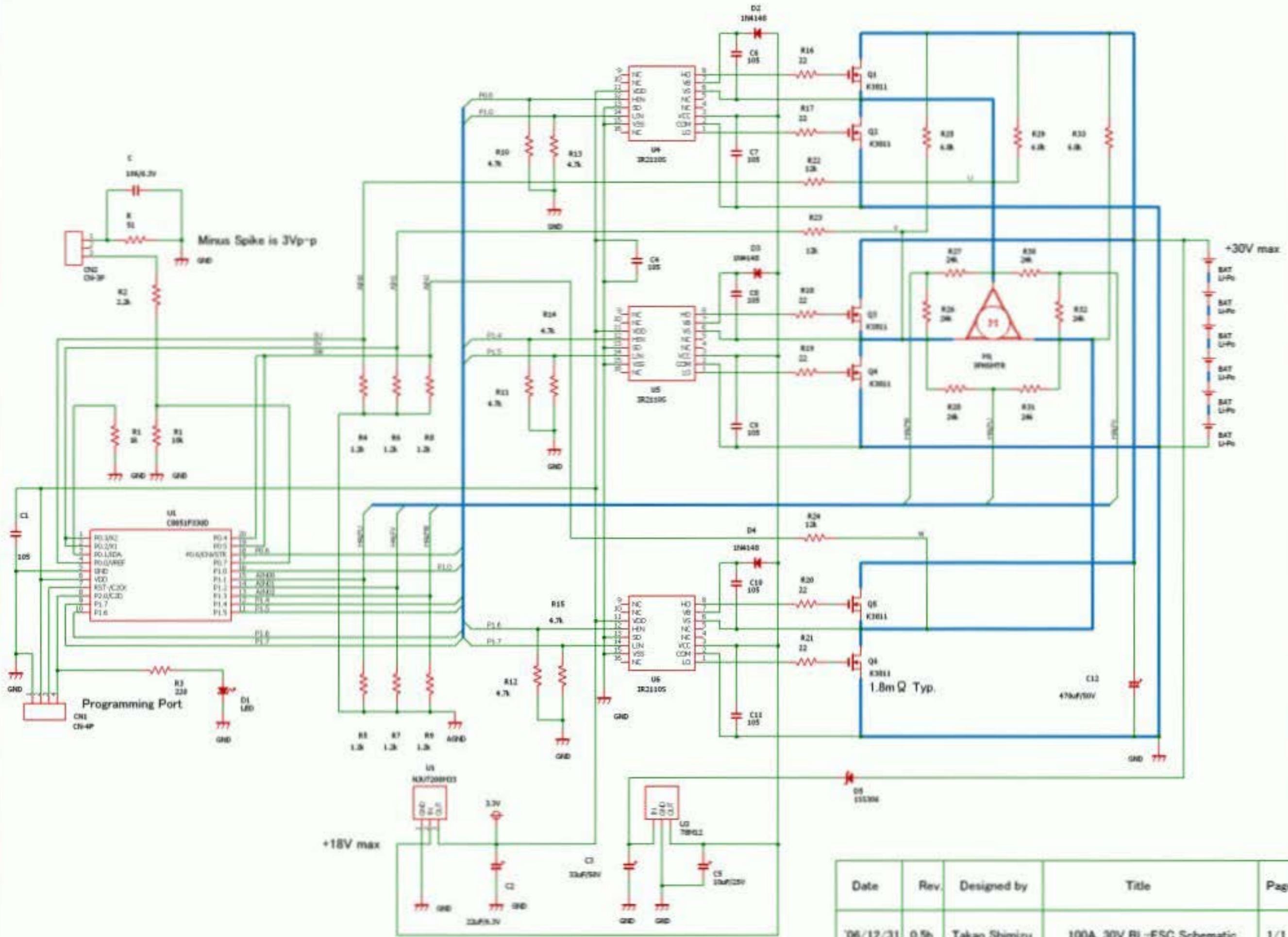



Date	Rev.	Designed by	Title	Page
106/12/31	0.5b	Takao Shimizu	100A, 30V BL-ESC Schematic	1/1

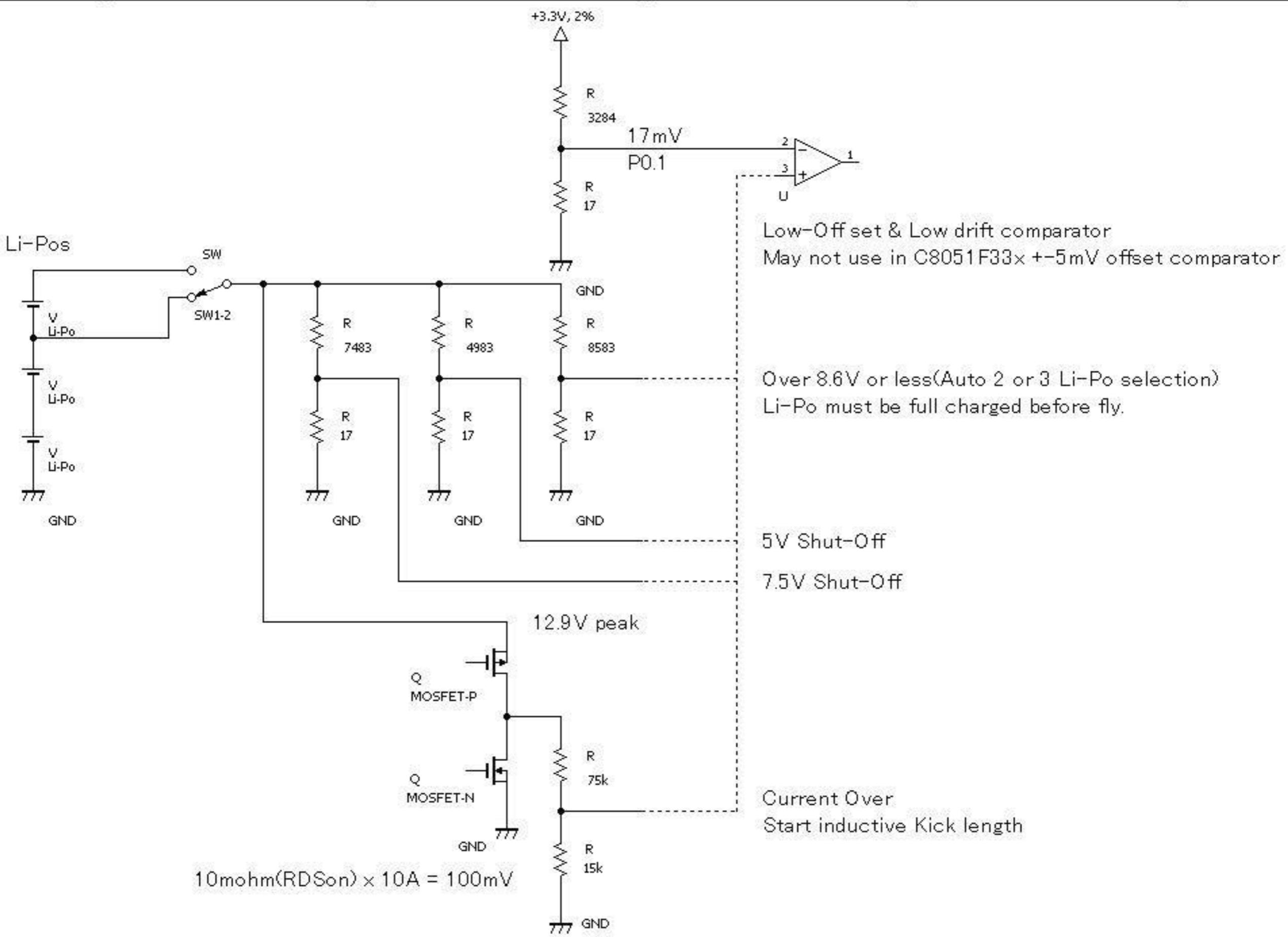

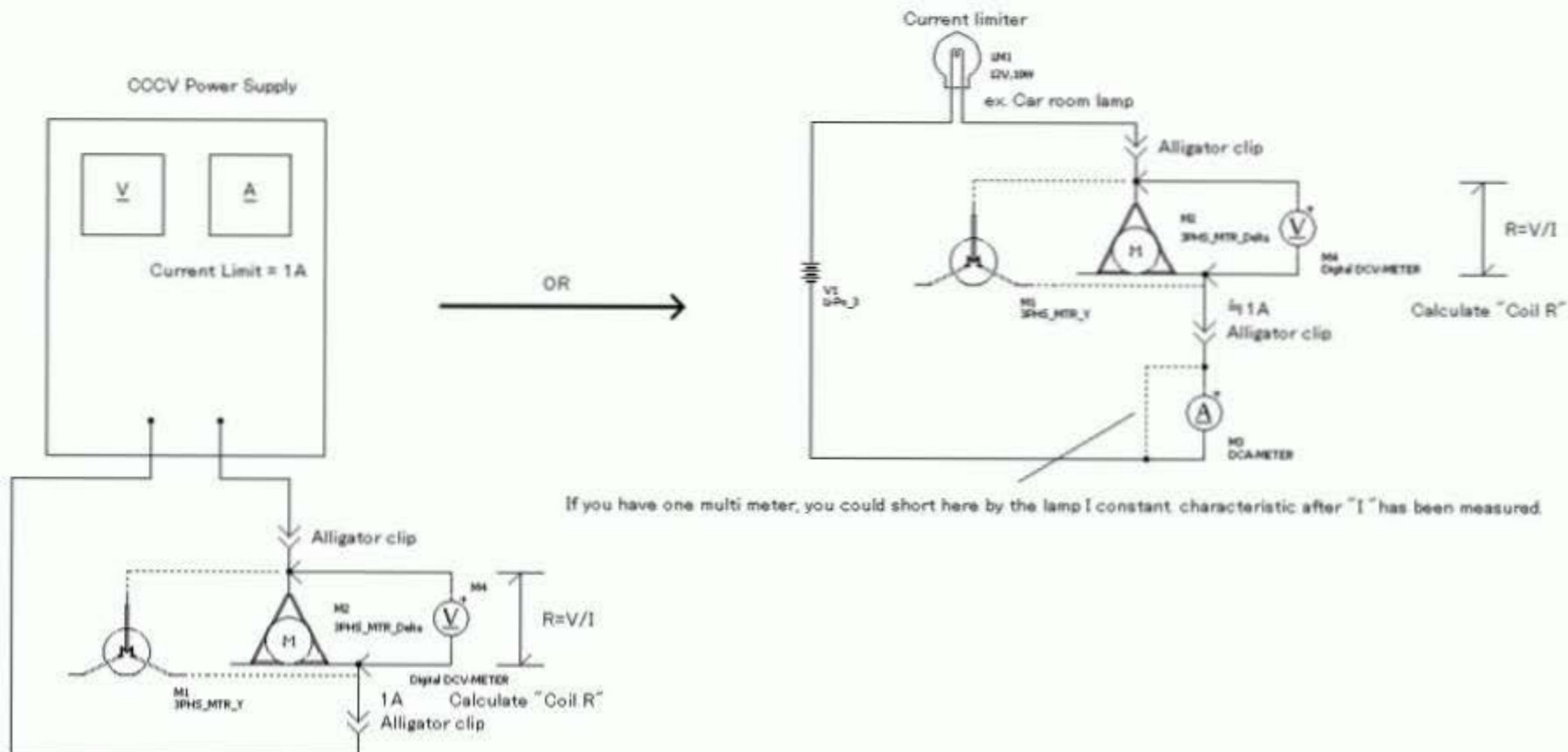


Date	Rev.	Designed by	Title	Page
06/01/10	0.1	Takao Shimizu	Measuring method of motor coil resistance	1/1


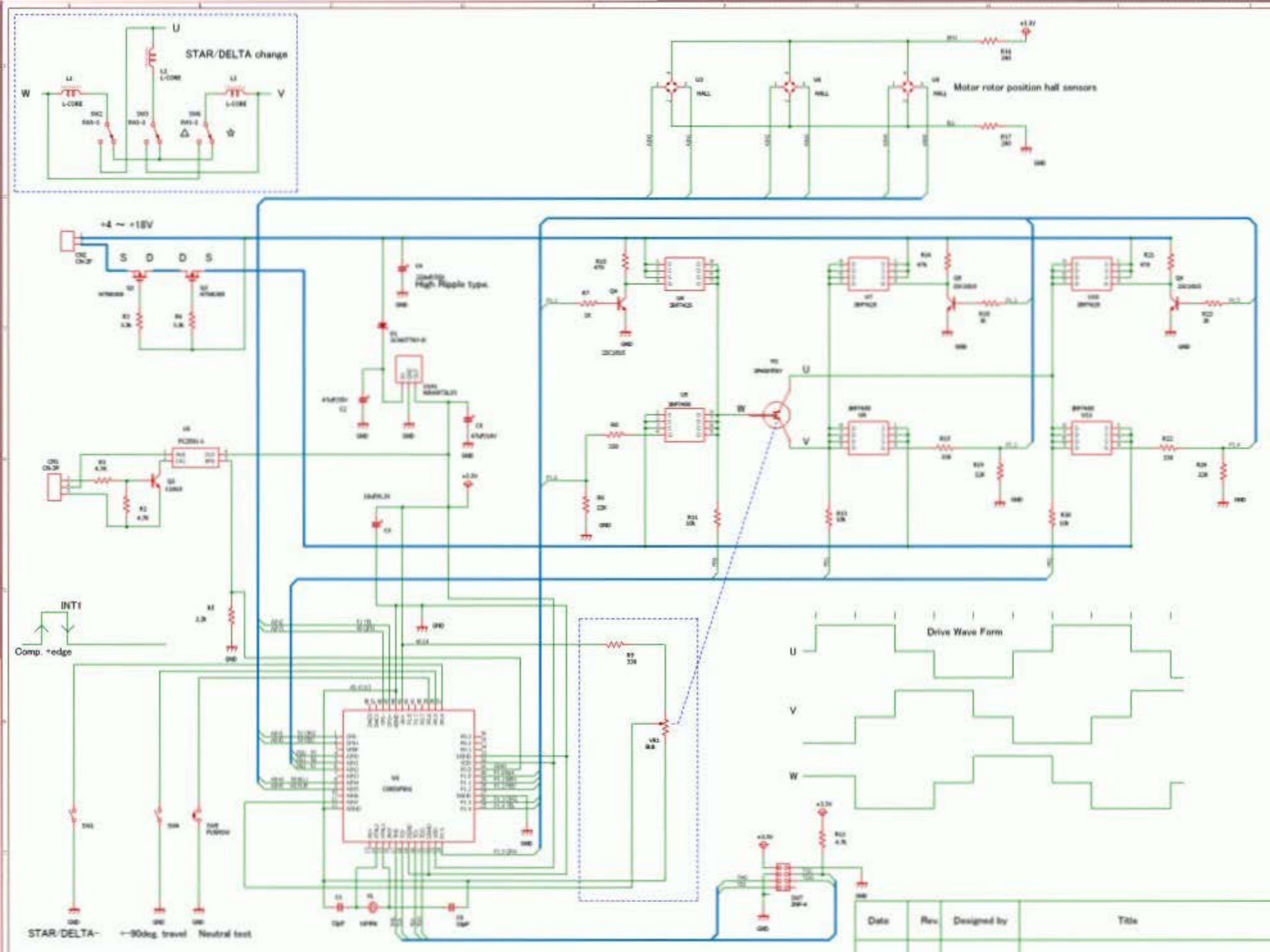


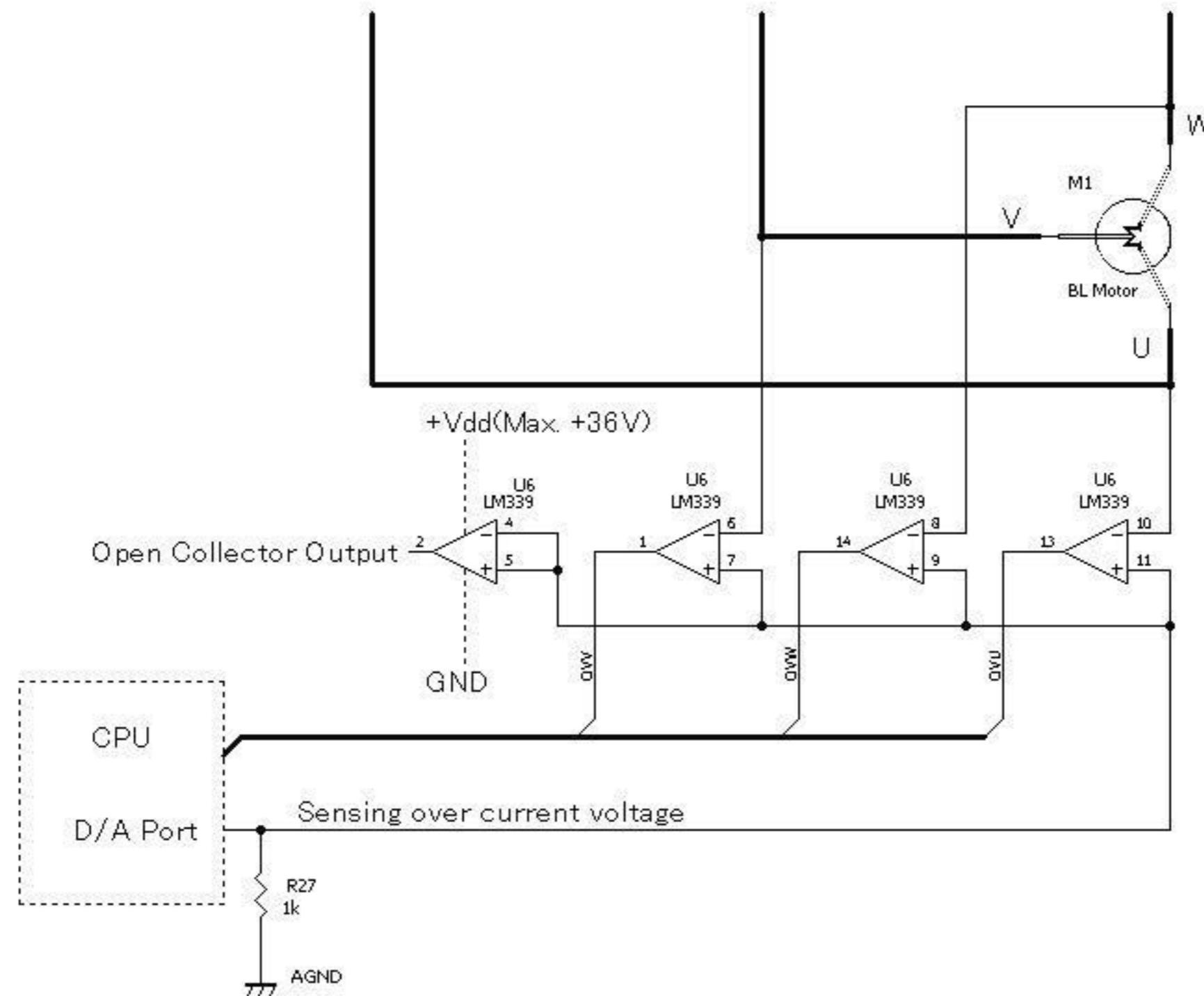

Date	Rev.	Designed by	Title	Page
'05/01/25	0.1	Takao Shimizu	BL-Motor over current sensing schematic	1/1

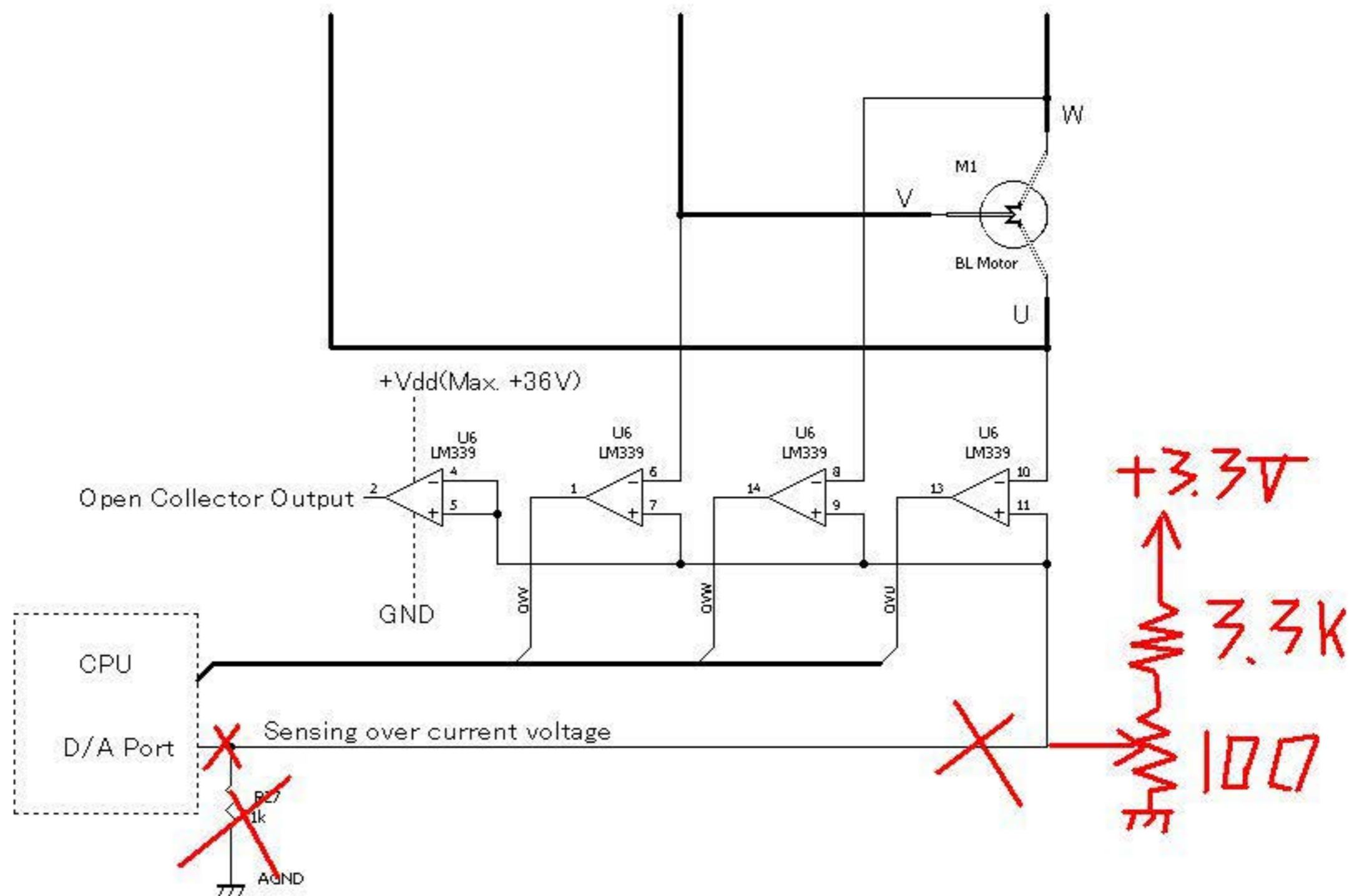



Date	Rev.	Designed by	Title	Page
'05/01/25	0.1	Takao Shimizu	BL-Motor over current sensing schematic	1/1

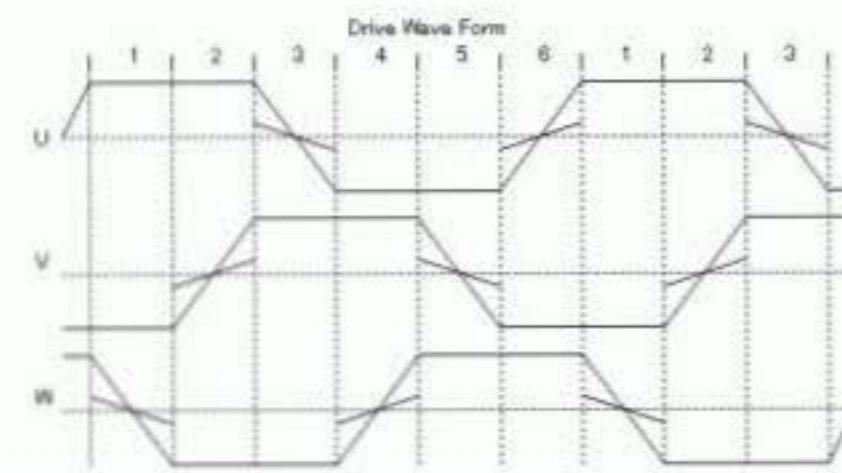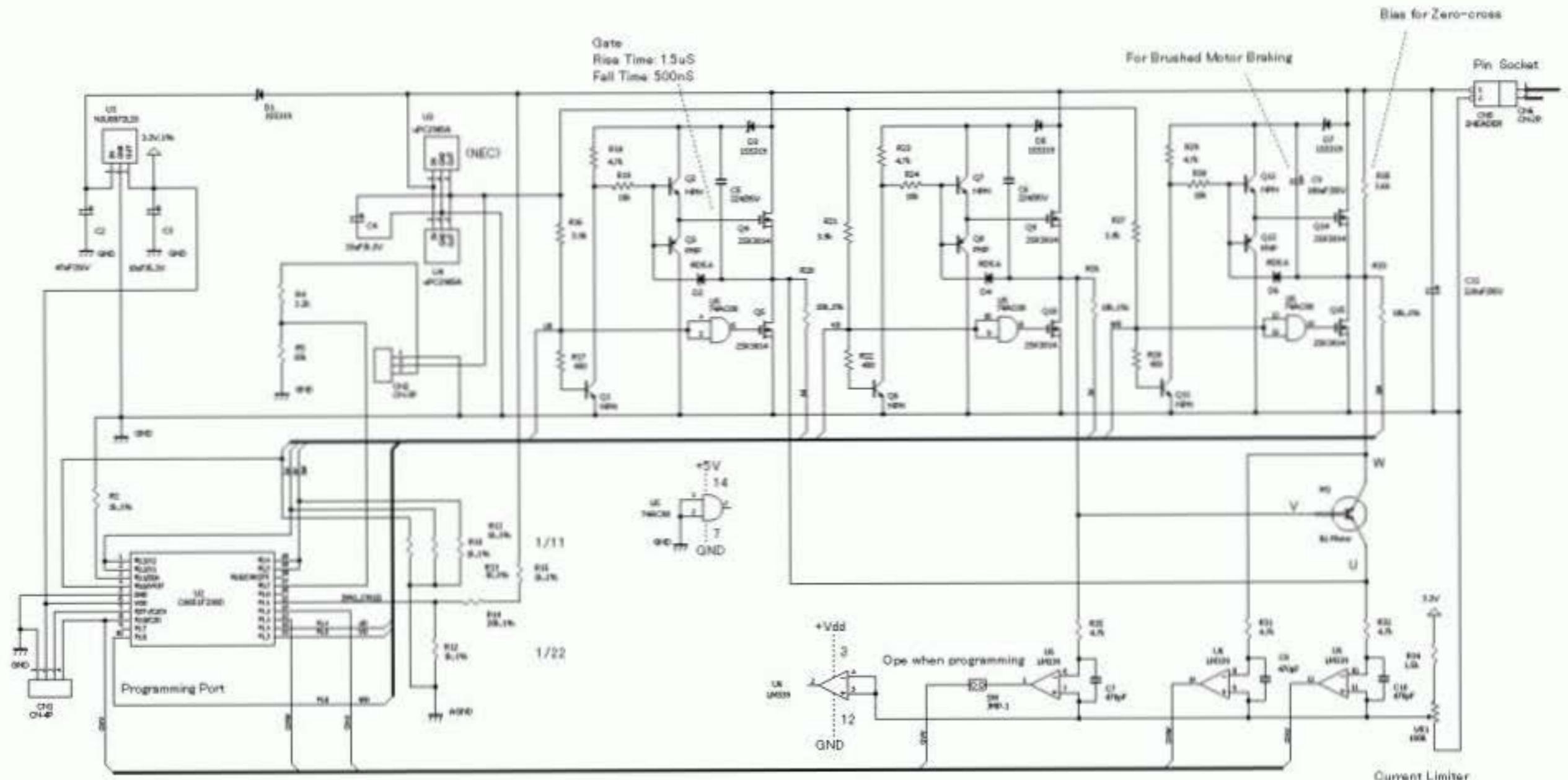


Each Cell Voltage Monitor

Date	Rev	Designed by	Title	Page
05/01/14	01	Takao Shimizu	Brushless Sensor-less Electric Speed Controller Schematic	1/1

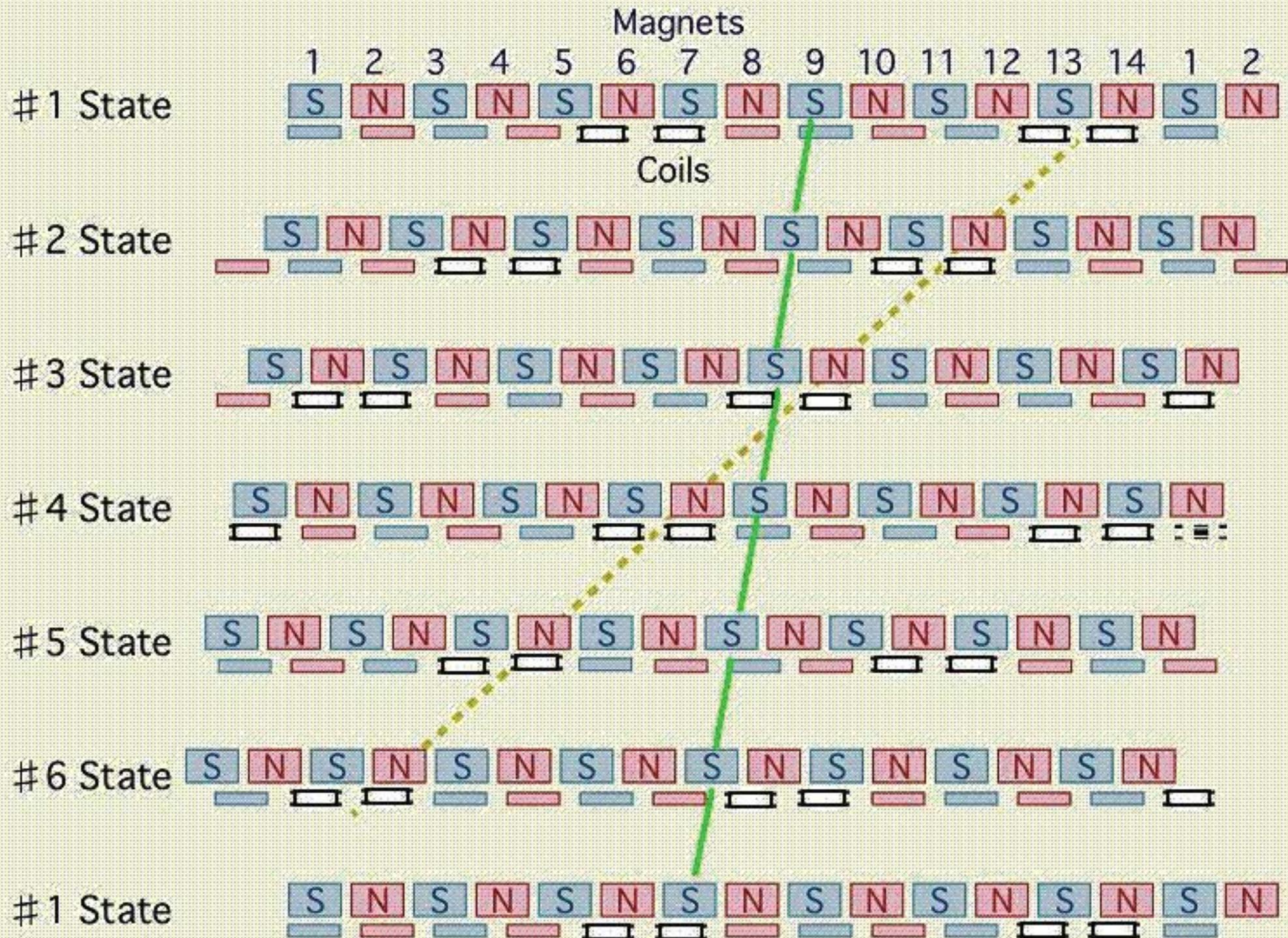

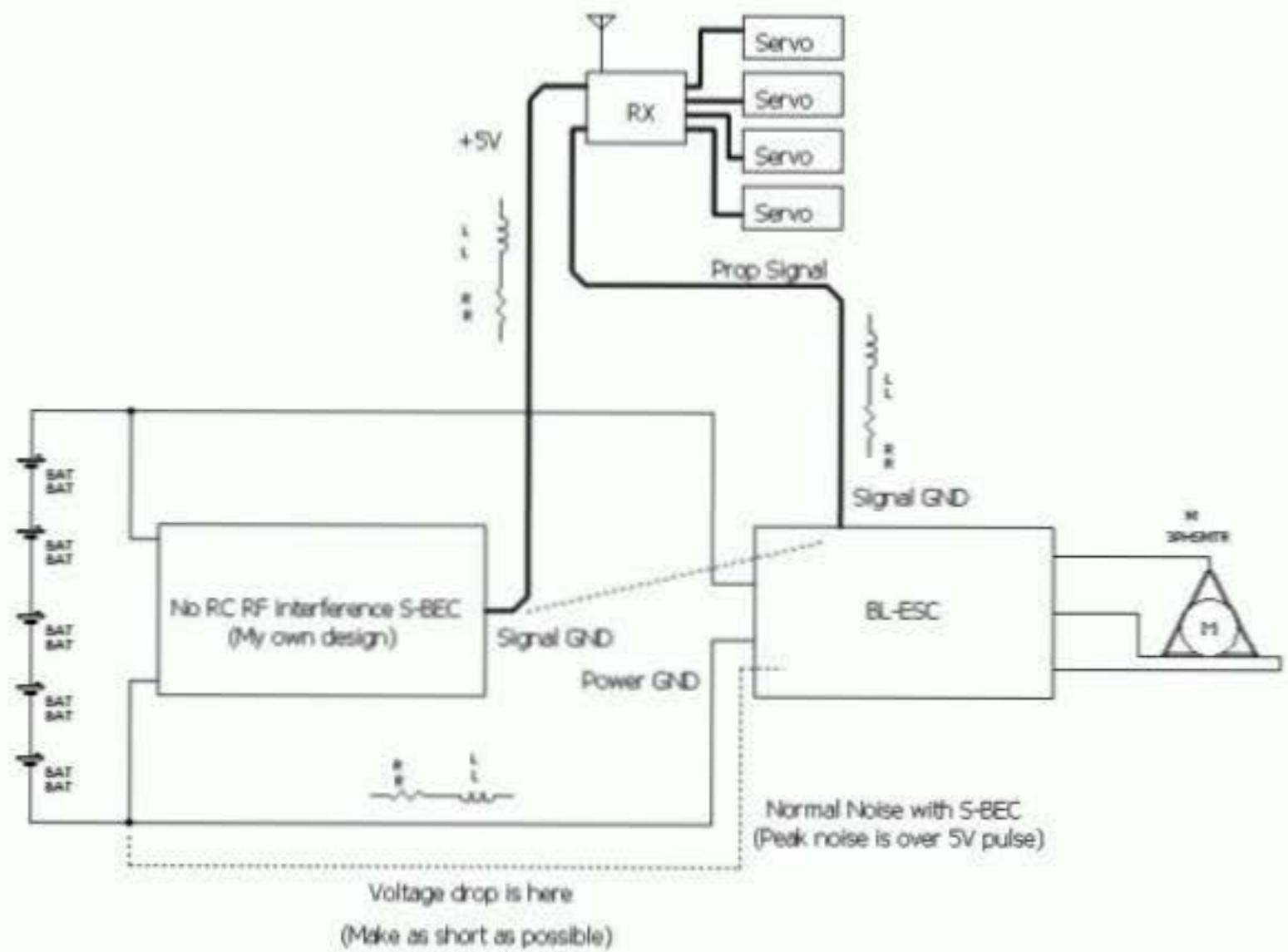

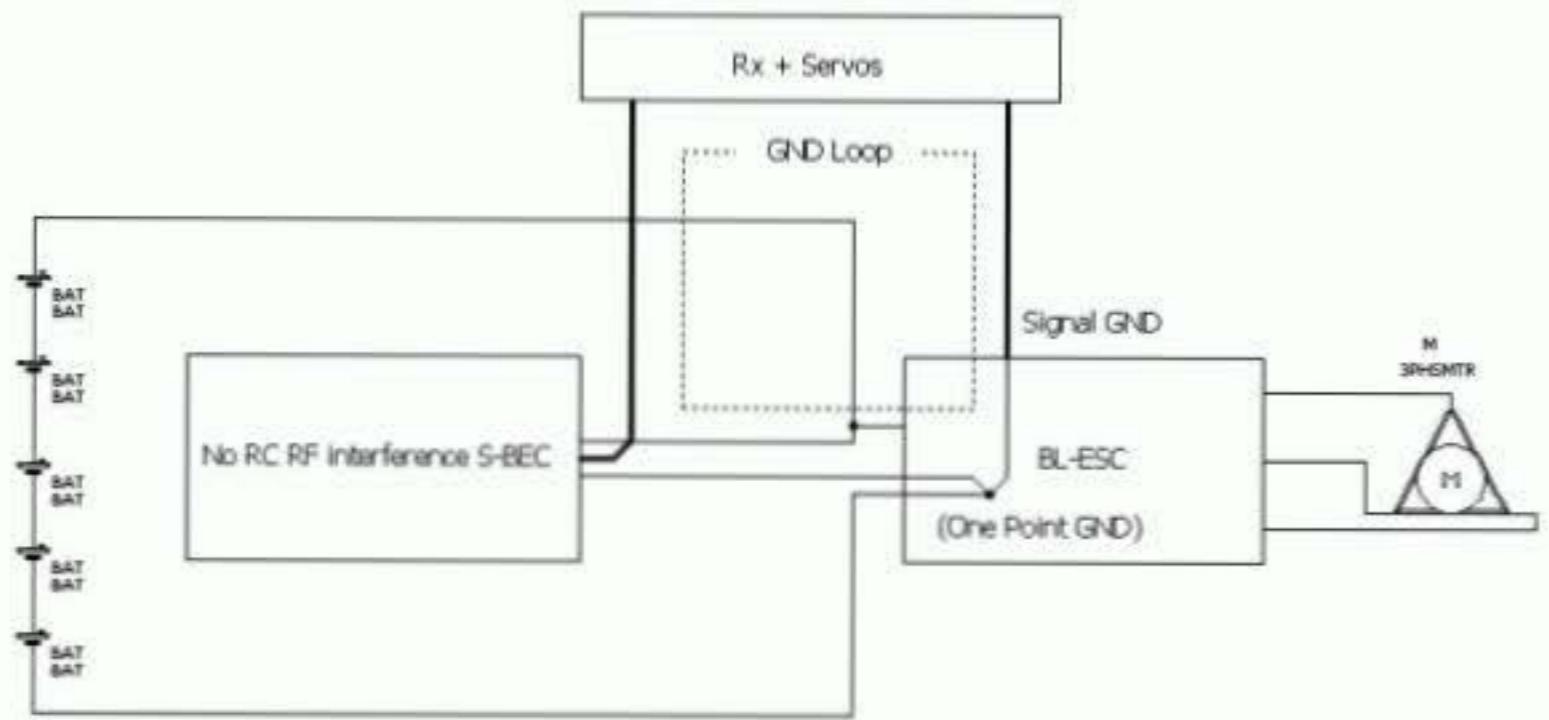S-BEC connection Problem
(System can not start)



The S-BEC power line GND loop problem

Date	Rev	Designed by	Title	Page
Feb 20, '06	0.1	Takao Shimizu	S-BEC Connection Problem	1/1


Tek


M


Stop


M Pos: 200.0 μ s

CH3

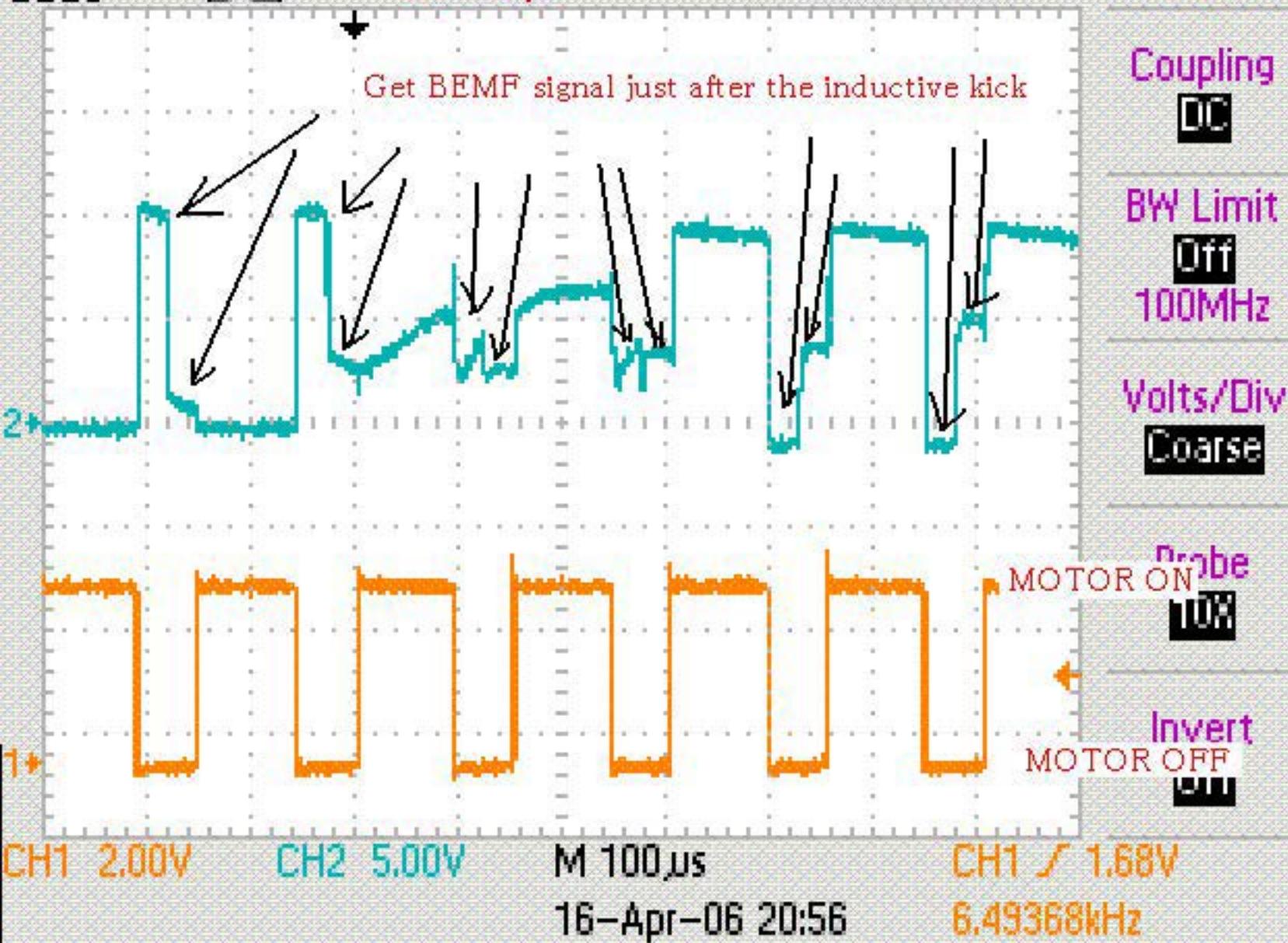


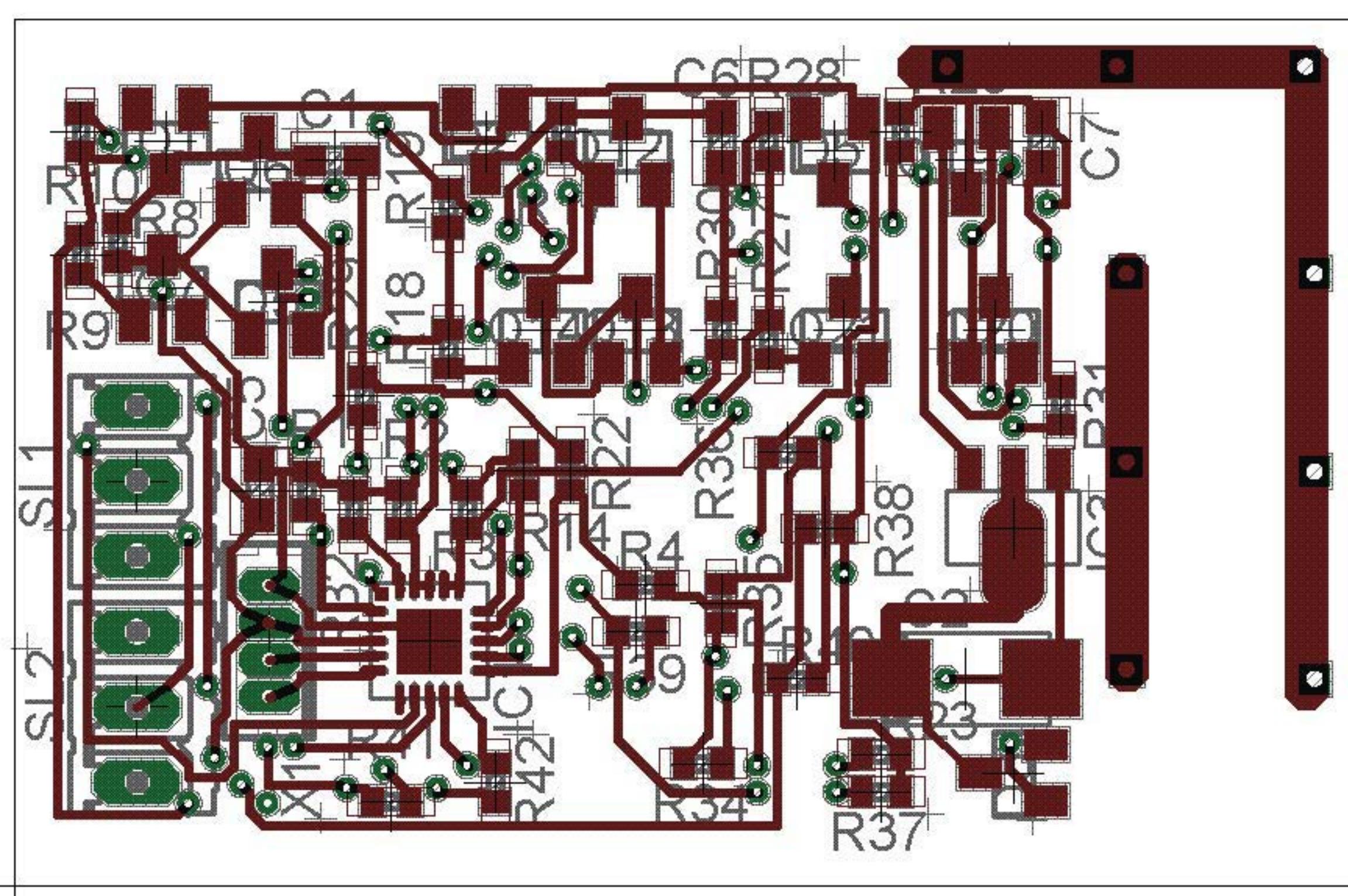

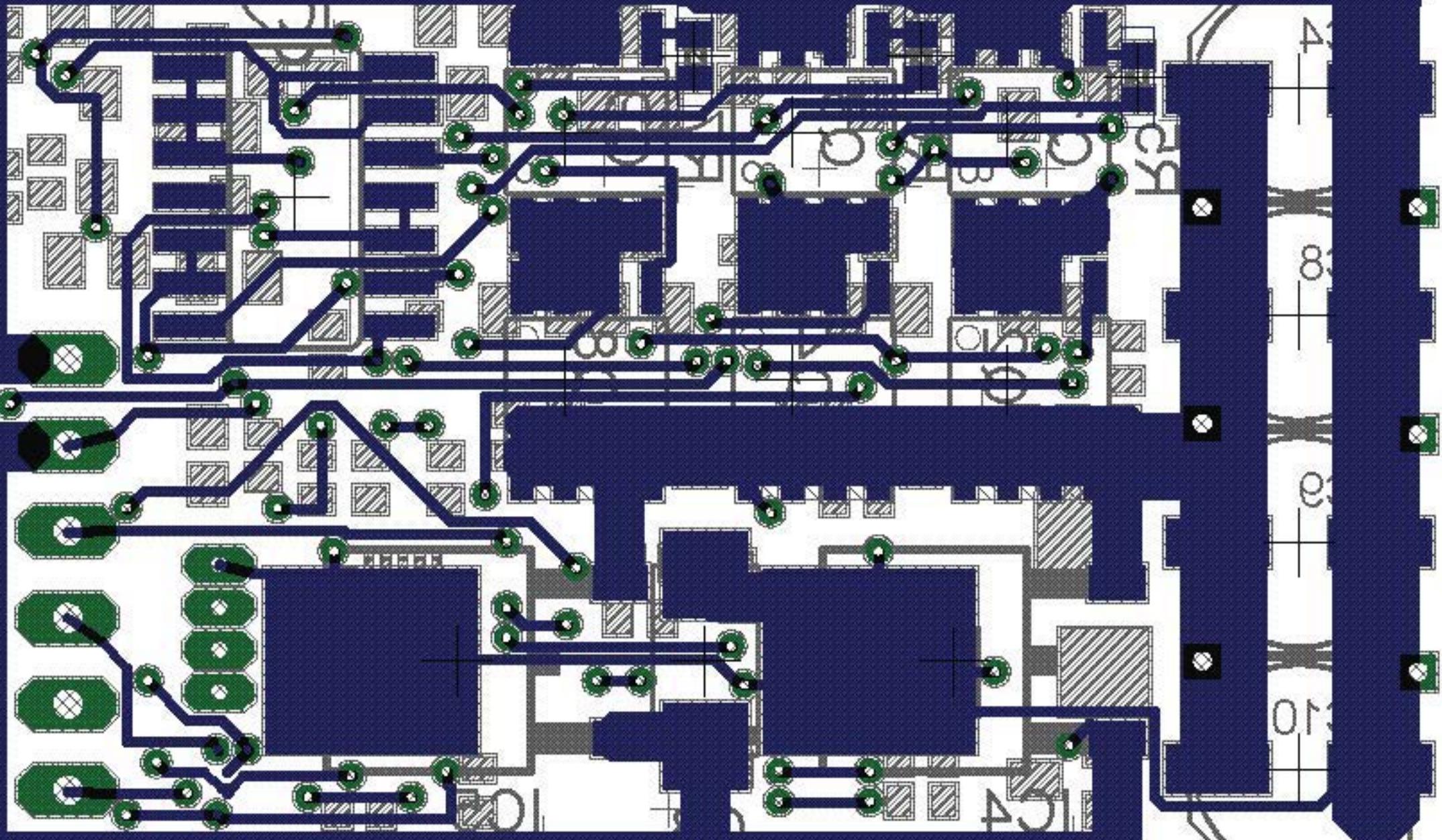

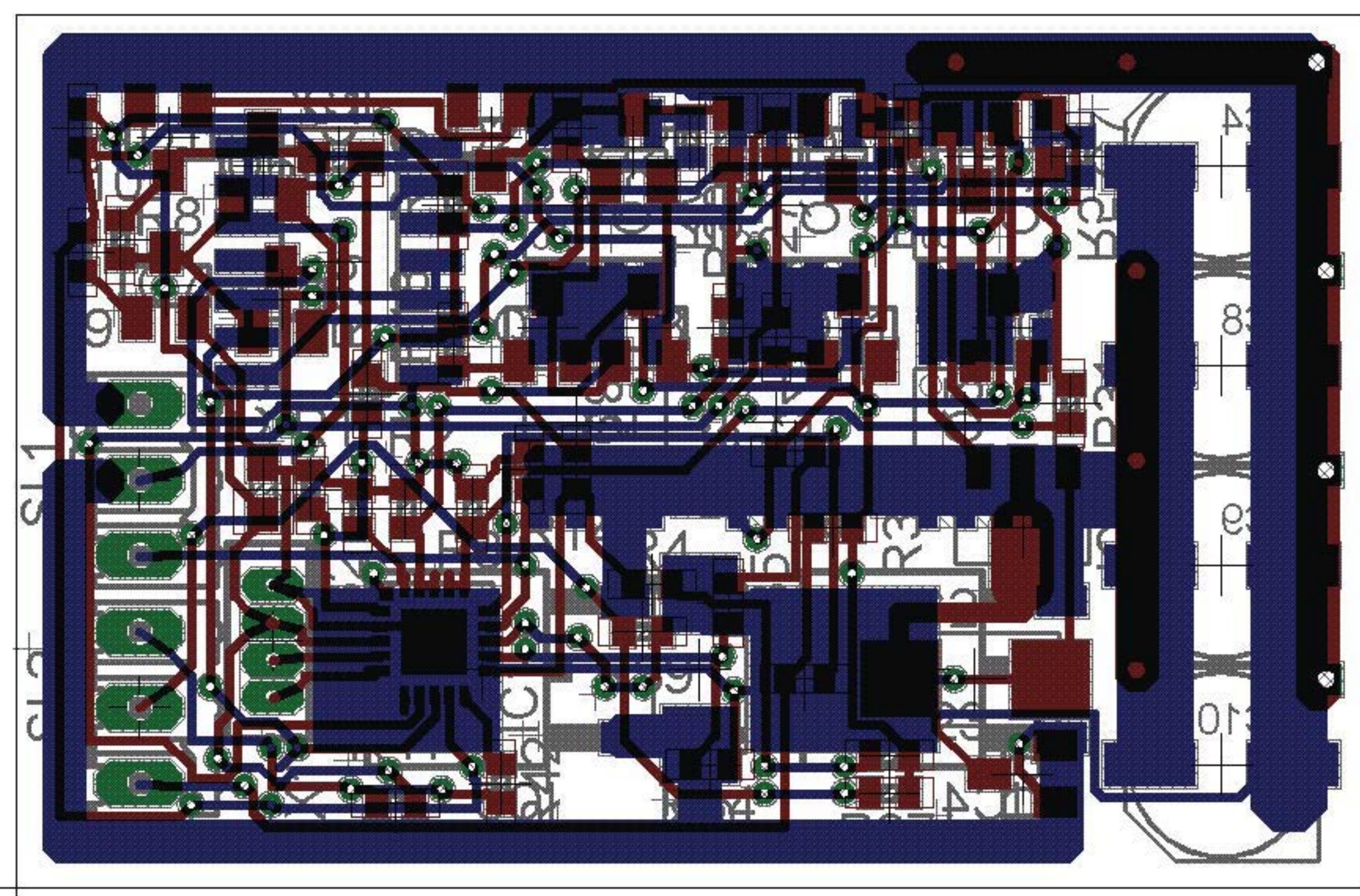


Zero Cross Control

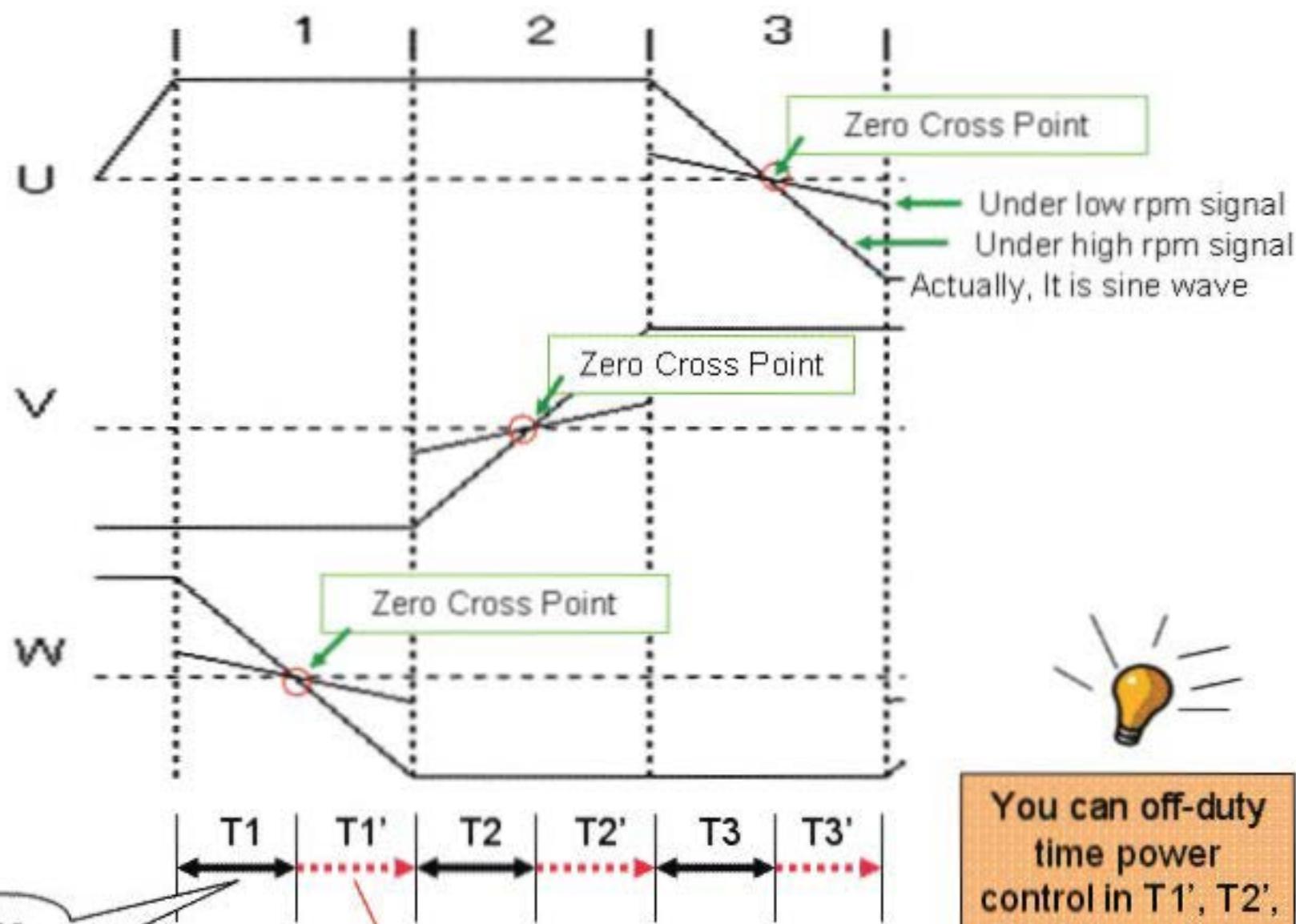


You can off-duty time power control in T1', T2', T3' (It is as timing advance)

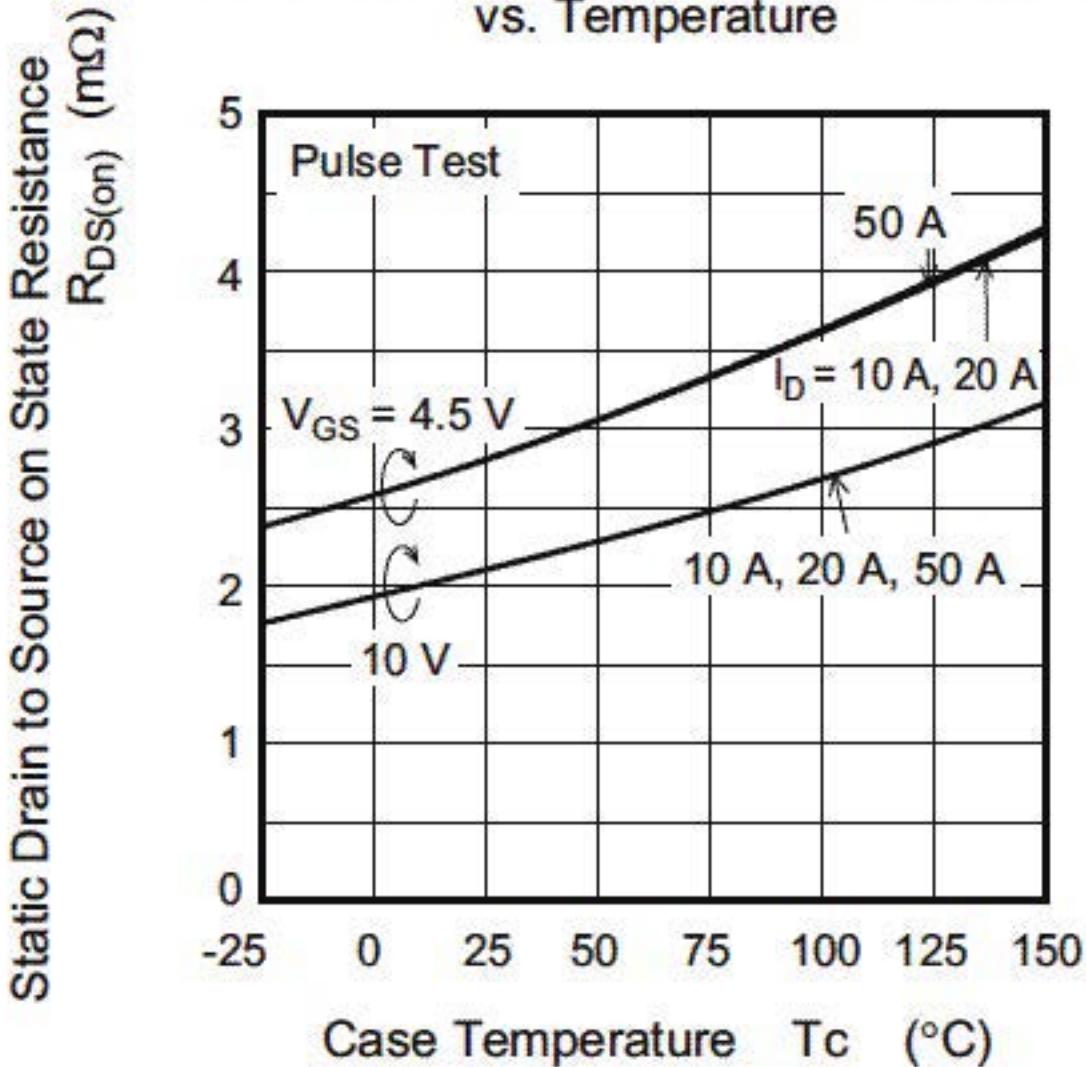Static Drain to Source on State Resistance vs. Temperature





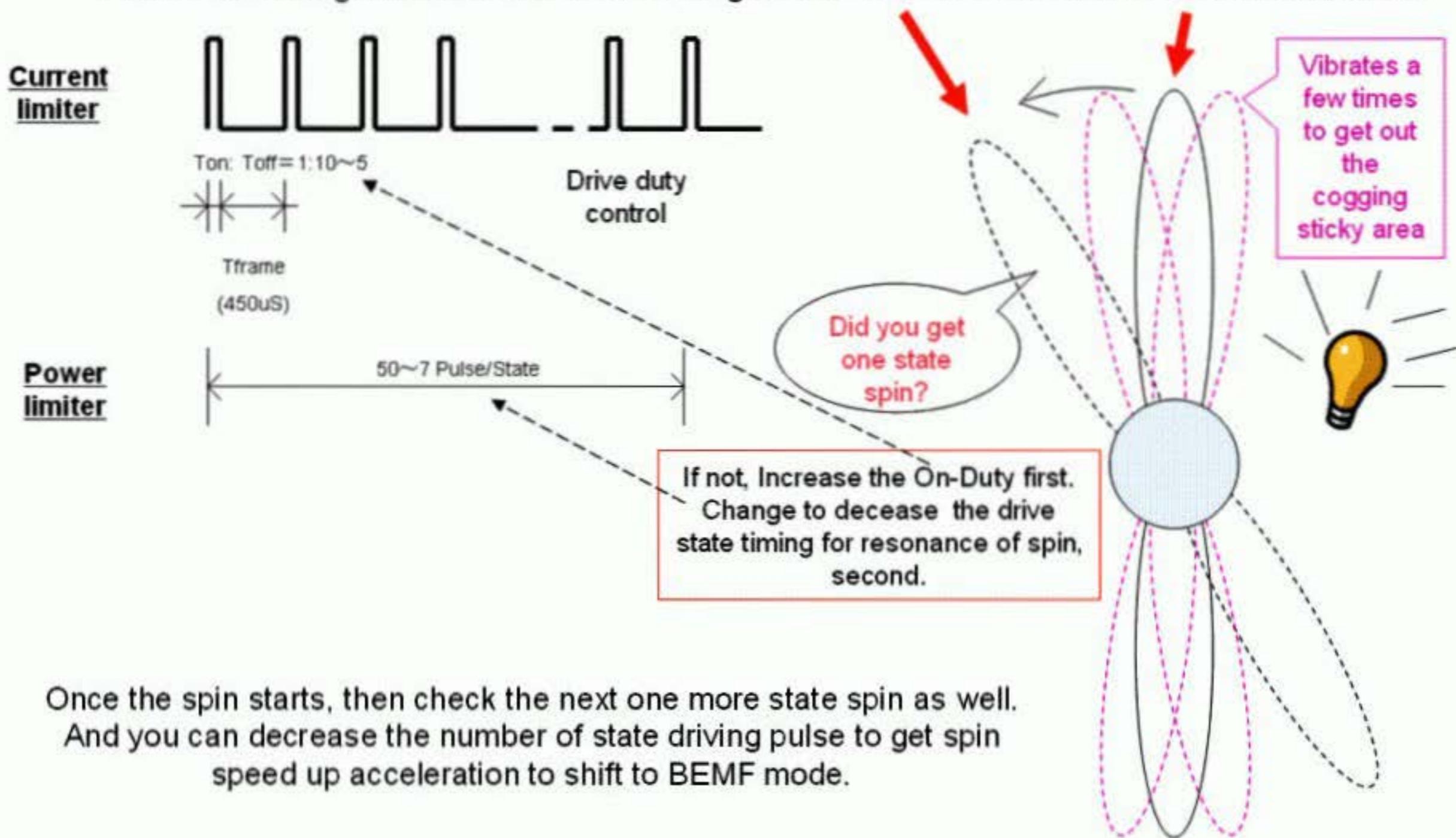
Get the shaft position by measuring the each state inductive kick length.
The minimum length of inductive kick is driving state. And next drive state is the start drive state.



Auto adjust for starting parameters

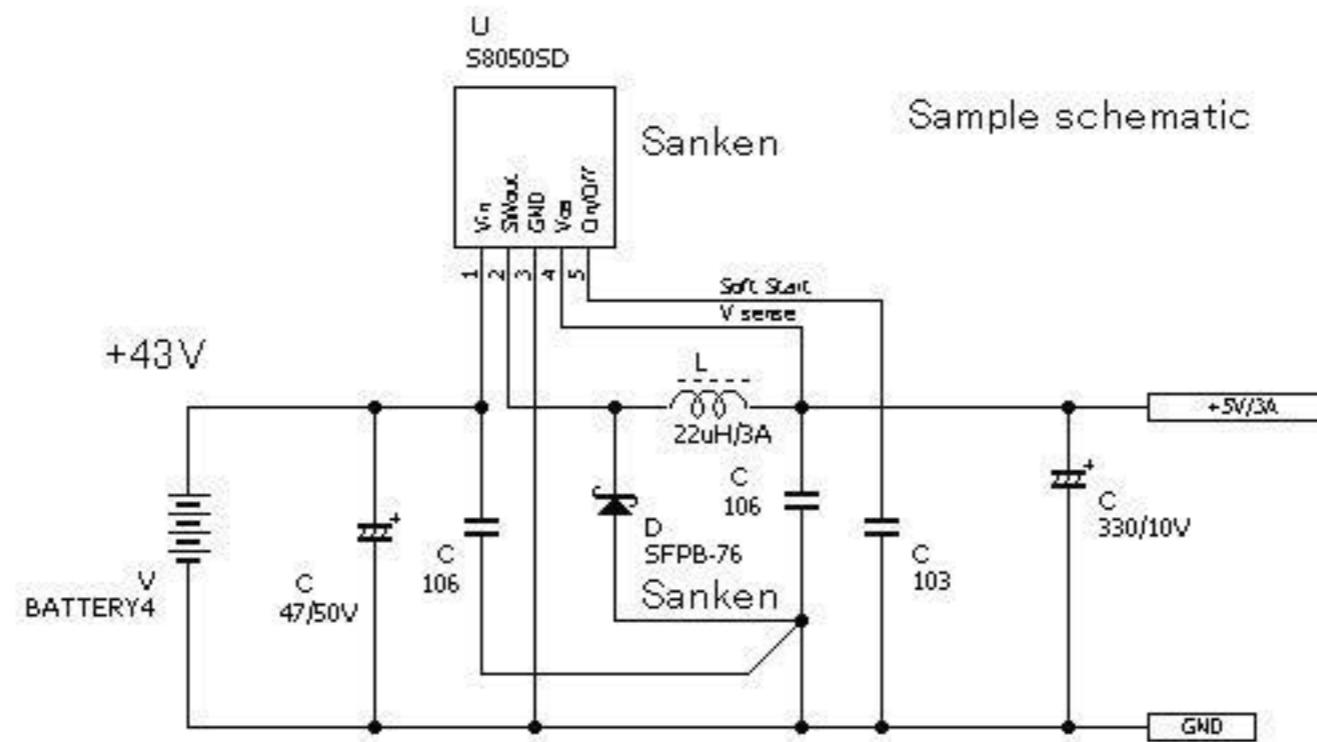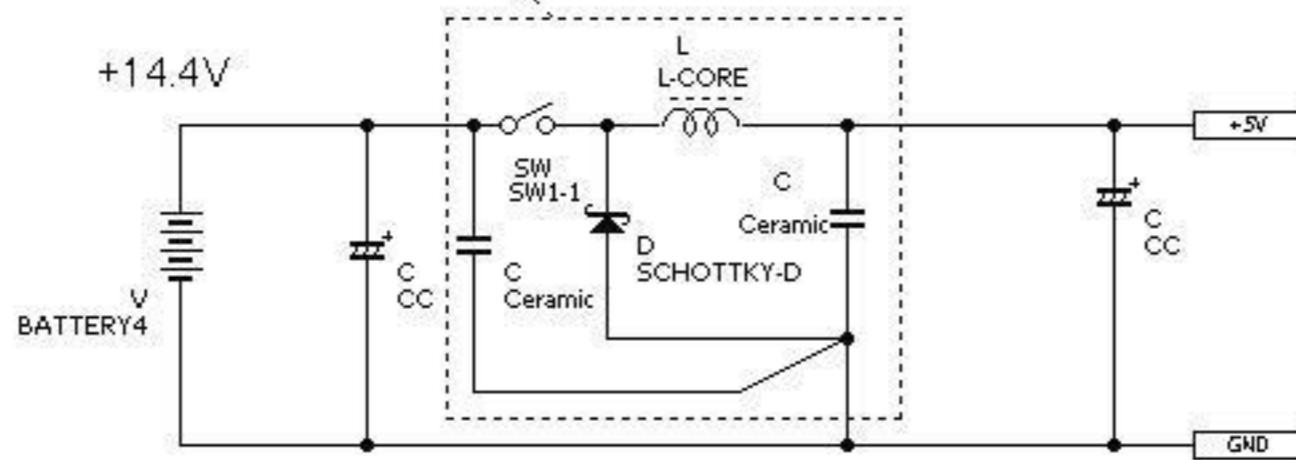
A B C D E
1
There is a possibility of RF interference from Sw. BEC.
The wiring point is making small as possible at switching area.
as the smallest antenna in high current loop.



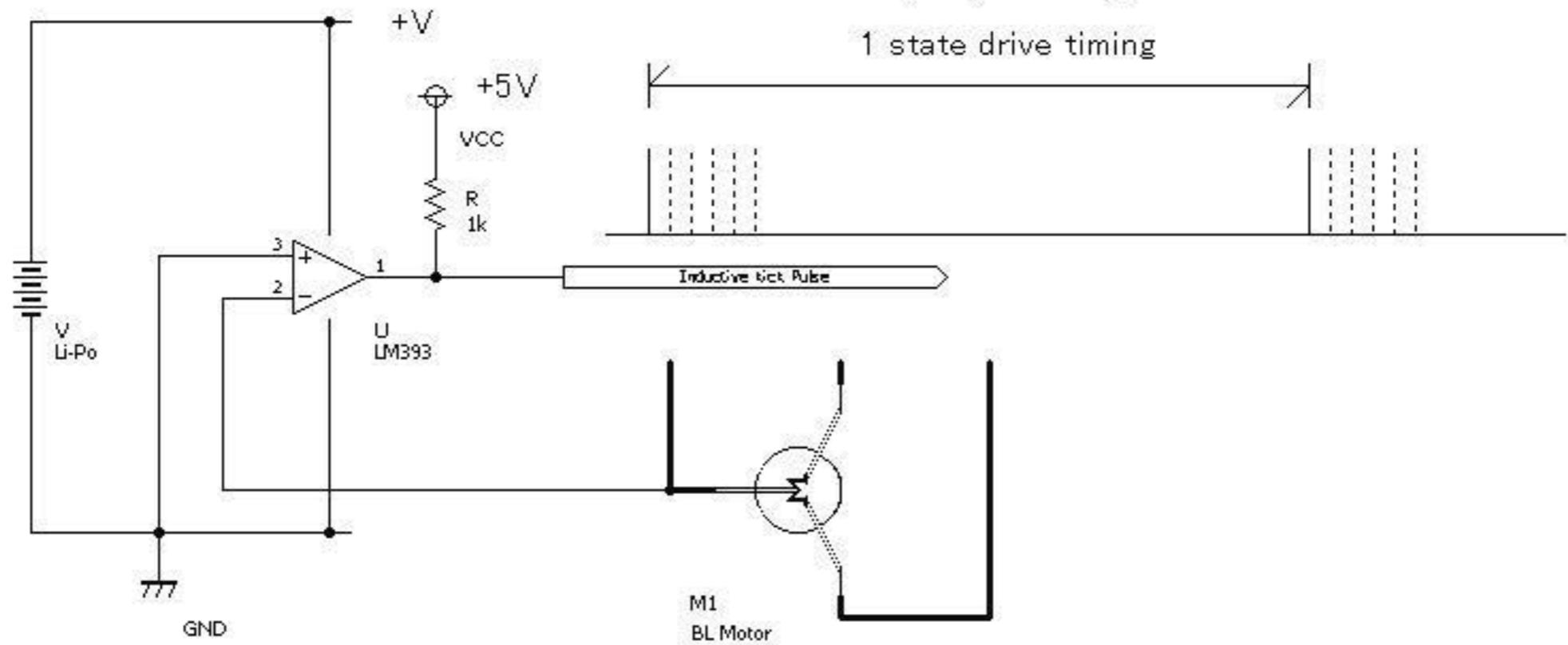


Date	Rev.	Designed by	Title	Page
'06/08/15	0.2	Takao Shimizu	RPM sensing tap	1/1


Points for Acceleration Control

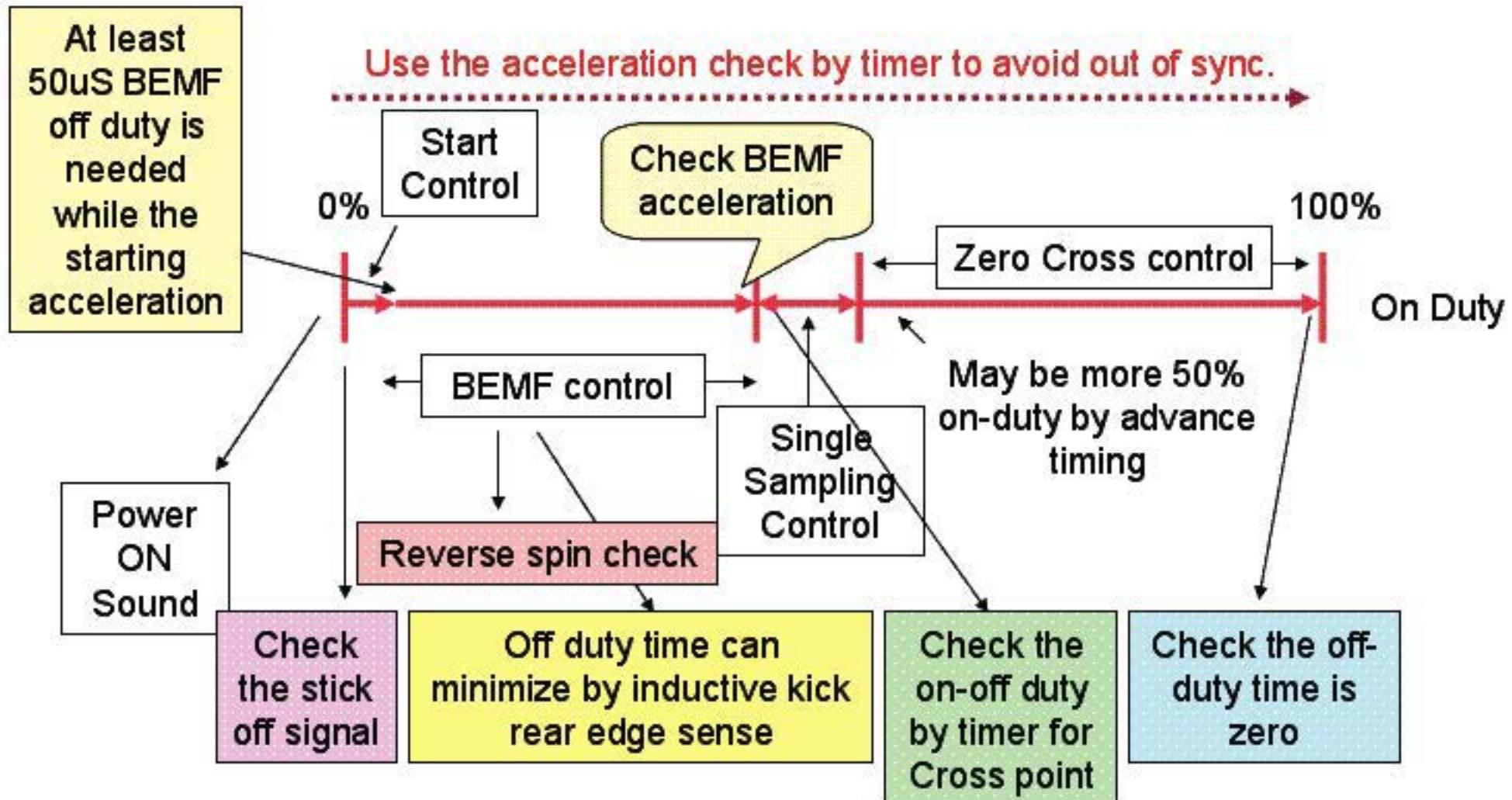

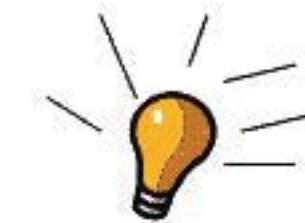The Single Sampling control for AUTO 50% power spin to start zero-cross control



The level sense of zero cross pint is already over in this loop. Therefore, the loop timing is very short. And the 50% power can preciously set.

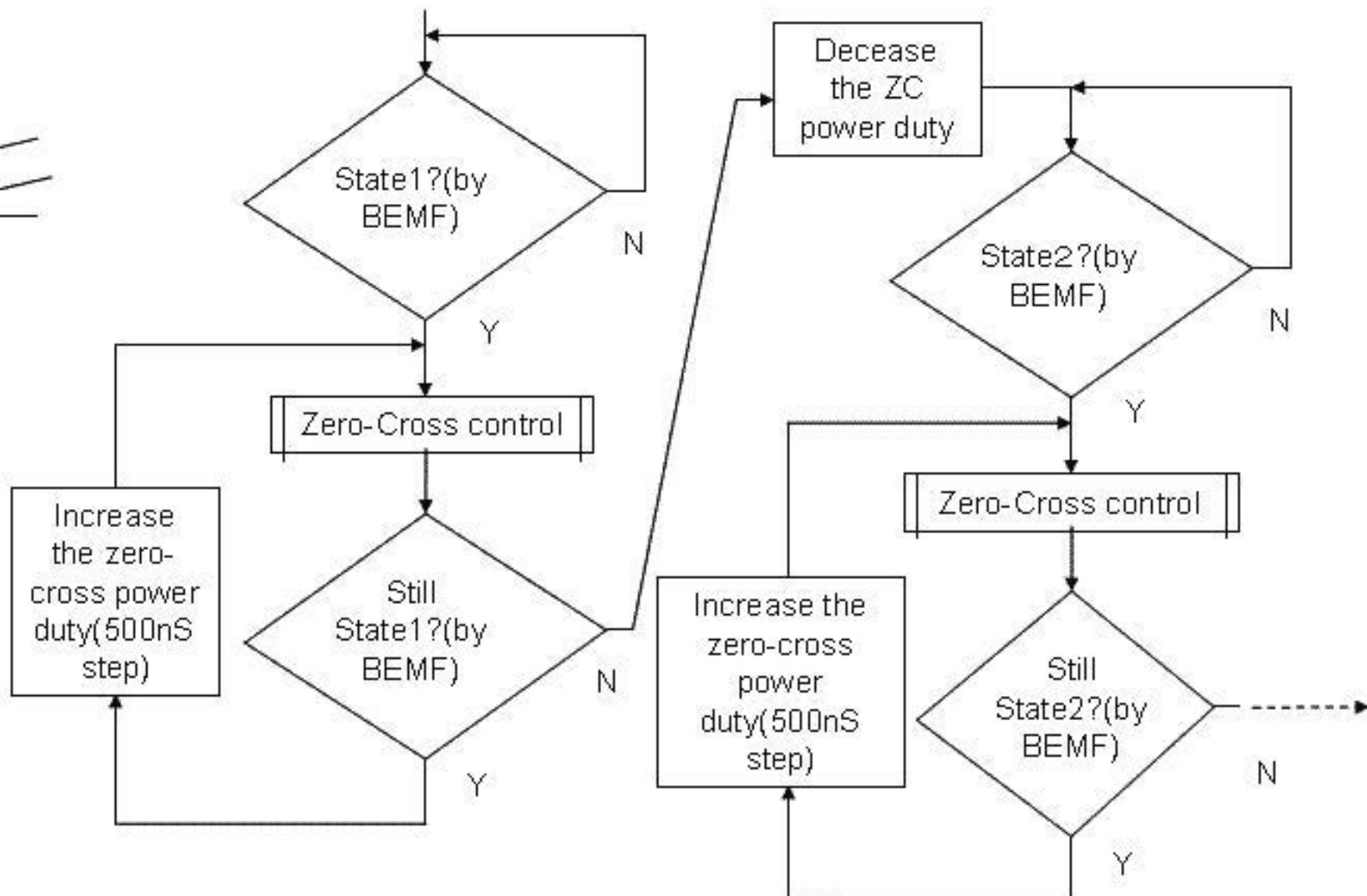

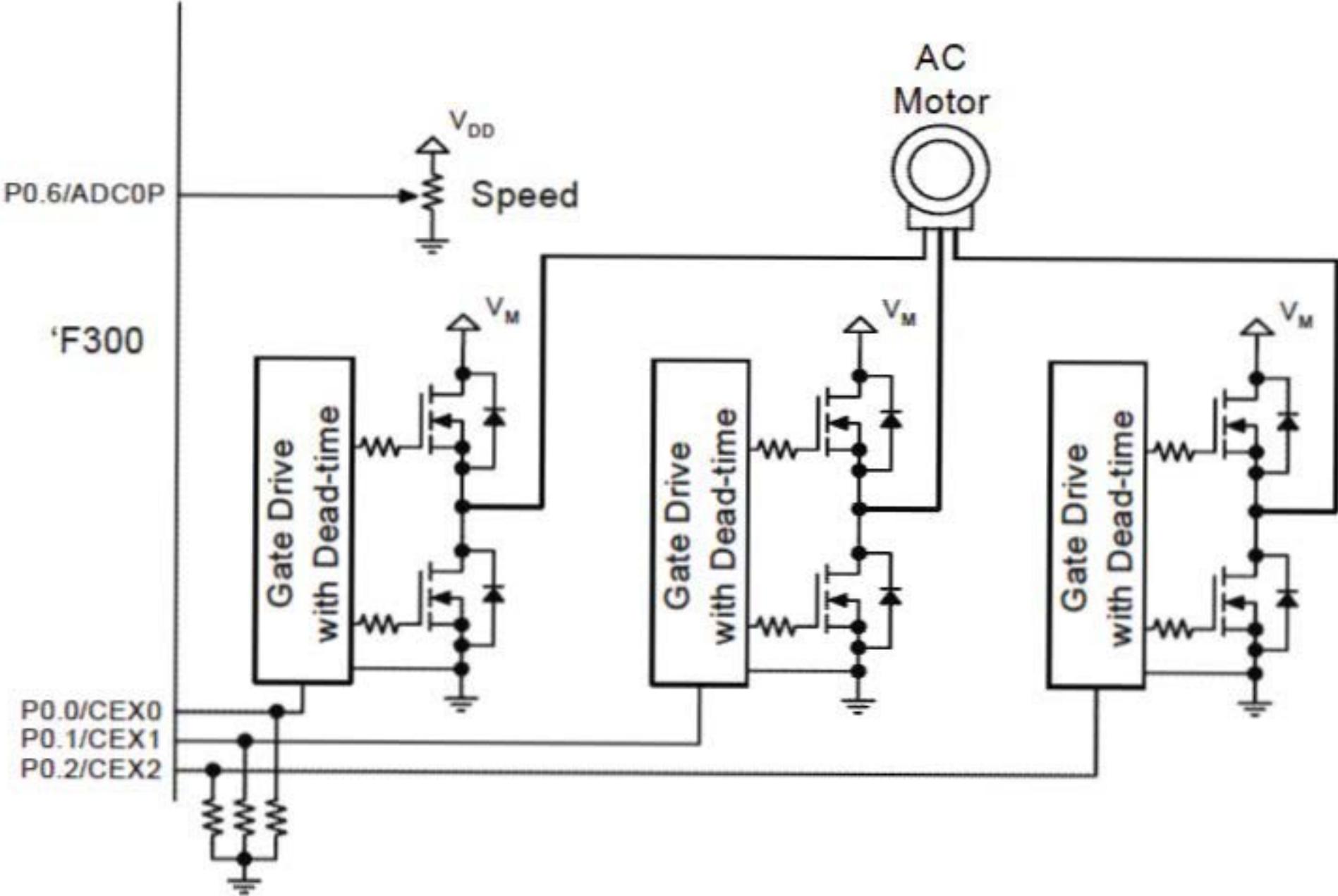


Figure 7. AC Induction Motor Drive


Tek

M

Stop

M Pos: 0.000s

TRIGGER

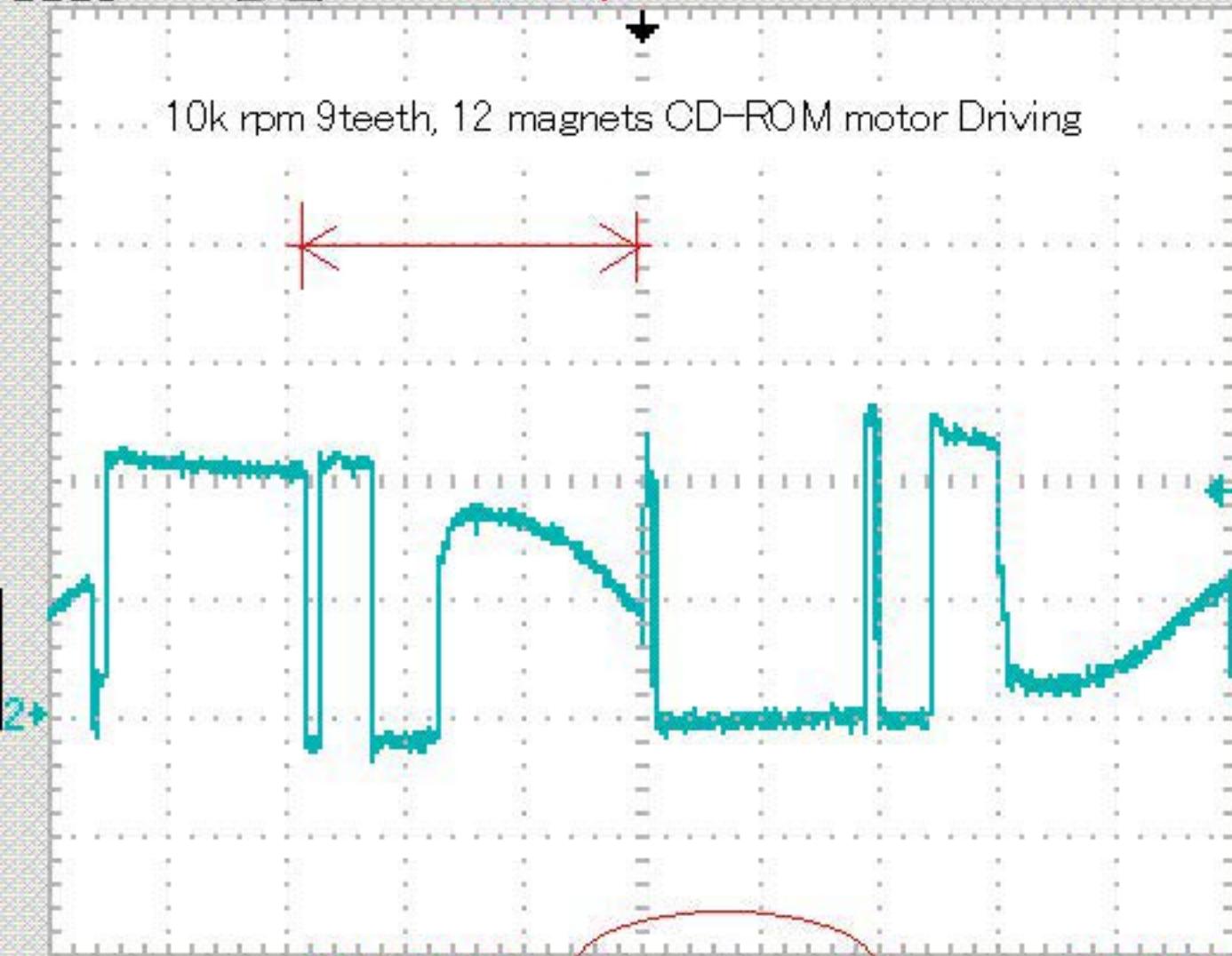

Type
Edge

Source
CH2



Slope
Rising

Mode
Normal

Coupling
DC

13-Sep-06 09:44

<10Hz

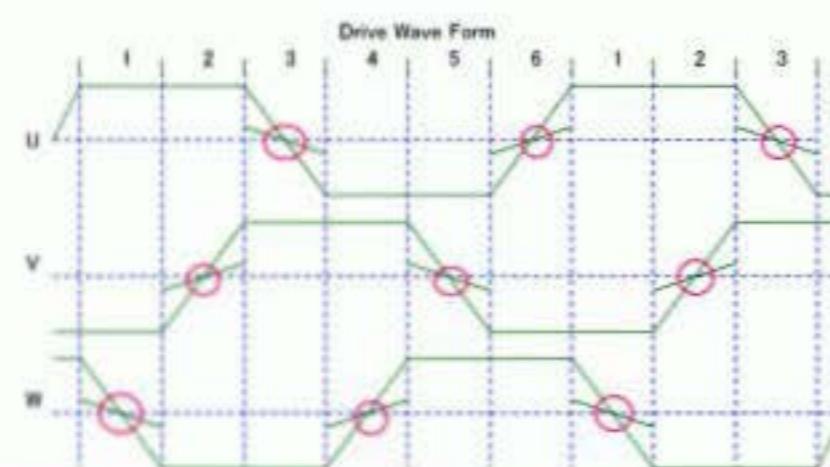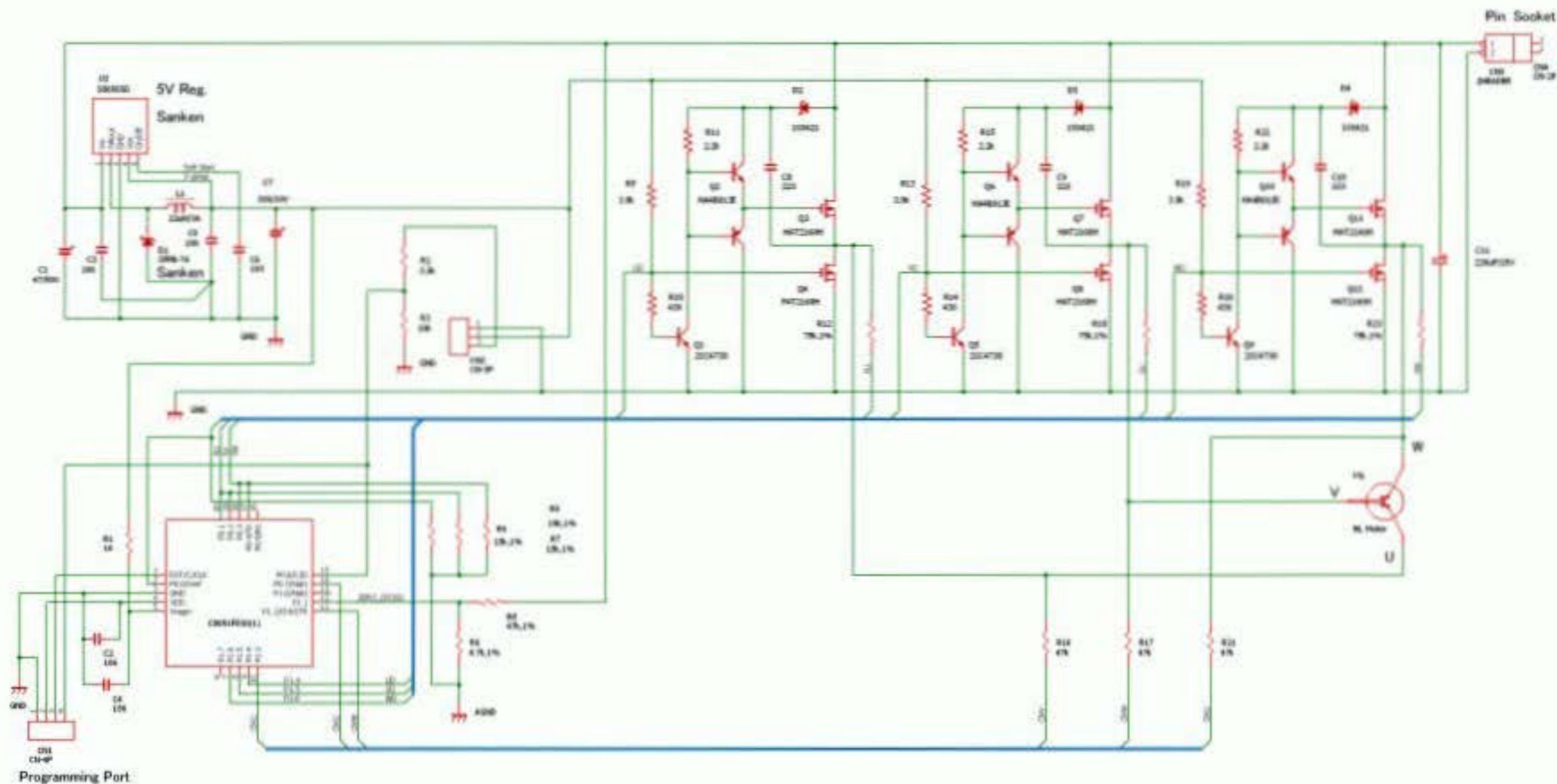



Date	Rev	Designed by	Title	Page
196/12/06	0.1a	Takao Shimizu	Brushless Sensor-less Electric Speed Controller Schematic	1/1

Table 14.1. Port I/O DC Electrical Characteristics V_{IO} = 2.7 to 5.25 V, -40 to +125 °C unless otherwise specified


Parameters	Conditions	Min	Typ	Max	Units
Output High Voltage	$I_{OH} = -3$ mA, Port I/O push-pull	TBD	—	—	V
	$I_{OH} = -10$ μ A, Port I/O push-pull	TBD	—	—	
	$I_{OH} = -10$ mA, Port I/O push-pull	—	TBD	—	
Output Low Voltage	V = 2.7 V: $I_{OL} = 10$ μ A	—	—	TBD	V
	$I_{OL} = TBD$	—	—	TBD	
	$I_{OL} = TBD$	—	TBD	—	
	V = 5.25 V: $I_{OL} = 10$ μ A	—	—	TBD	
	$I_{OL} = 8.5$ mA	—	—	TBD	V
	$I_{OL} = 25$ mA	—	TBD	—	
Input High Voltage		TBD	—	—	V
Input Low Voltage		—	—	TBD	V
Input Leakage Current	Weak Pullup Off	—	—	\pm TBD	μ A
	Weak Pullup On, $V_{IN} = 0$ V; $V = 2.0$ V	—	< 0.11	TBD	
	Weak Pullup On, $V_{IN} = 0$ V; $V = 2.4$ V	—	< 0.14	TBD	

Typical Transfer Characteristics

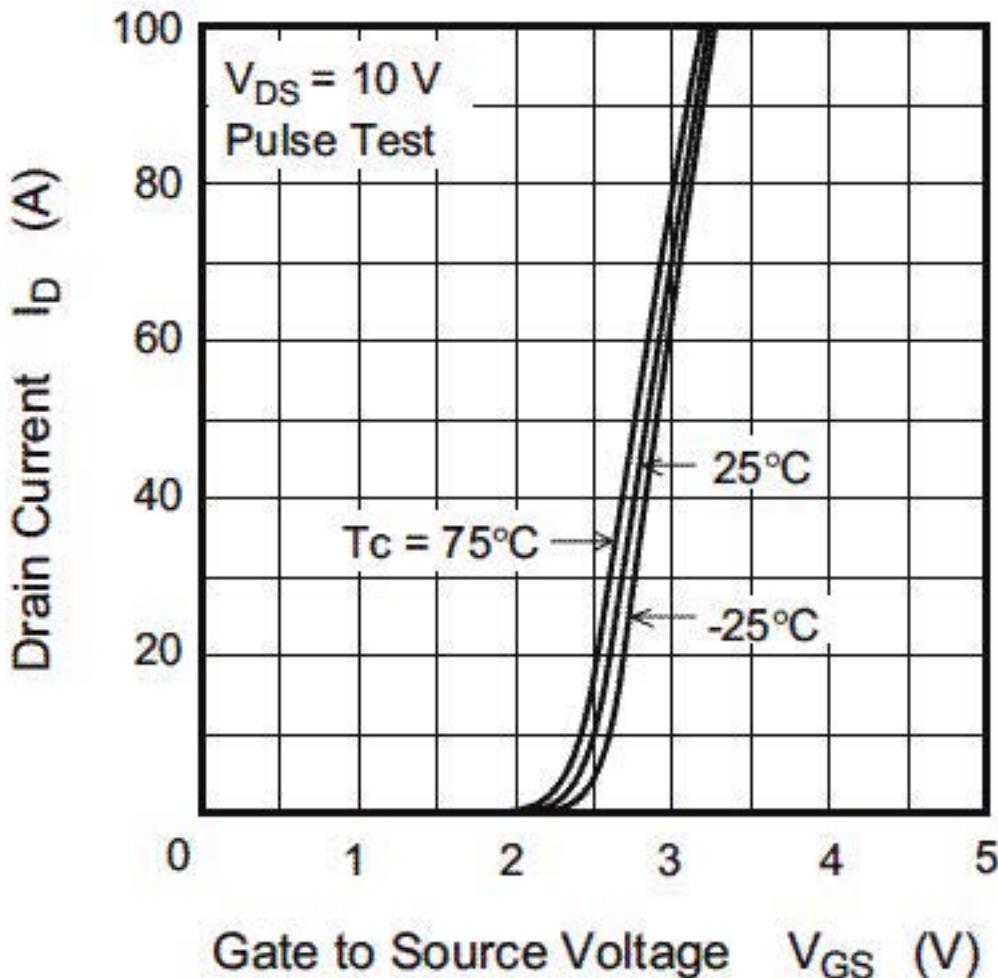

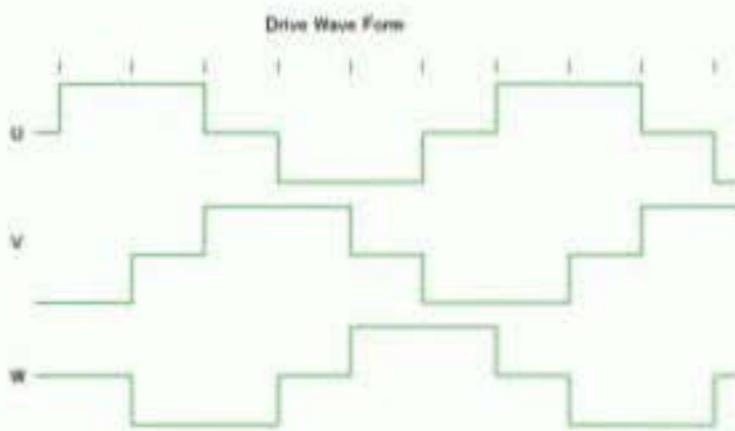


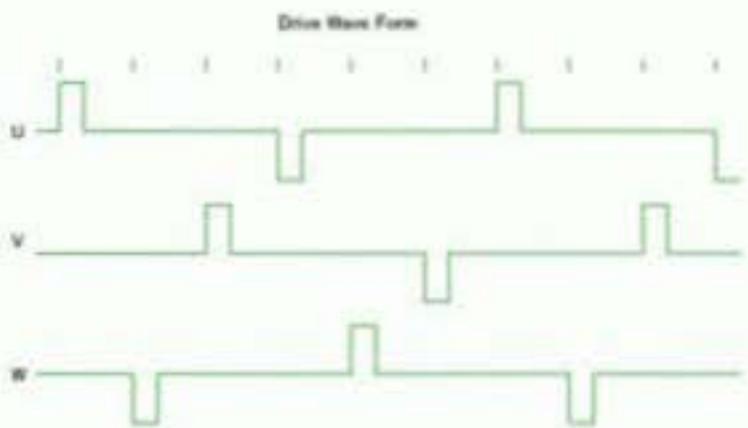Can not drive the coil too small resistance.





You can reduce the starting current. But, It only vibrate only... Never start.

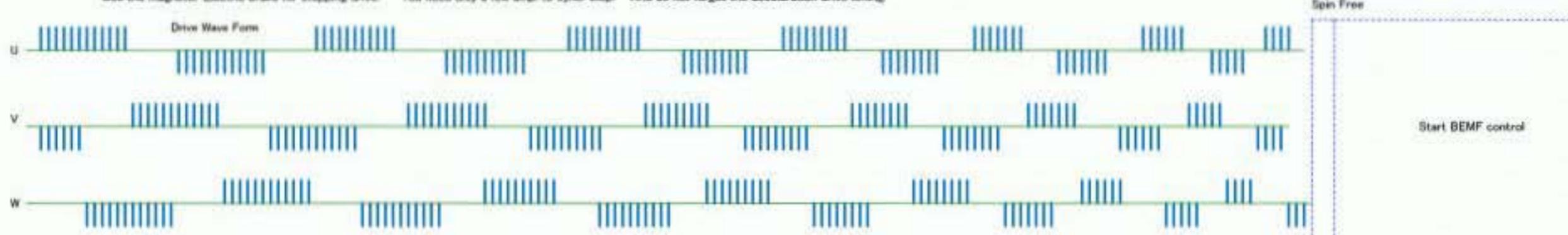
Use the magnetic-Electric brake for stopping drive. You need only a few amp. to sync. stop. And do not forget the acceleration drive timing.



Date	Rev	Designed by	Title	Page
07/01/10 0.1		Takeshi Shimizu	Sensor-less Brush-less Motor starting control image	1/1

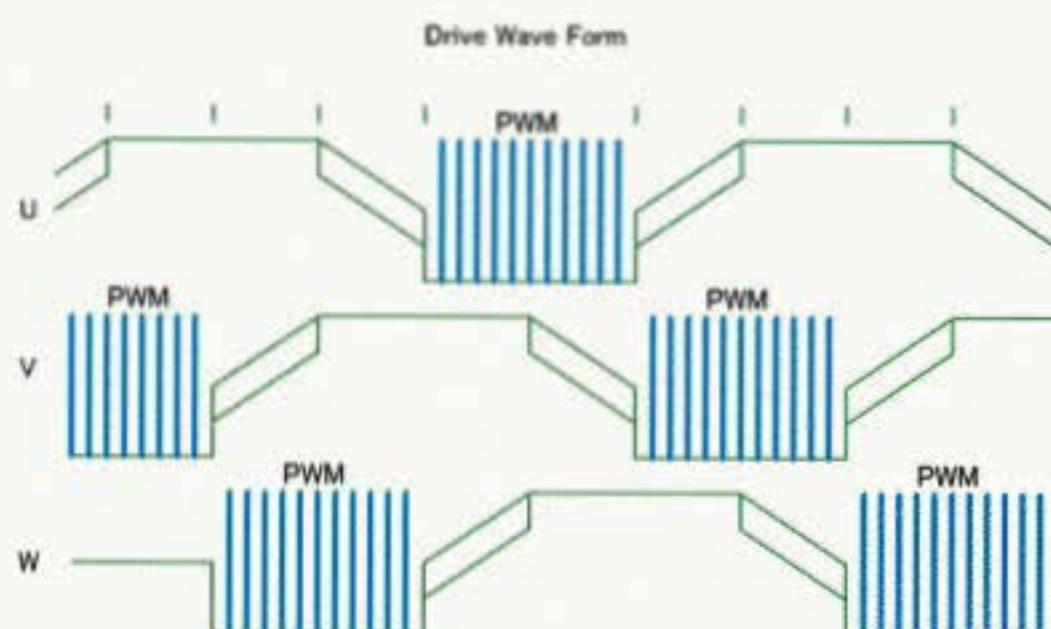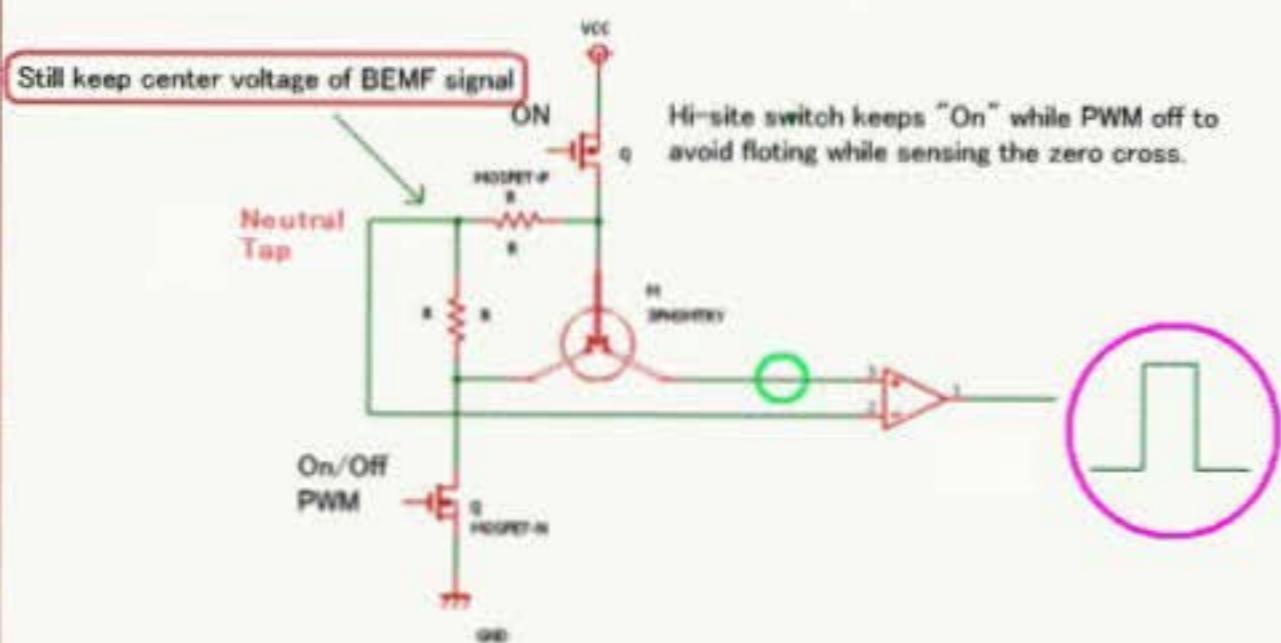


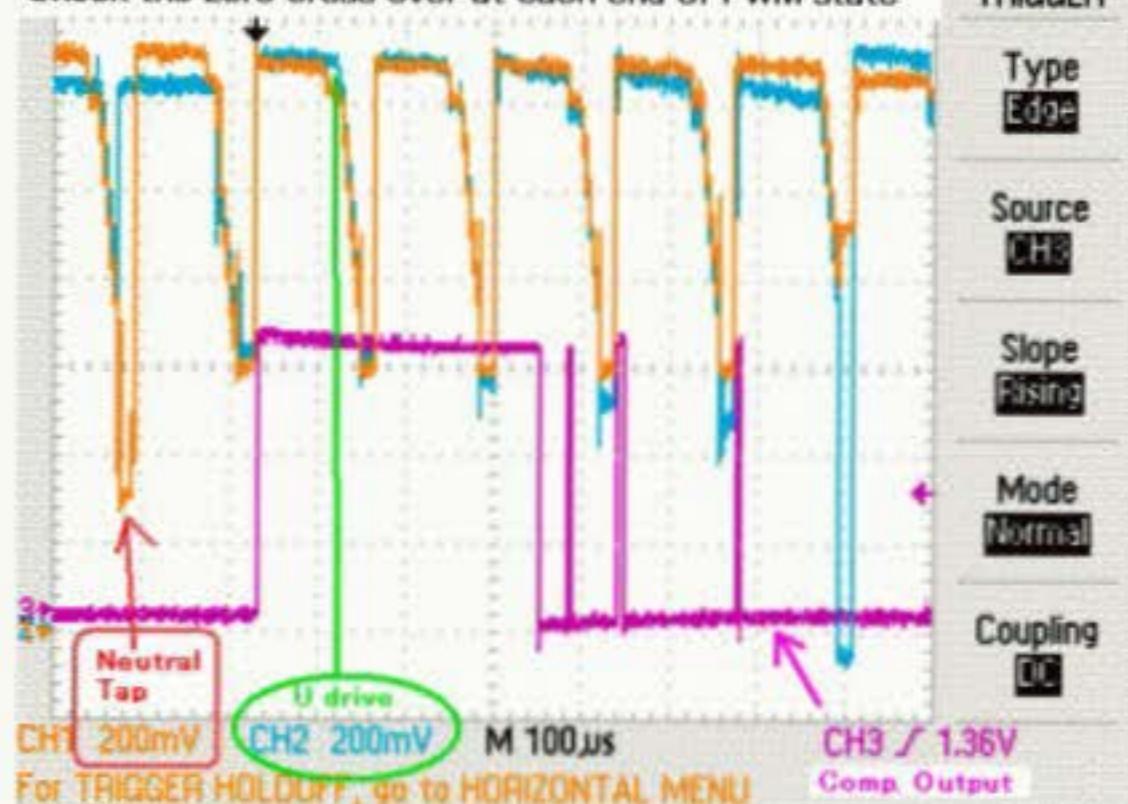Check the zero cross over at each end of PWM state



Date	Rev.	Designed by	Title	Page
07/01/20	0.1	Takao Shimizu	Zero Cross sensing while PWM switching	1/1

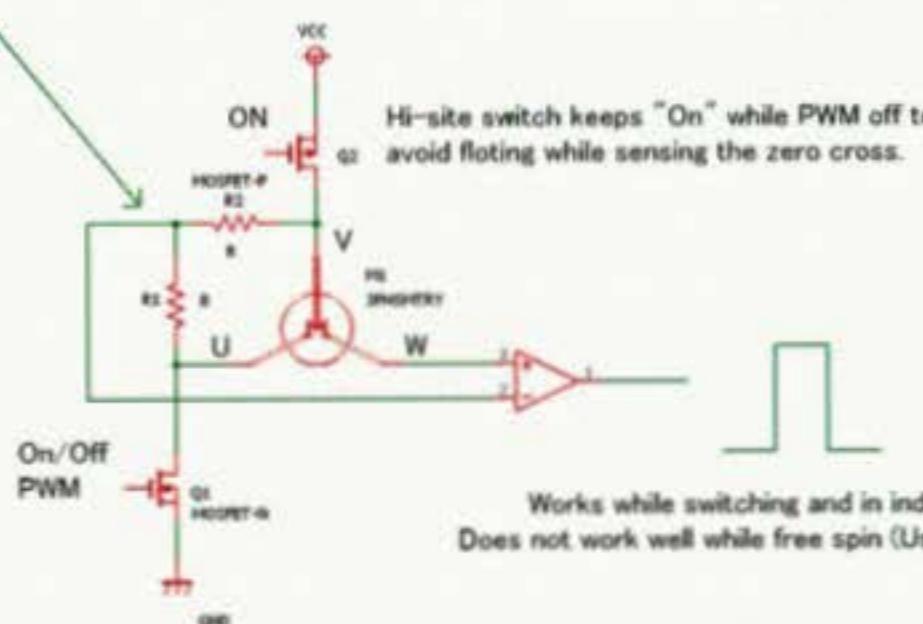
Still keep center voltage of BEMF signal while switching, and in inductive kick



Hi-side switch keeps "On" while PWM off to avoid floating while sensing the zero cross.

Works while switching and in inductive kick.
Does not work well while free spin (Use BEMF control instead).

Virtual Neutral

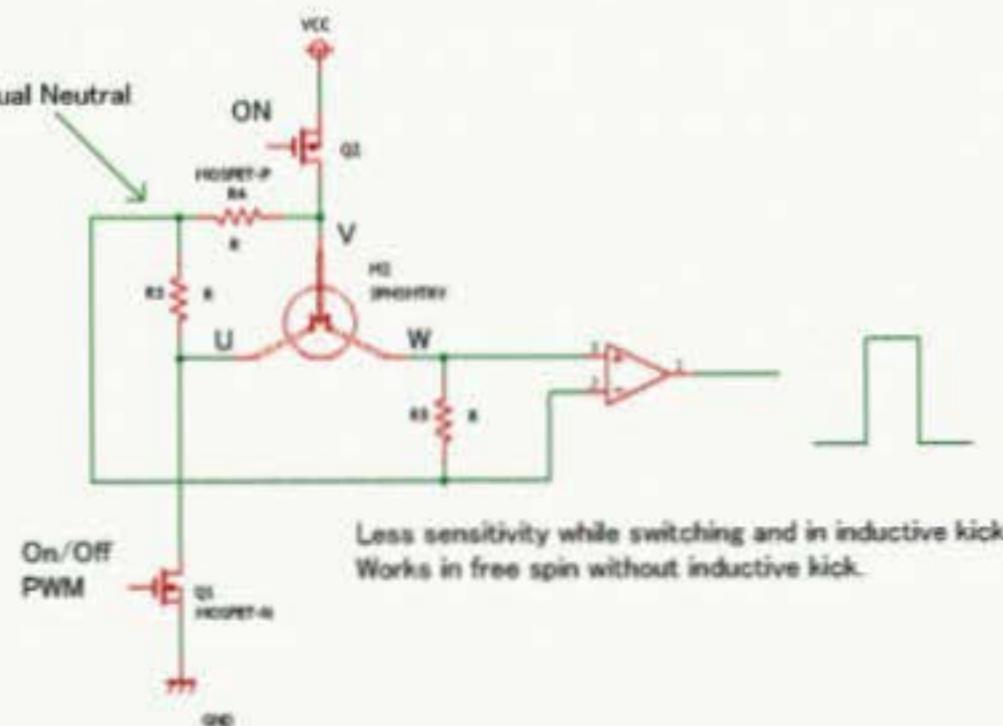


Less sensitivity while switching and in inductive kick.
Works in free spin without inductive kick.

Fig.1: Two wire center tap sensing

Fig.2: Virtual Neutral sensing

Drive Wave Form

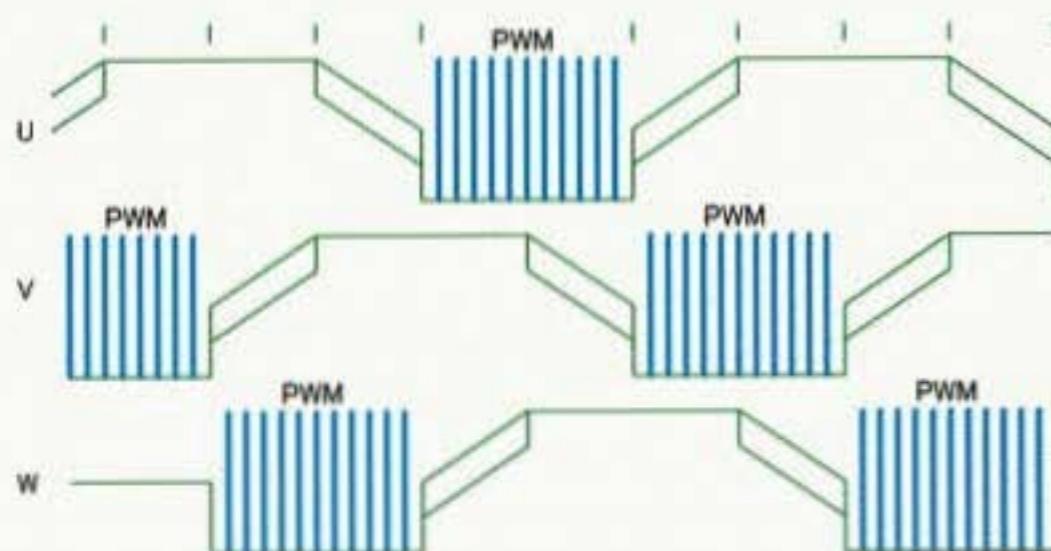

Note:

- * Each generative voltage wave is 120 degree difference while PWM off as free spin.
But, the activated lines are 180 degree difference in switching drive mode.

- * There is the difference of $R_{ds\text{-ON}}$ between Q1 and Q2

Date	Rev.	Designed by	Title	Page
07/01/27	0.2	Takao Shimizu	Zero Cross sensing while PWM switching	1/1


Tek

M

Stop

M Pos: 0.000s

CH3

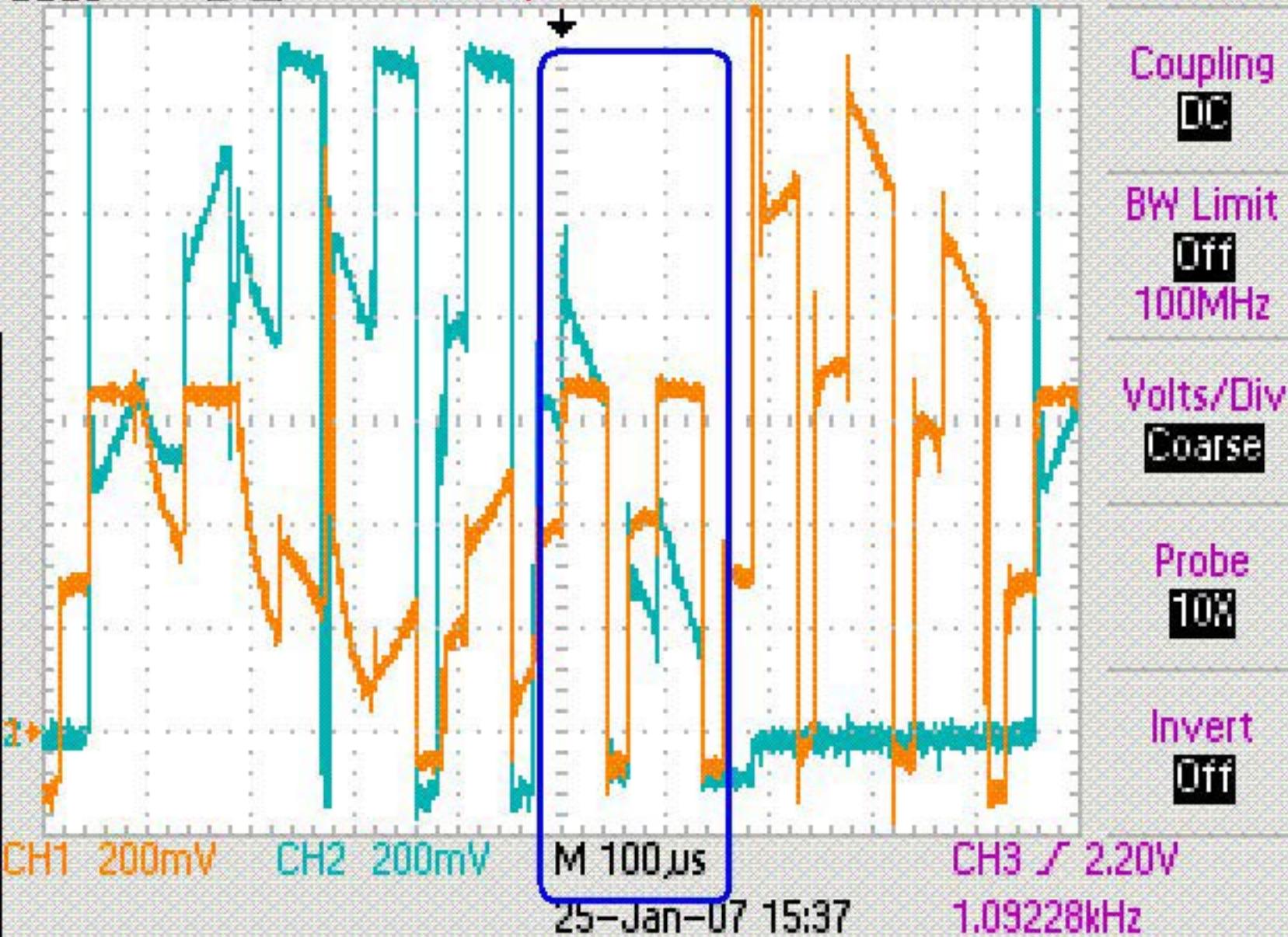


Tek

M

Stop

M Pos: 0.000s

CH3

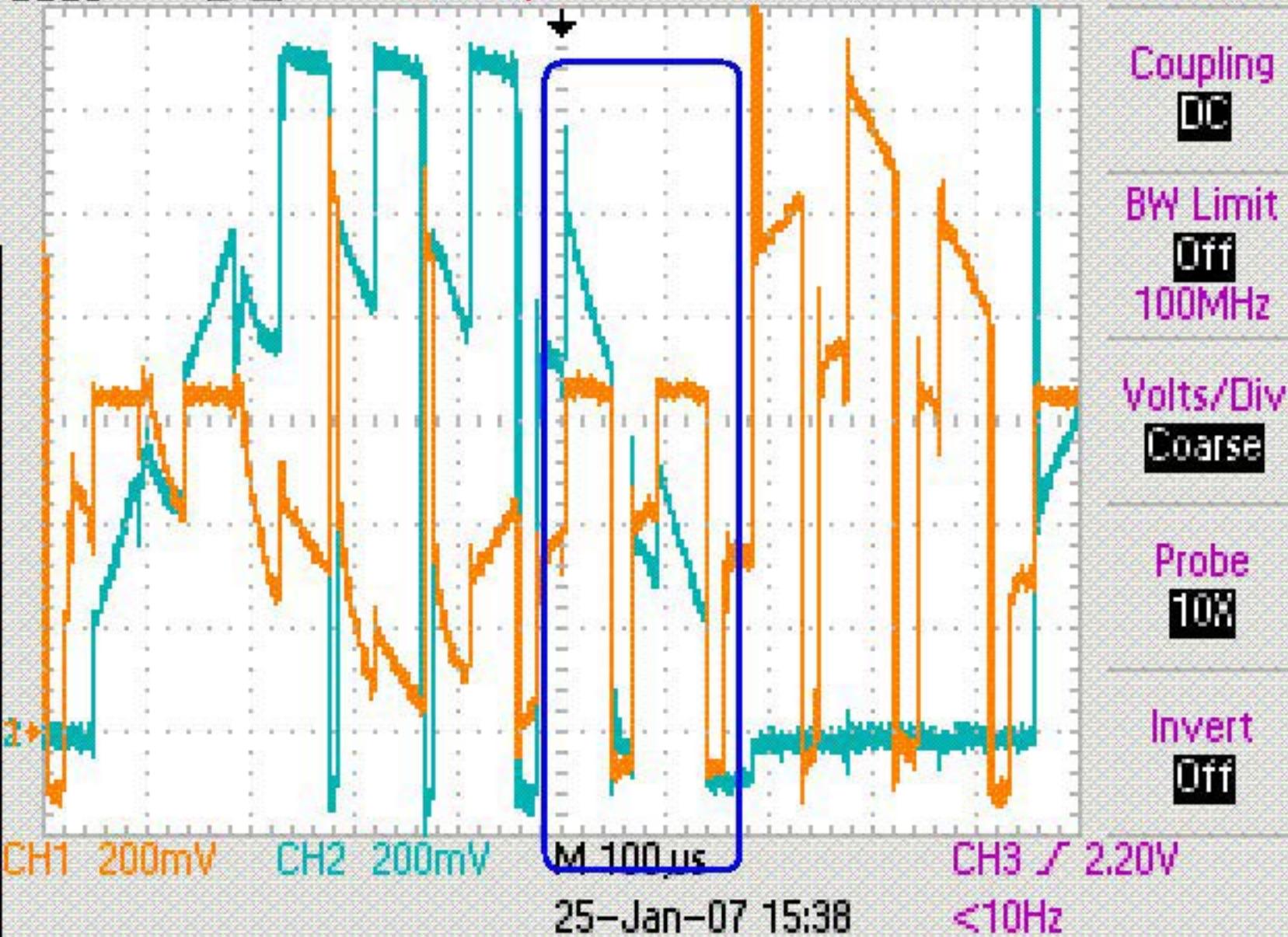


Tek

M

T Trig'd

M Pos: 0.000s

CH3

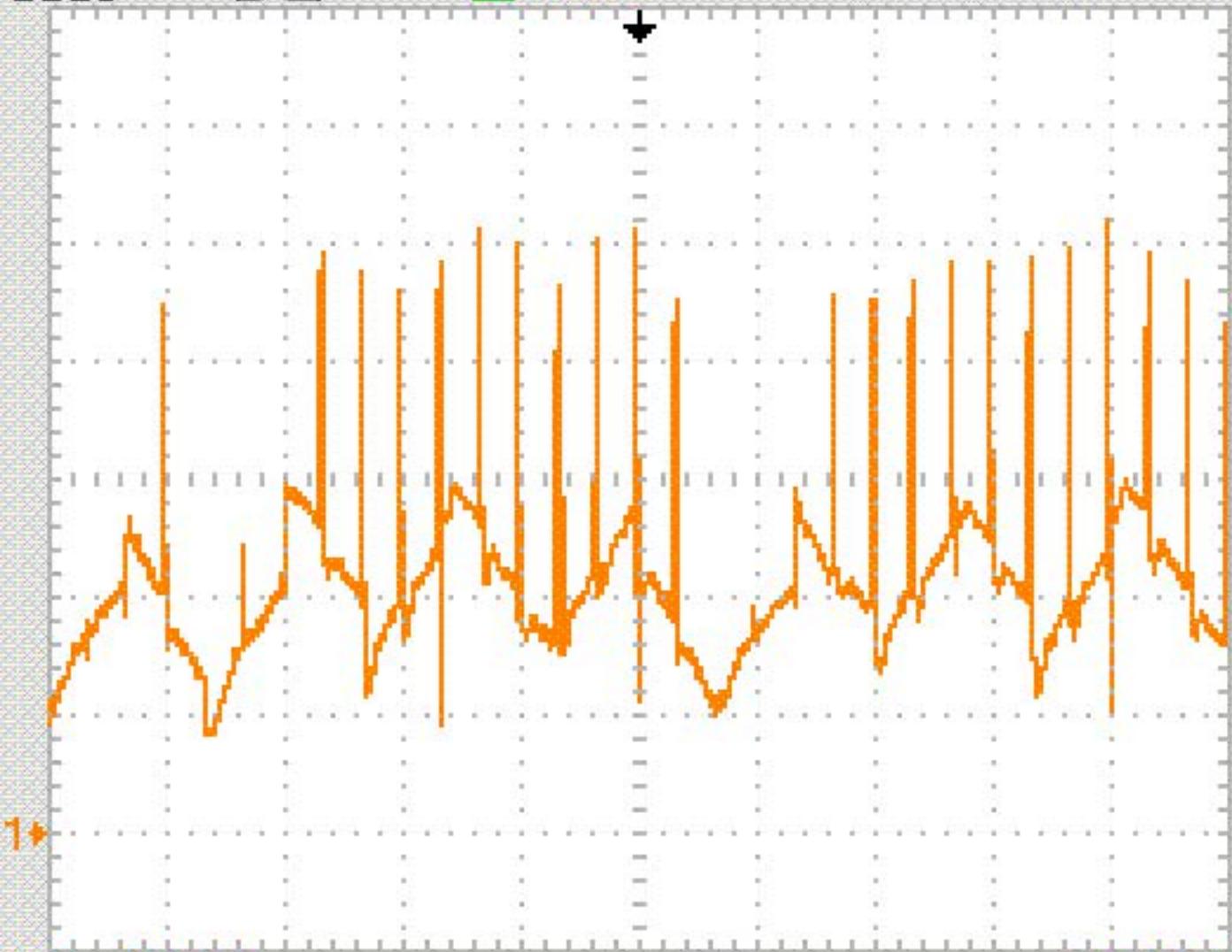

CH1 200mV

M 250 μ s

CH3 / 3.20V

27-Jan-07 15:16

940.224Hz

Coupling

DC

BW Limit

Off

100MHz

Volts/Div

Coarse


Probe

10X

Invert

Off

Fig : 1/2 VDD sensing

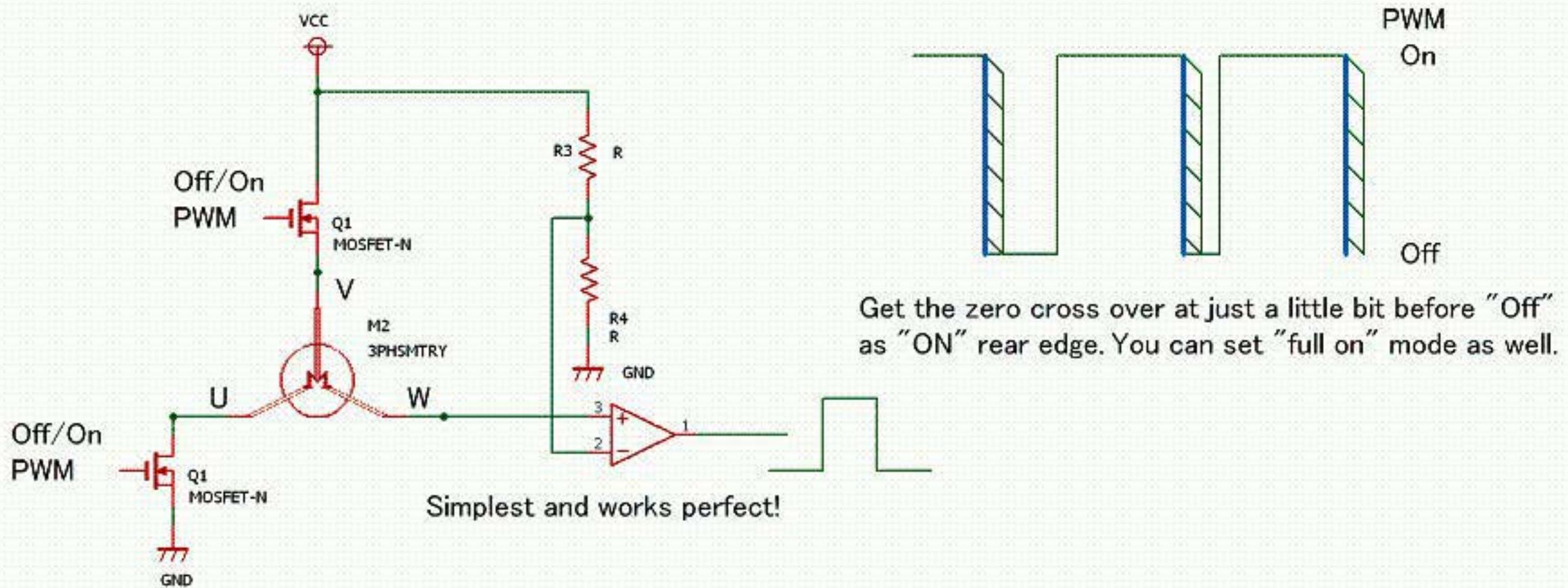

Note:

*Use same MOSFET both H/L site.

*"Off" first, And "On". Get the zero cross detect result at the of "ON" fall egde for sampling.

Date	Rev.	Designed by	Title	Page
'07/01/27	0.2	Takao Shimizu	Zero Cross sensing while PWM switching	1/1


Tek

fl.

T Trig'd

M Pos: 0.000s

CH3

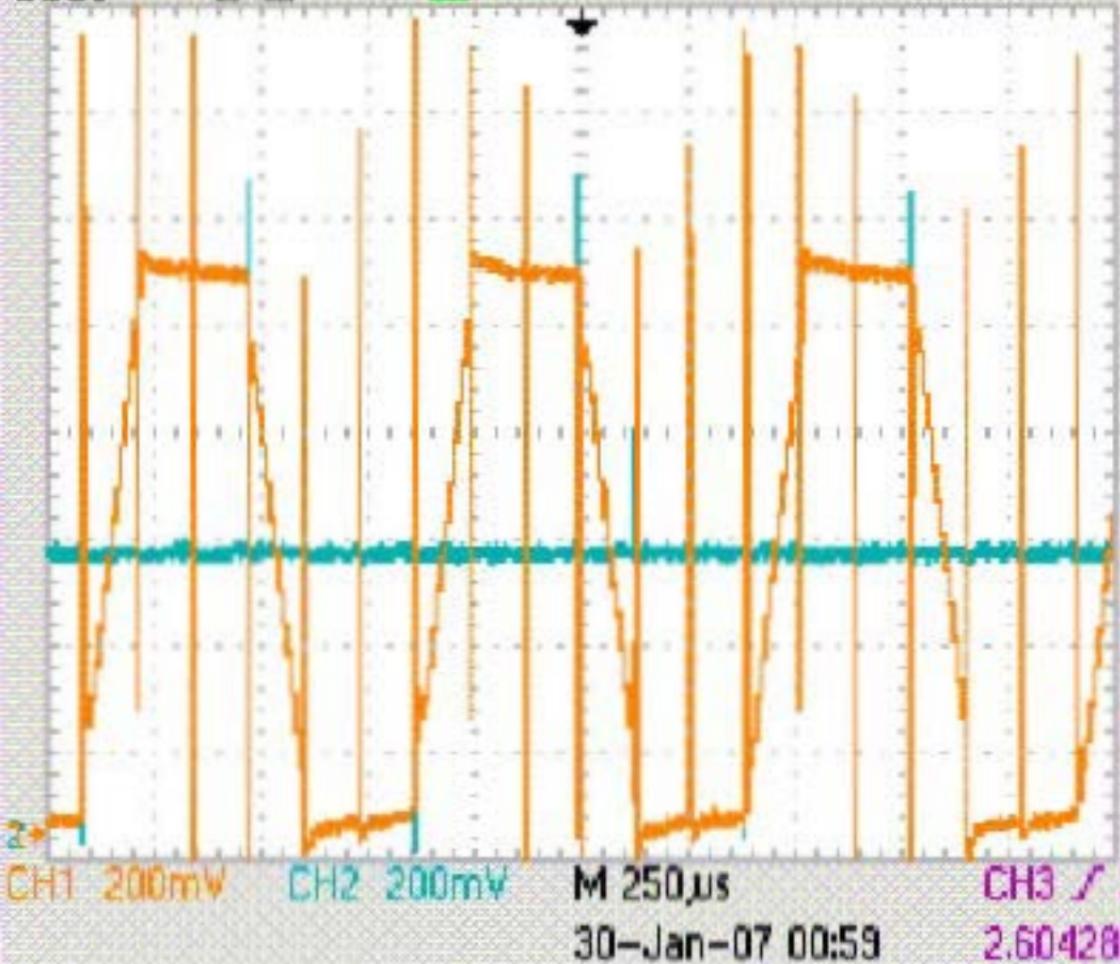

Coupling

DC

BW Limit

Off

100MHz

Volts/Div

Coarse

Probe

10X

Invert

Off


Tek

Flu

T Trig'd

M Pos: 0.000s

CH3

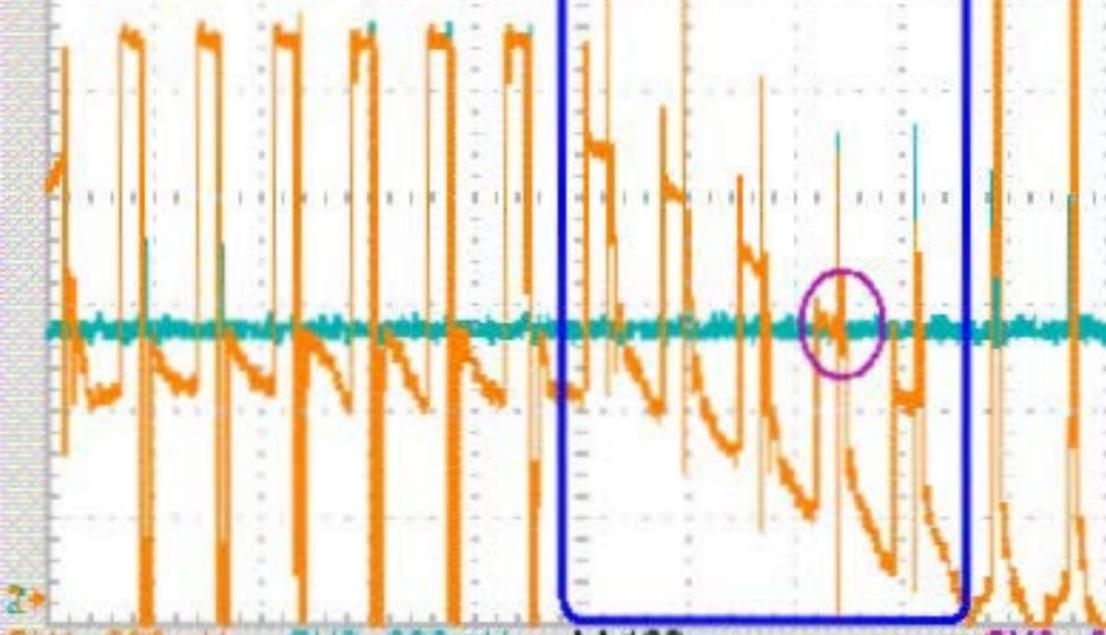

Coupling

DC

BW Limit

Off

100MHz

Volts/Div

Coarse

Probe

10X

Invert

Off


Tek

In

T Trig'd

M Pos: -200.0ns

CH3

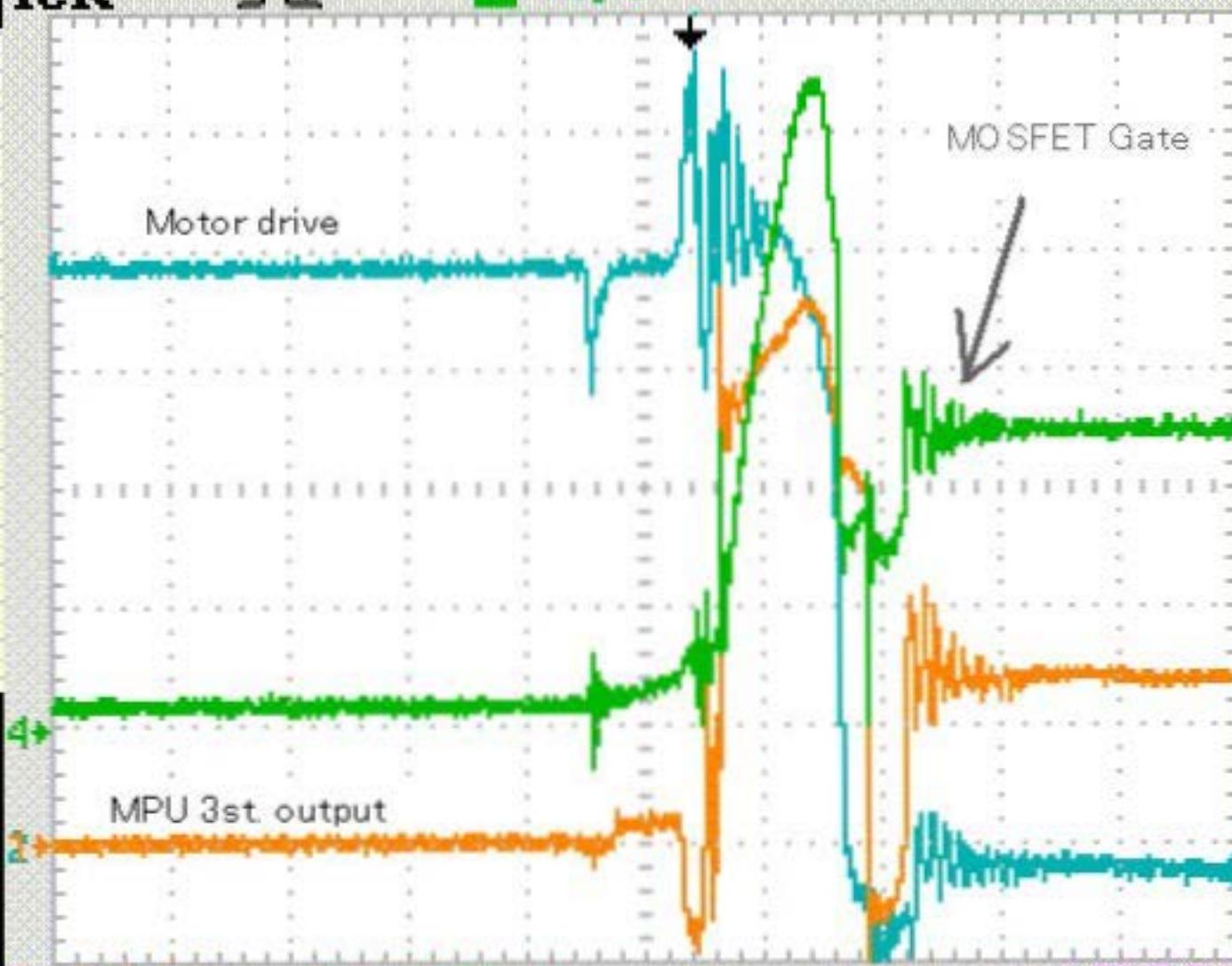

Coupling

DC

BW Limit

Off

100MHz

Volts/Div

Coarse

Probe

10X

Invert

Off

CH1 1.00V

CH2 200mV


M 500ns

CH3 2.88V

CH4 500mV

18-Feb-07 15:49

1.01485kHz

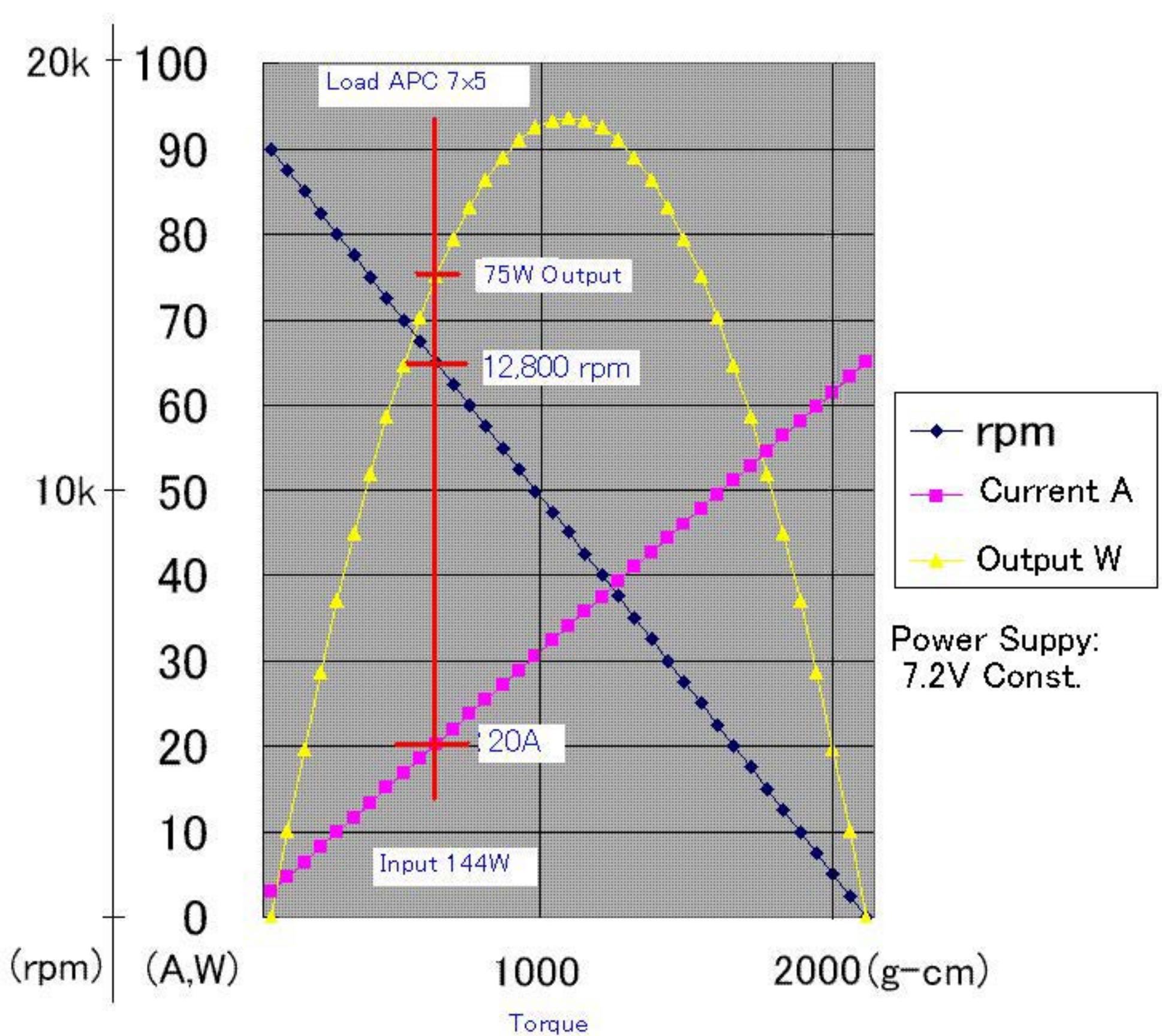

RS-540 Sports tuned motor
(Tamiya Brand)

8.7.5.3 If the motor is sensored:

It must use a six position JST ZH connector model number ZHR-6 or equivalent connector with 6 JST part number SZH-002T-PO.5 26-28 awg contacts or equivalent.

Wire sequence must be as follows:

Pin #1- Black wire-ground potential

Pin #2- Orange wire-phase C


Pin #3- White wire-phase B

Pin #4- Green wire-phase A

Pin #5- Blue wire-temp control, 10 k Thermistor referenced to ground potential

Pin #6- Red wire-+ 5.0 volts =/- 10% Mine is 3.3V operation CPU. This is over Vdd.

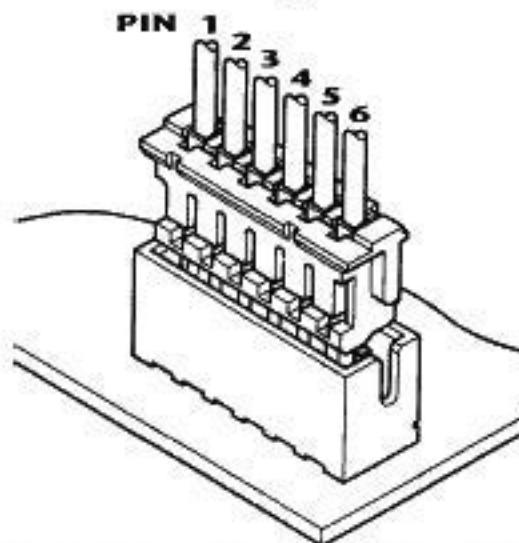For clarification pin #1 is on the left hand side of the above connector with the wires exiting the top of the connector and the plastic tangs that hold the contacts in the housing are facing forward. See drawing below.



Coil temp?


Compatible speed control must use the six position JST header part number X-6B-ZR-SMX-TK (where the X denotes the style of the header), or equivalent.

The power connector has to be clearly marked A, B, C. on both speed control and motor.


A for phase A

B for phase B


C for phase C

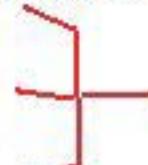


The comparator may be
installed in the motor?

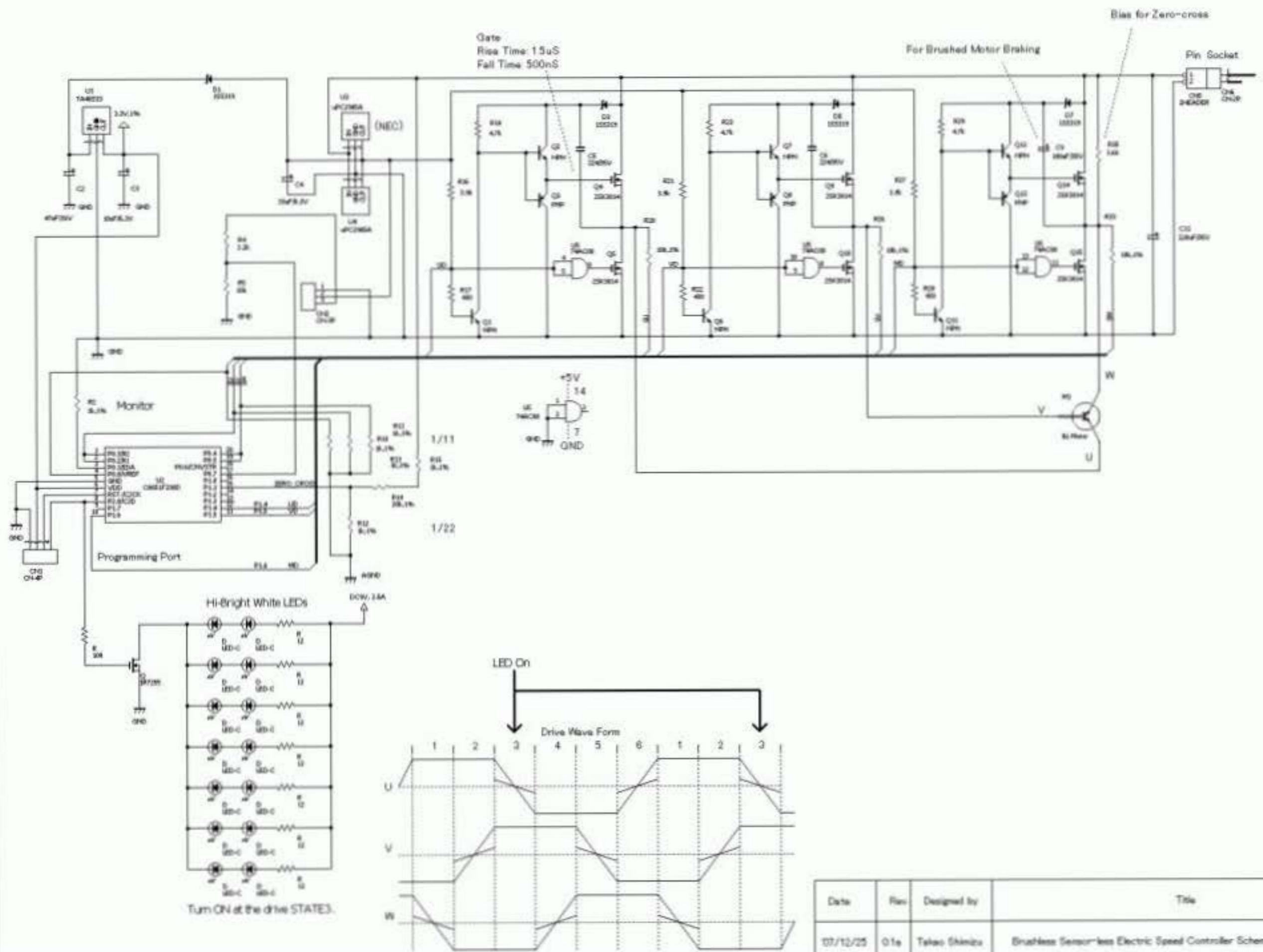


ATmega48

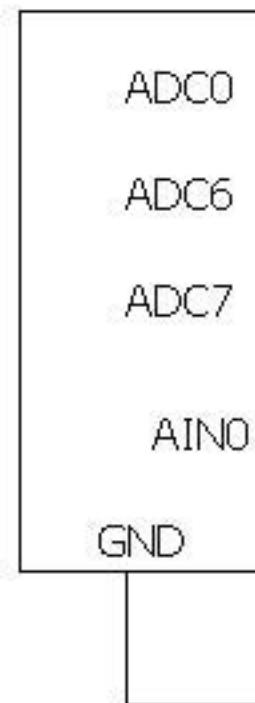

Virtual Center Tap
Point

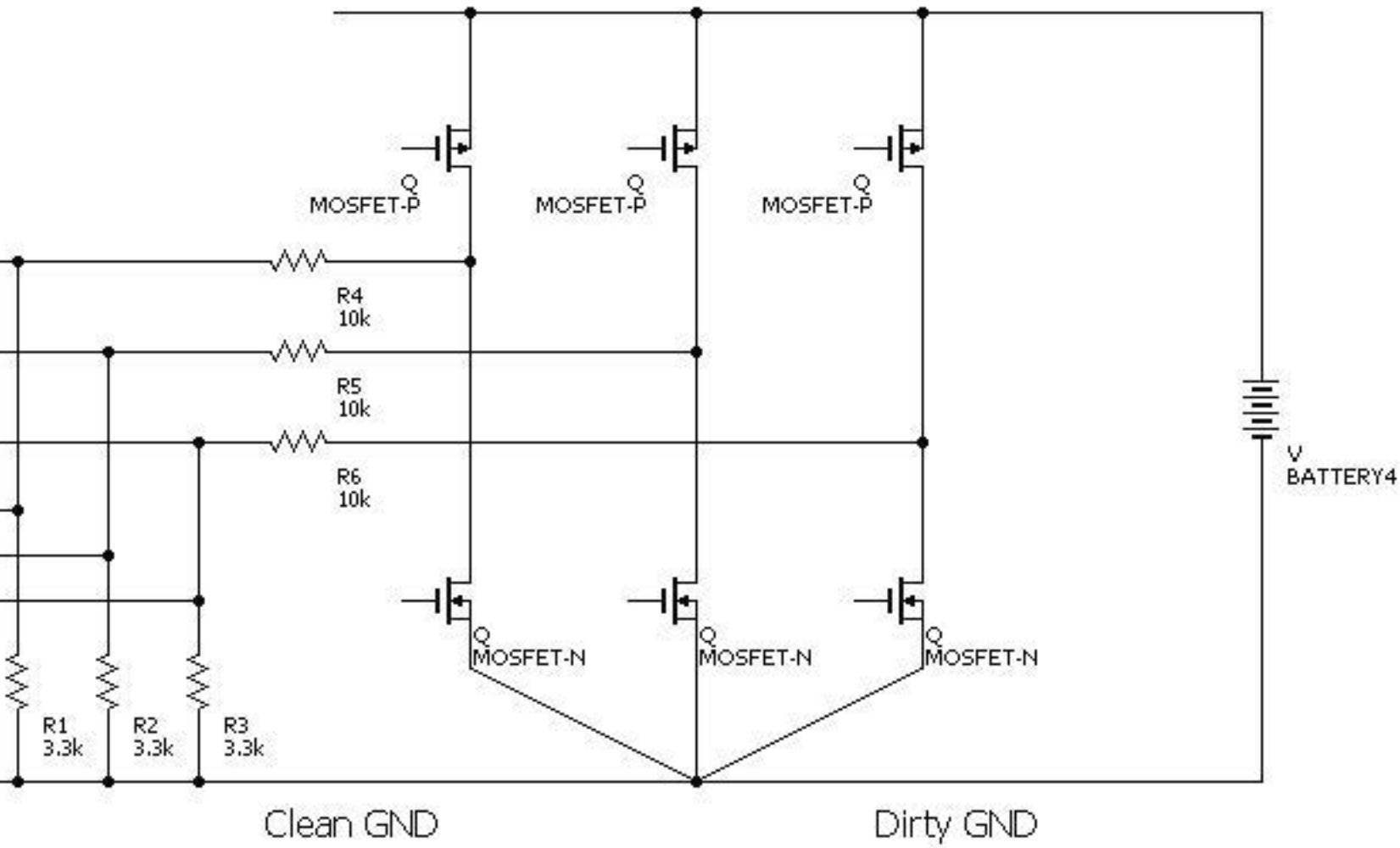


Minimum capacity
battery



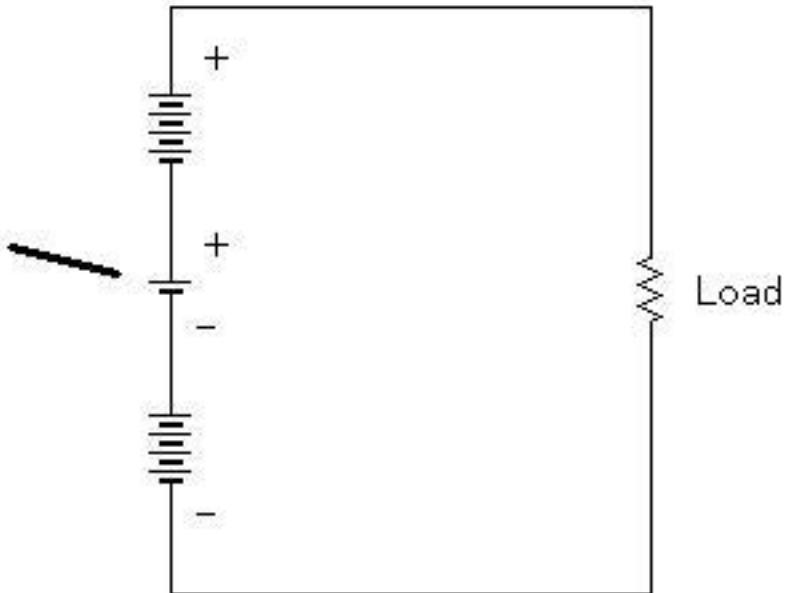


Discharging

All Same circuit

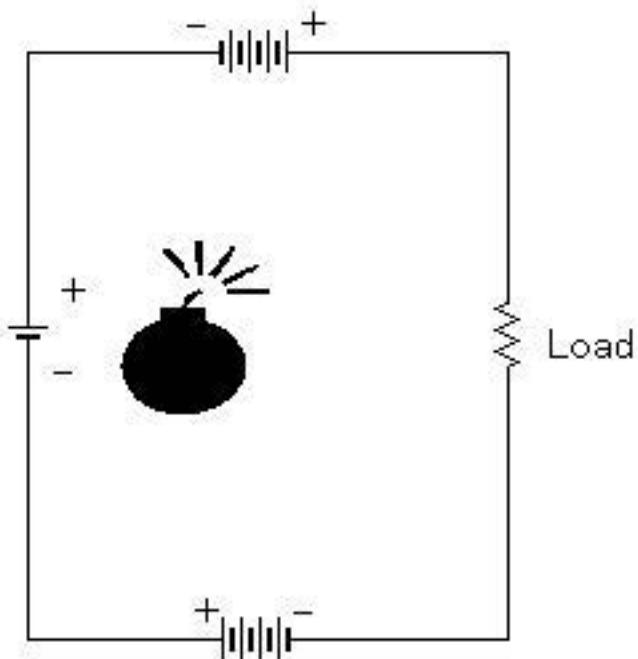
Finally, this battery is reverse
charged!



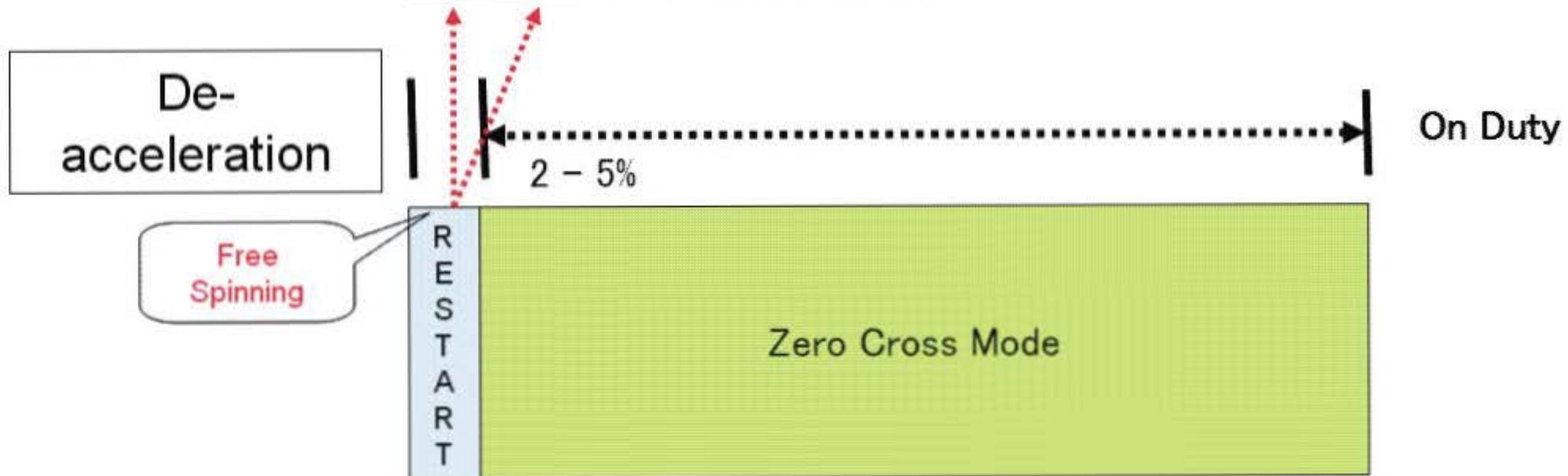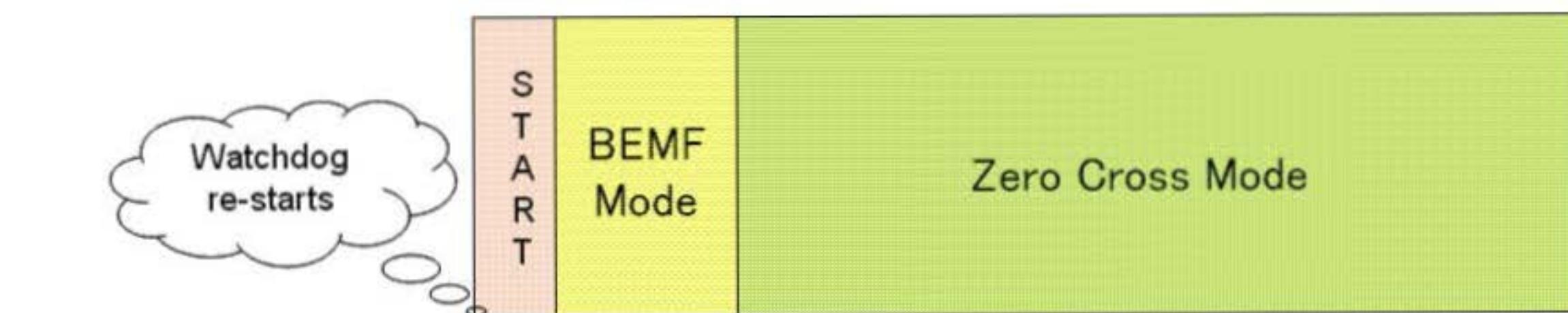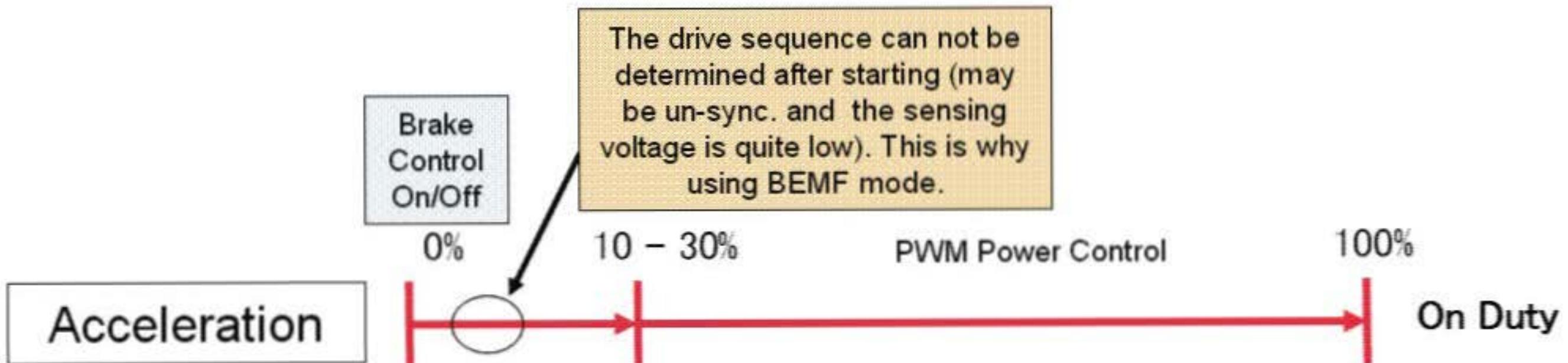

Control modes in BL-ESC

Propo. Rx Interface

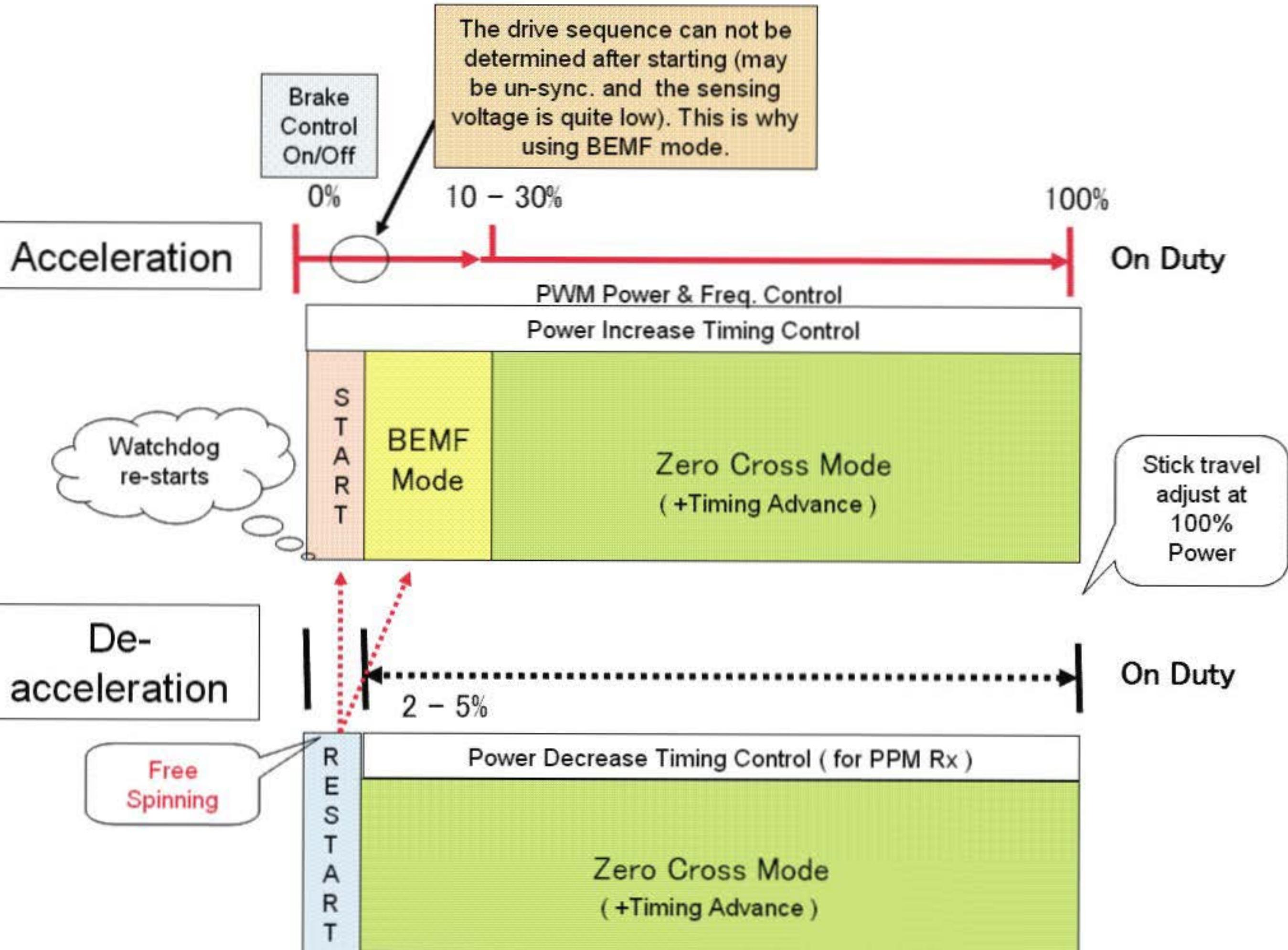

Control modes in BL-ESC

Propo. Rx Interface

For folding prop.

Brake Control On/Off

0%

The drive sequence can not be determined after starting (may be un-sync. and the sensing voltage is quite low). This is why using BEMF mode.

100% power setting control

100%

Acceleration



PWM Power & Freq. Control

Power Increase Timing Control

S T A R T

BEMF Mode

Zero Cross Mode
(+Timing Advance)

Watchdog re-starts

Stick travel adjust at 100% Power

De-acceleration

2 - 5%

Inverse logarithm power proportional control + Over current protection

On Duty

Free Spinning


R E S T A R T

Power Decrease Timing Control (for PPM Rx)


Zero Cross Mode
(+Timing Advance)


Control modes in BL-ESC

Propo. Rx Interface

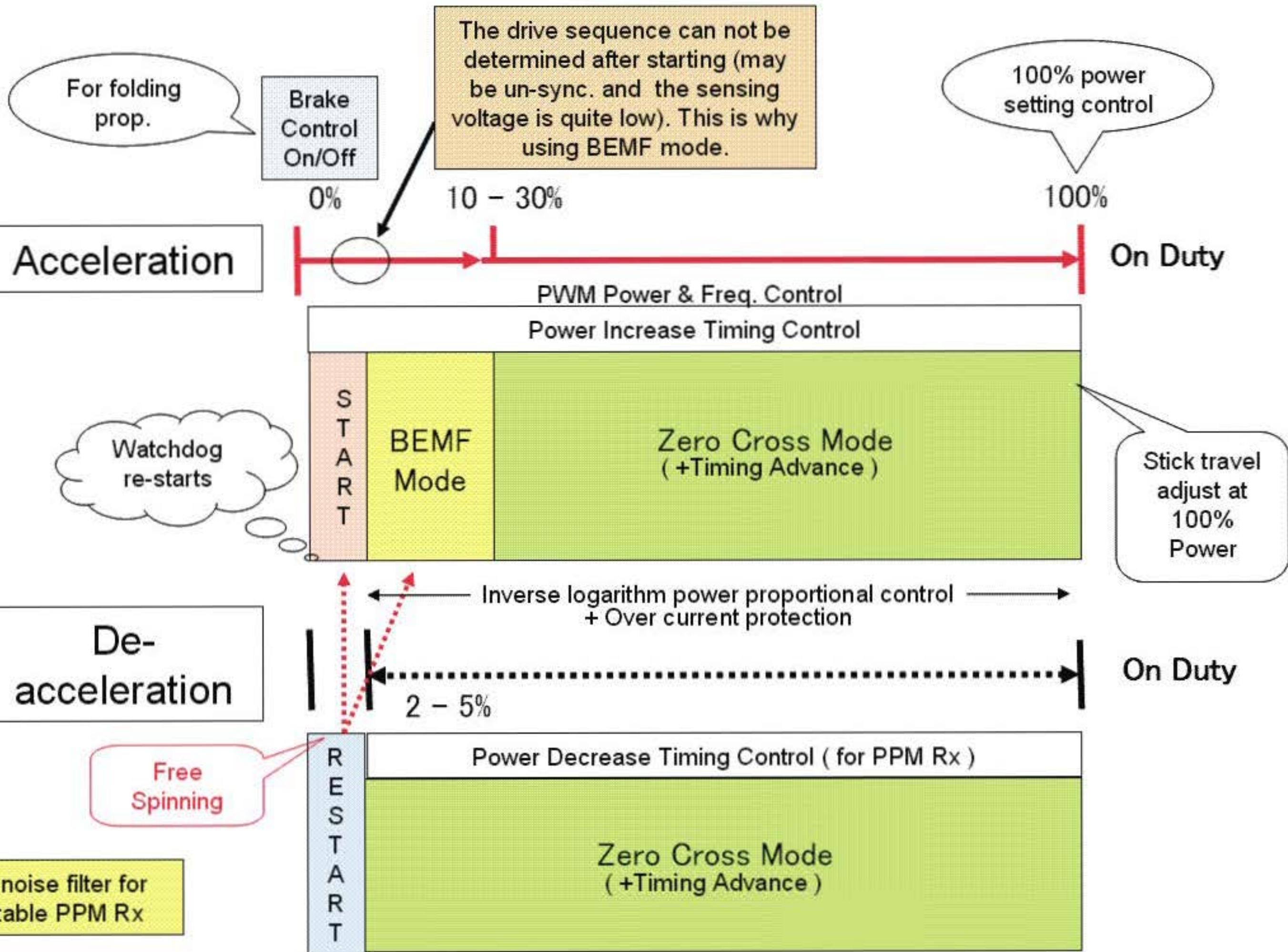


Control modes in BL-ESC

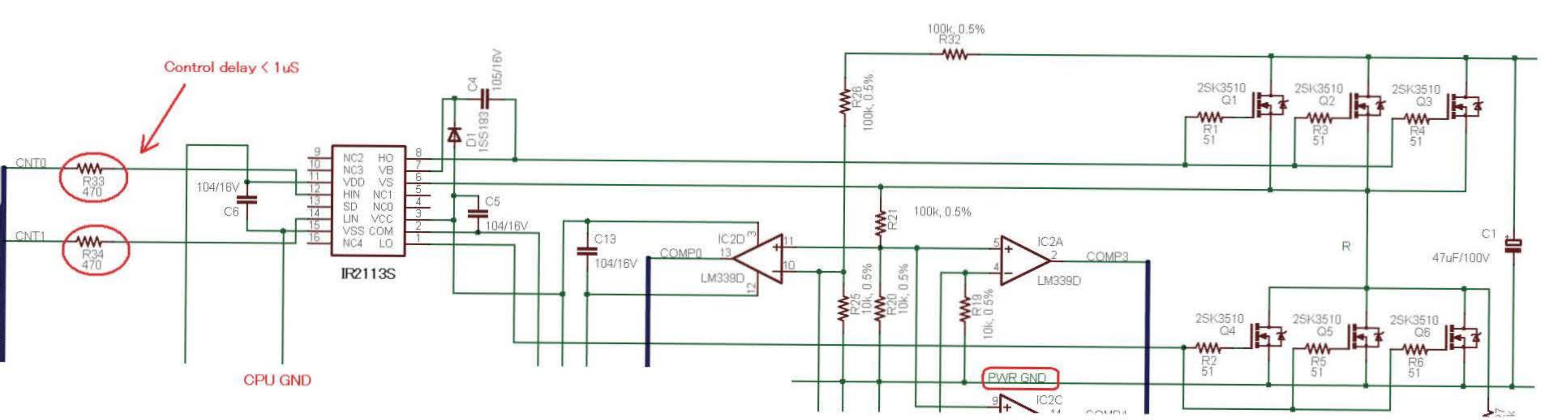

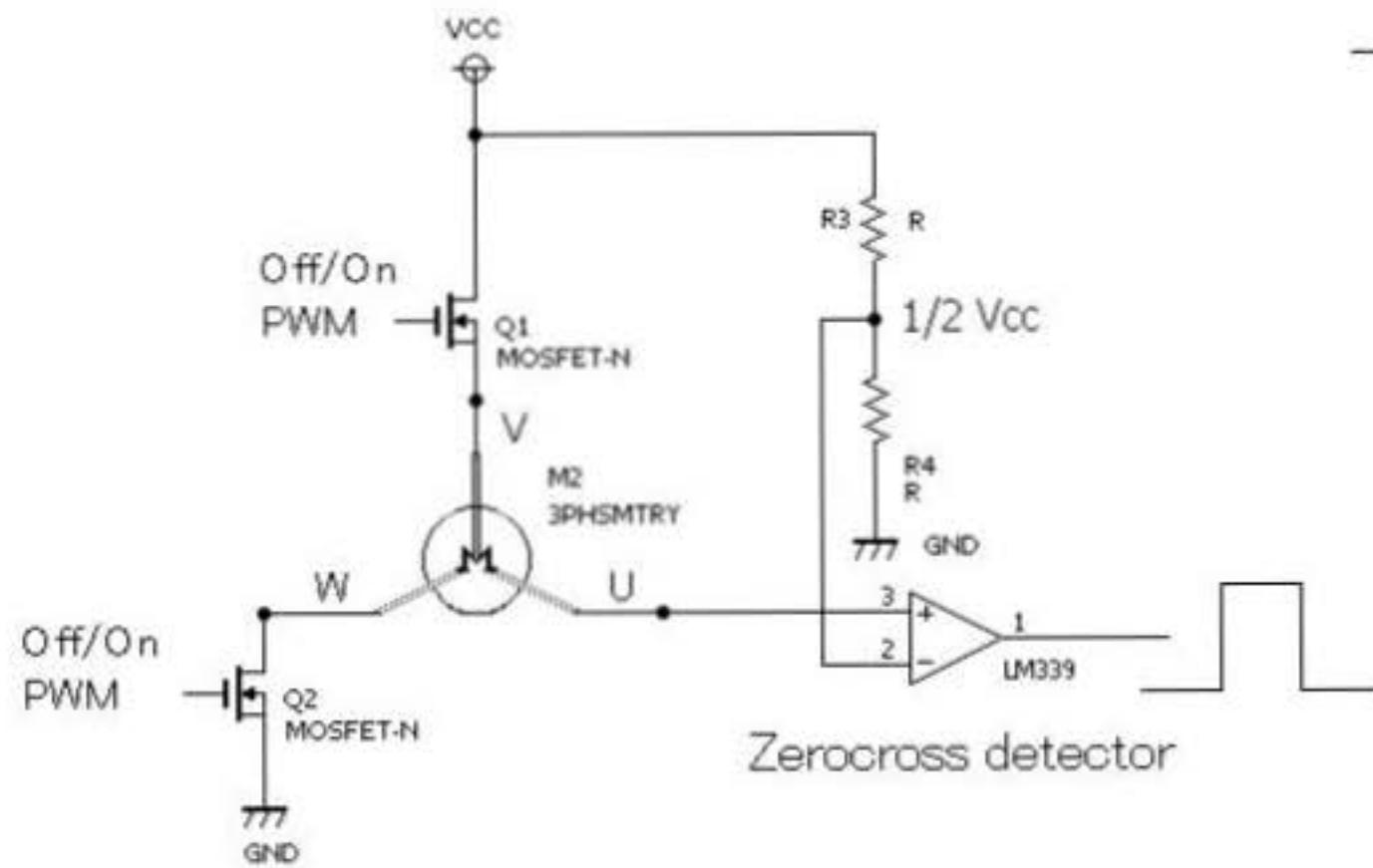

サンプリングタイミング

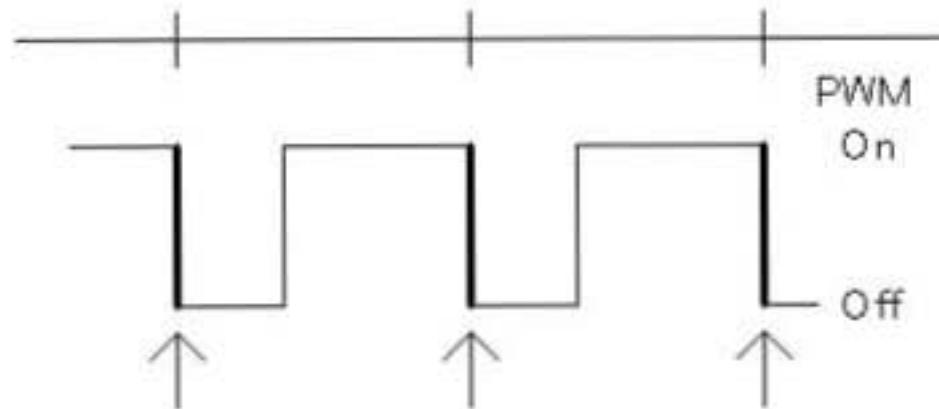

The Zerocross detection timing is just before PWM off as PWM on rear edge. Also, "Full On" 100% power PWM rear edge timing. This timing does not cause any transient noise problem. And C8051Fxxx's comparator can be hysteresis level and response timing by software.



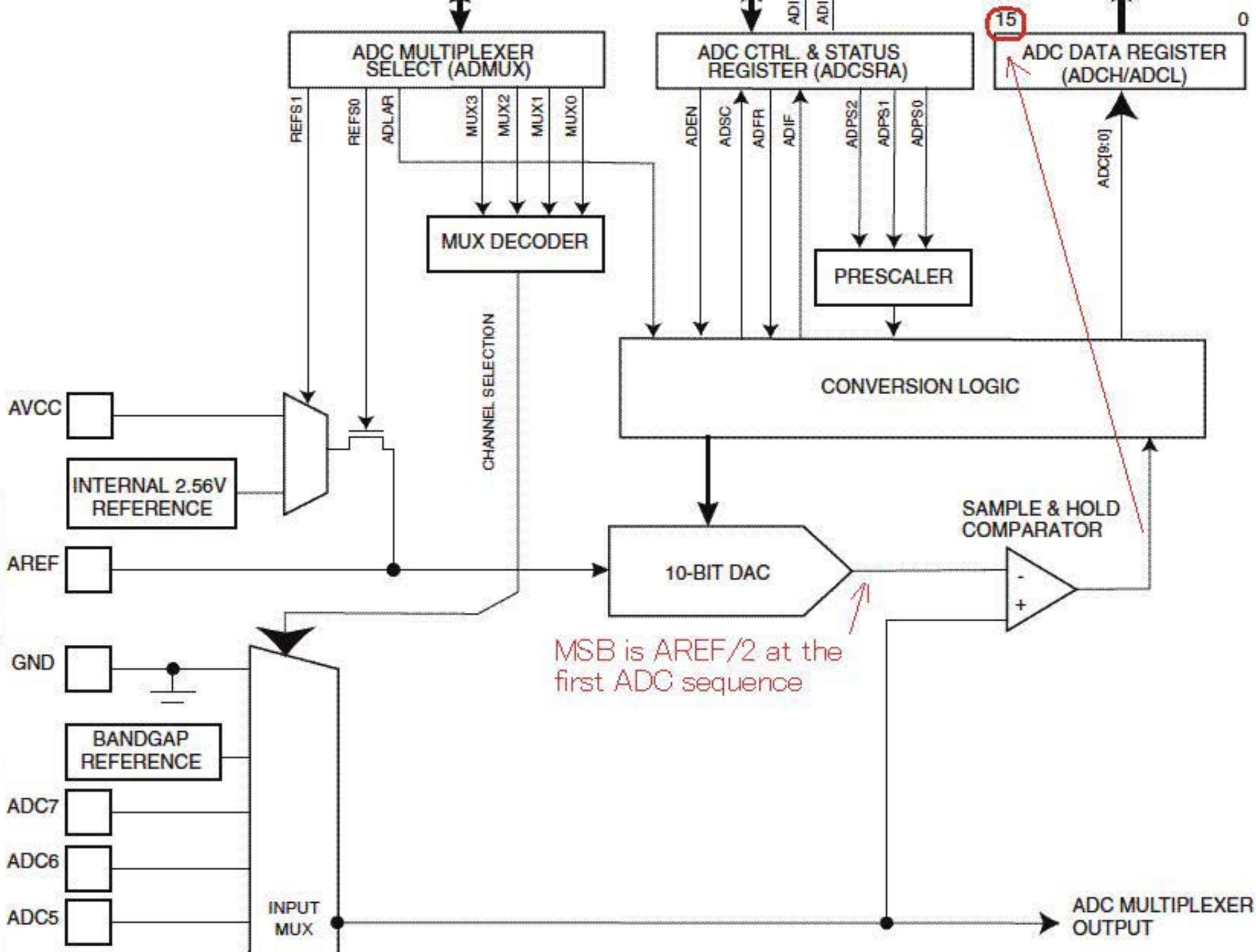
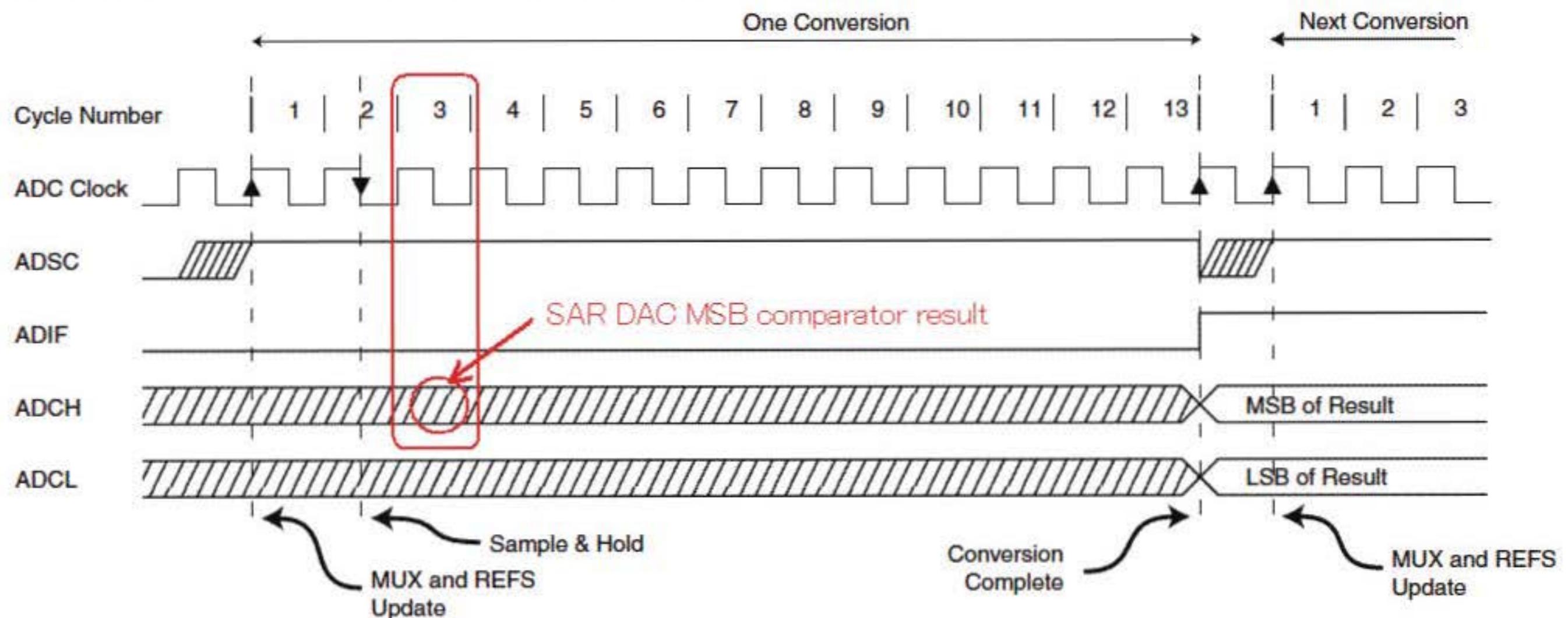


Figure 93. ADC Timing Diagram, Single Conversion


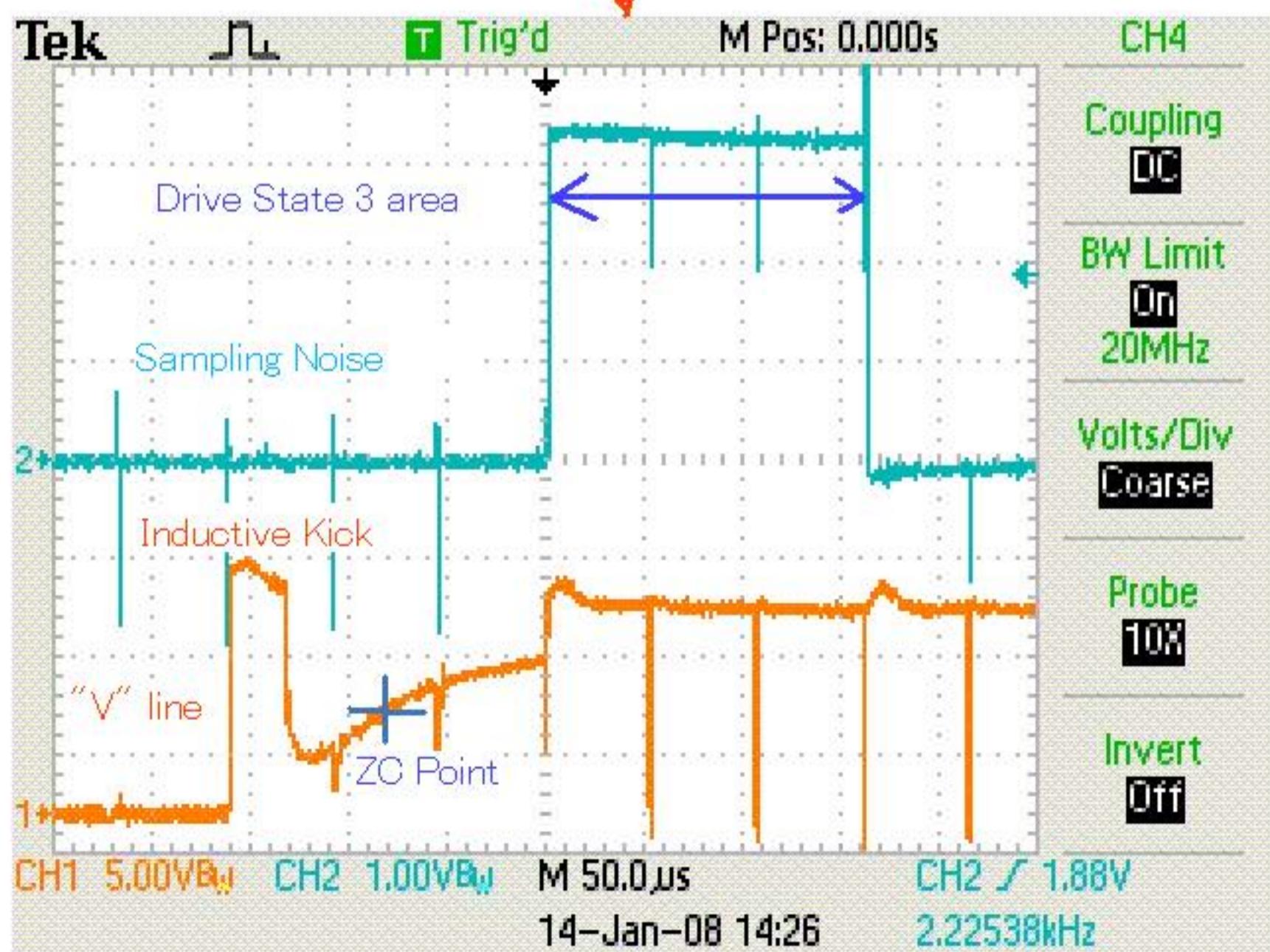


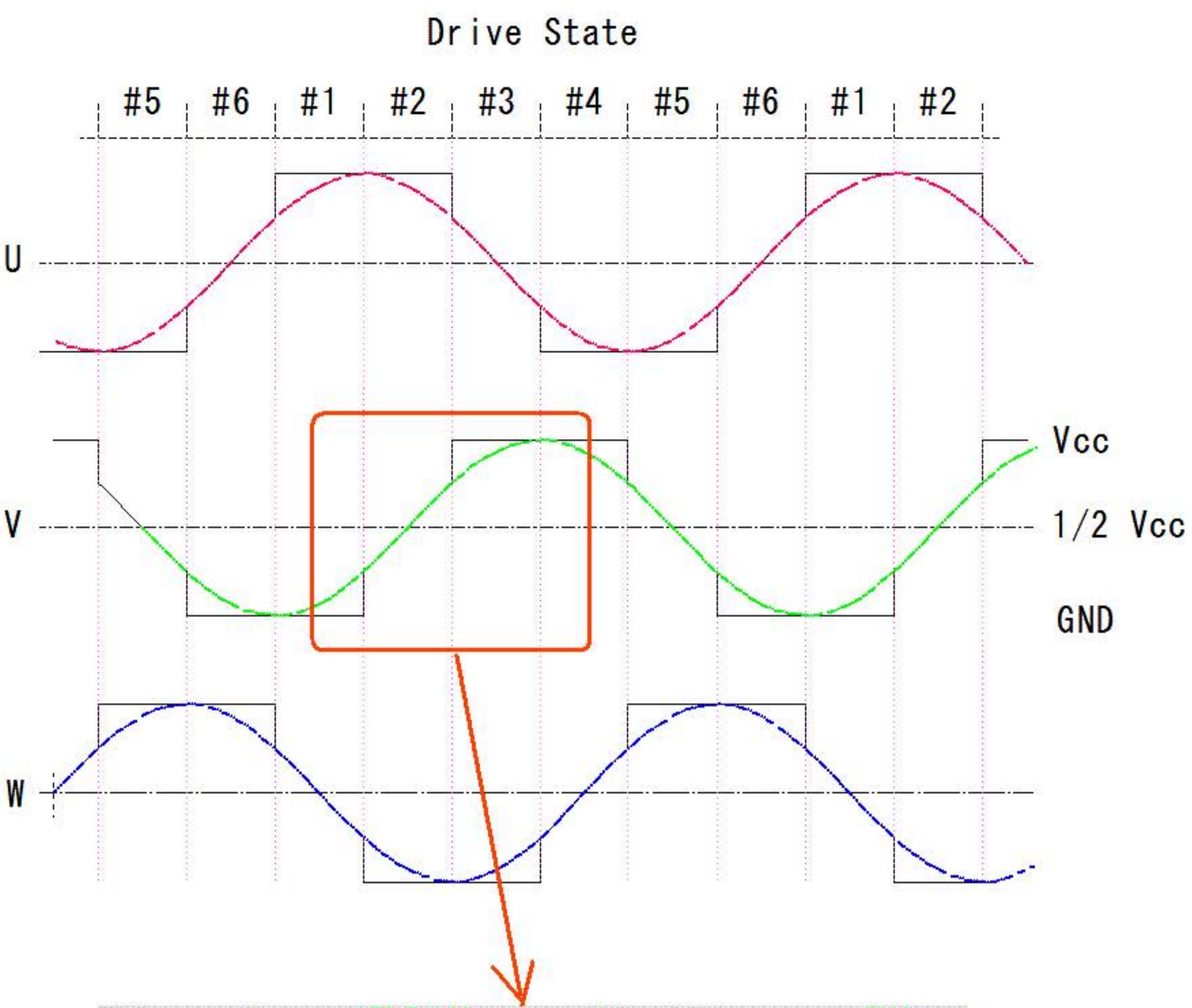



→ 10,000 rpm ←

9 stator, 12 magnets
motor.


Figure 89. Analog Comparator Block Diagram⁽²⁾

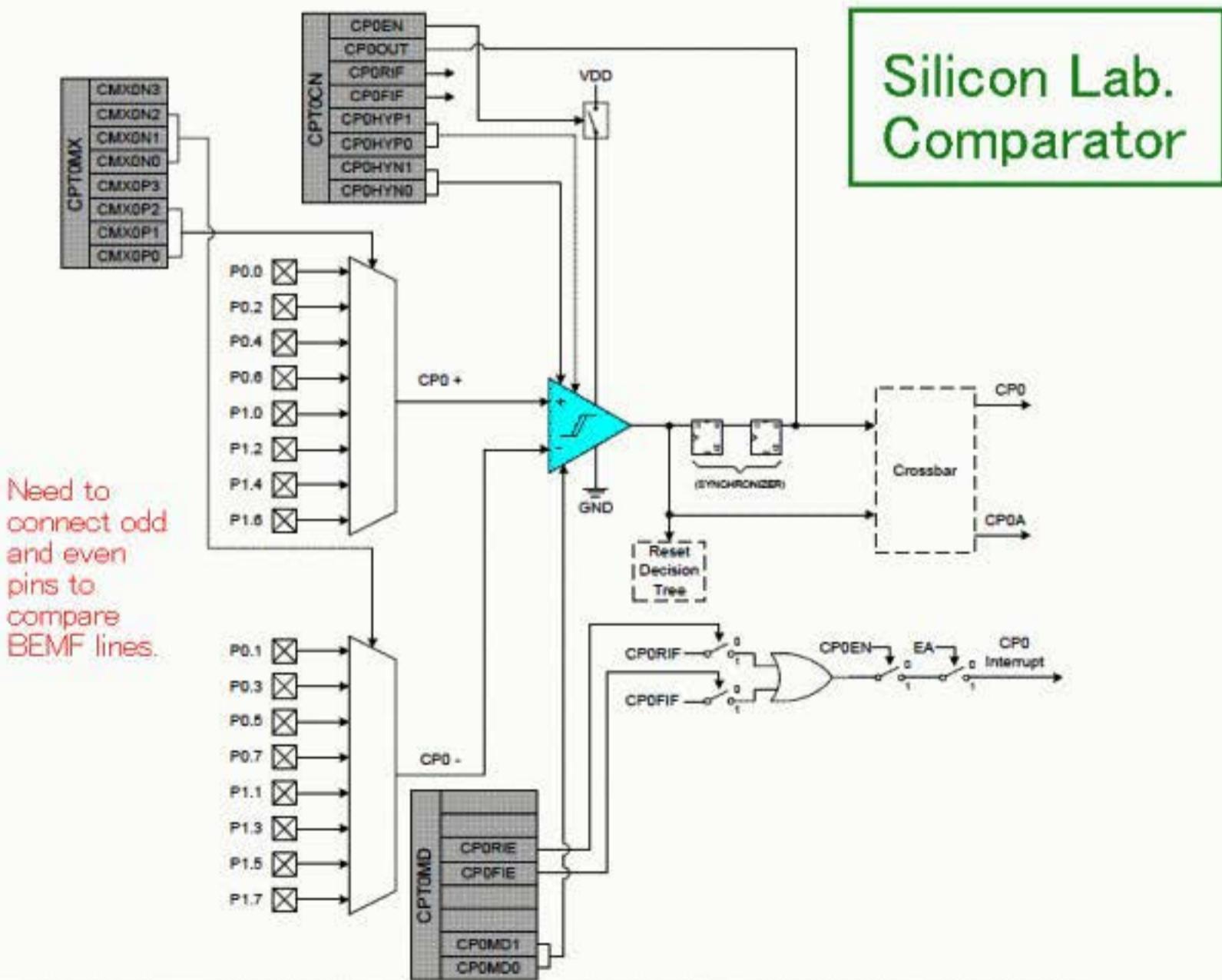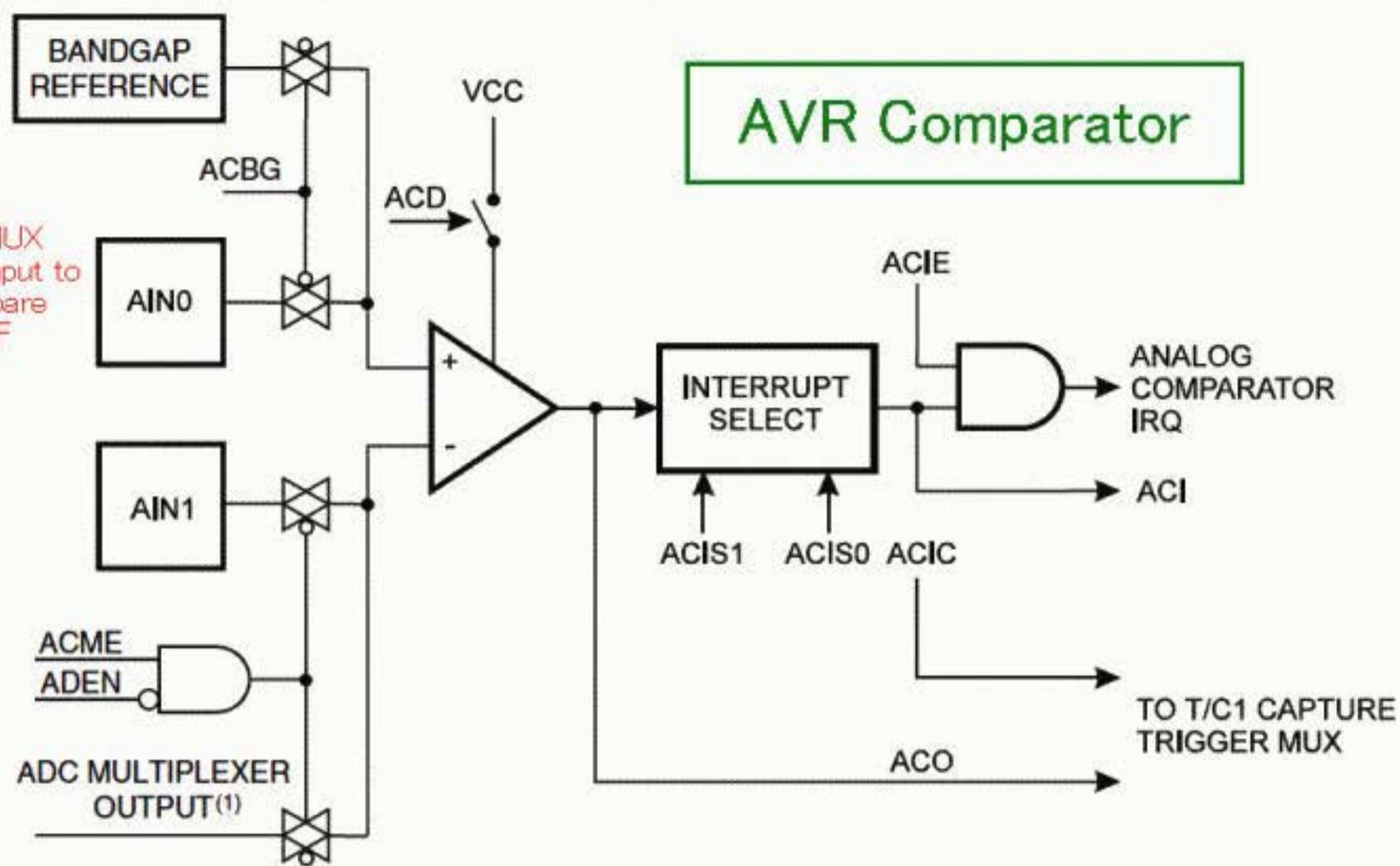

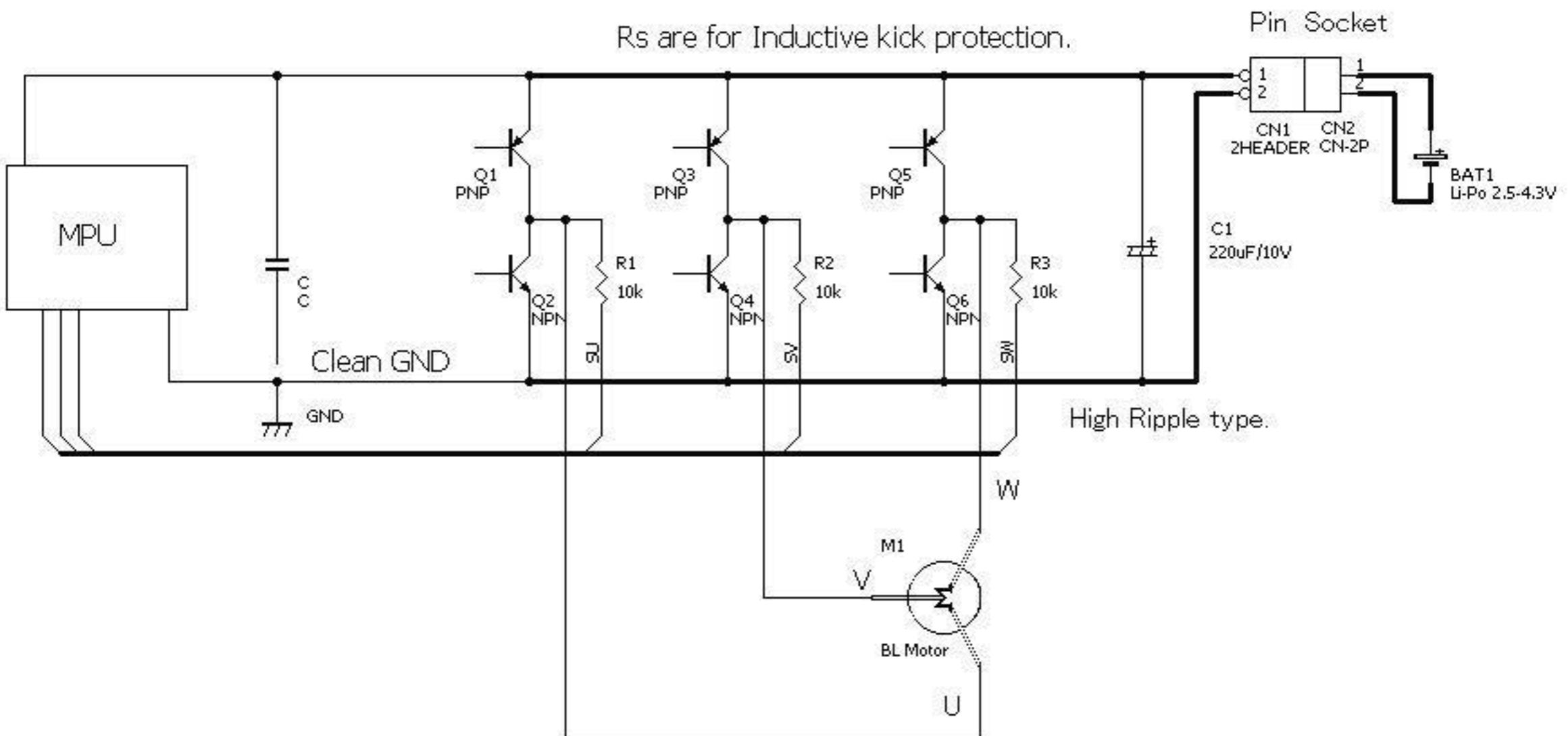

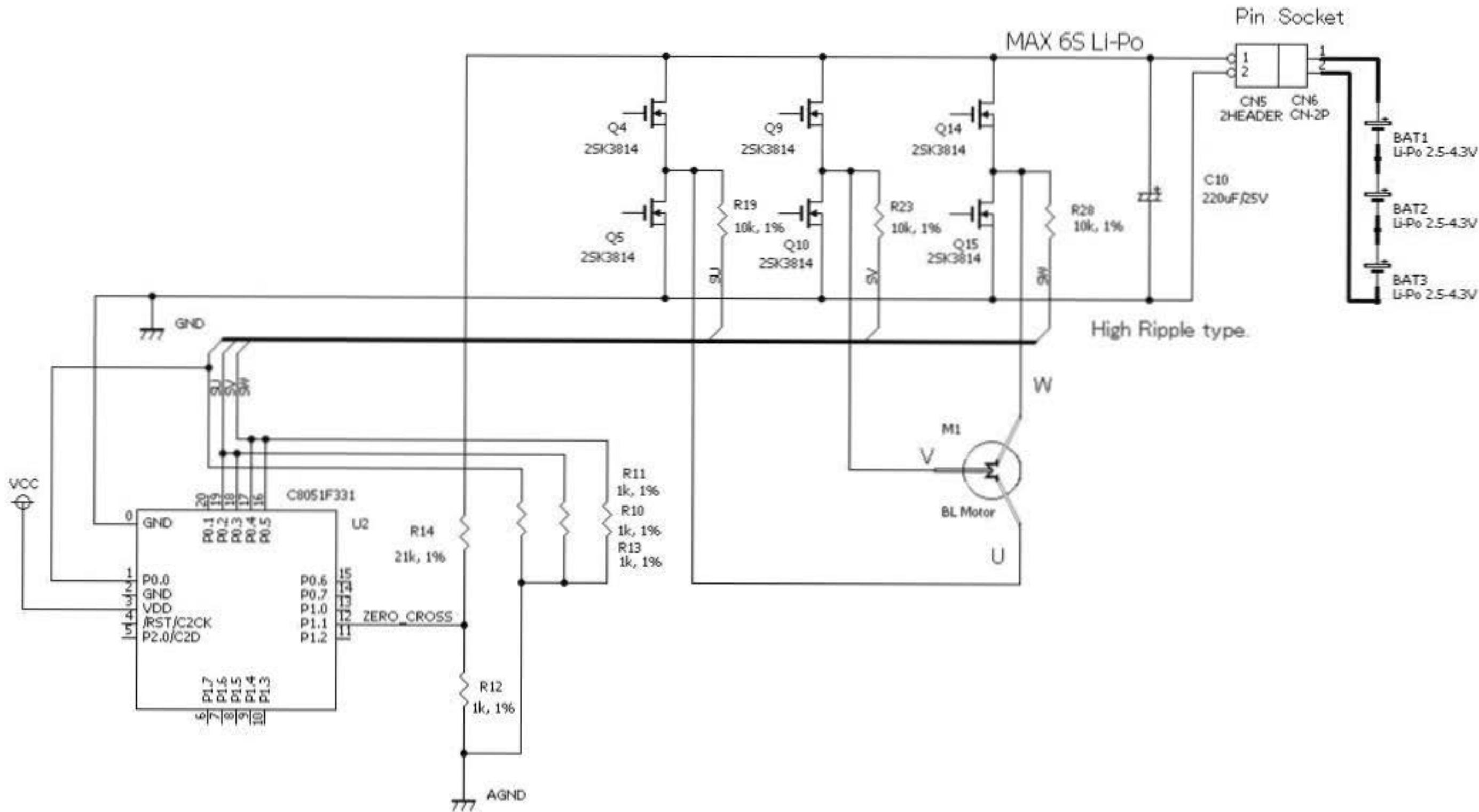

Inductive Kick Path (Charge up C1&V1)

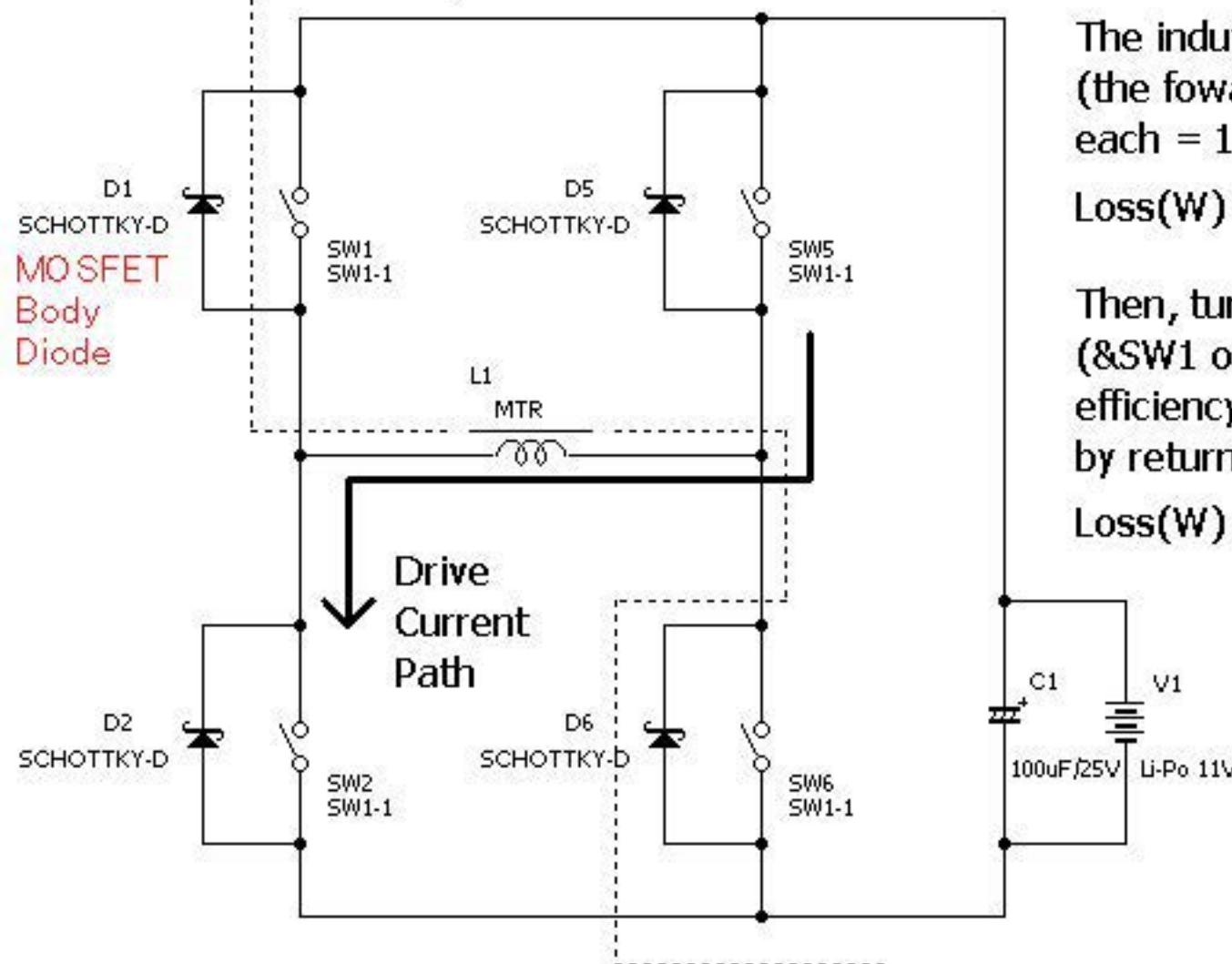


The inductive kick heats up D1&D6 (the forward voltage drop loss is about 0.6V each = 1.2V) just after SW2&SW5 PWM turn-off.


$$\text{Loss(W)} = 1.2V \times \text{Kick current}$$


Then, turn-on SW1 on(& SW6 off) or SW6 on (&SW1 off) at PWM-off to get more power efficiency(only one diode voltage drop = 0.6V) by returning the inductive kick energy to C1&V1.

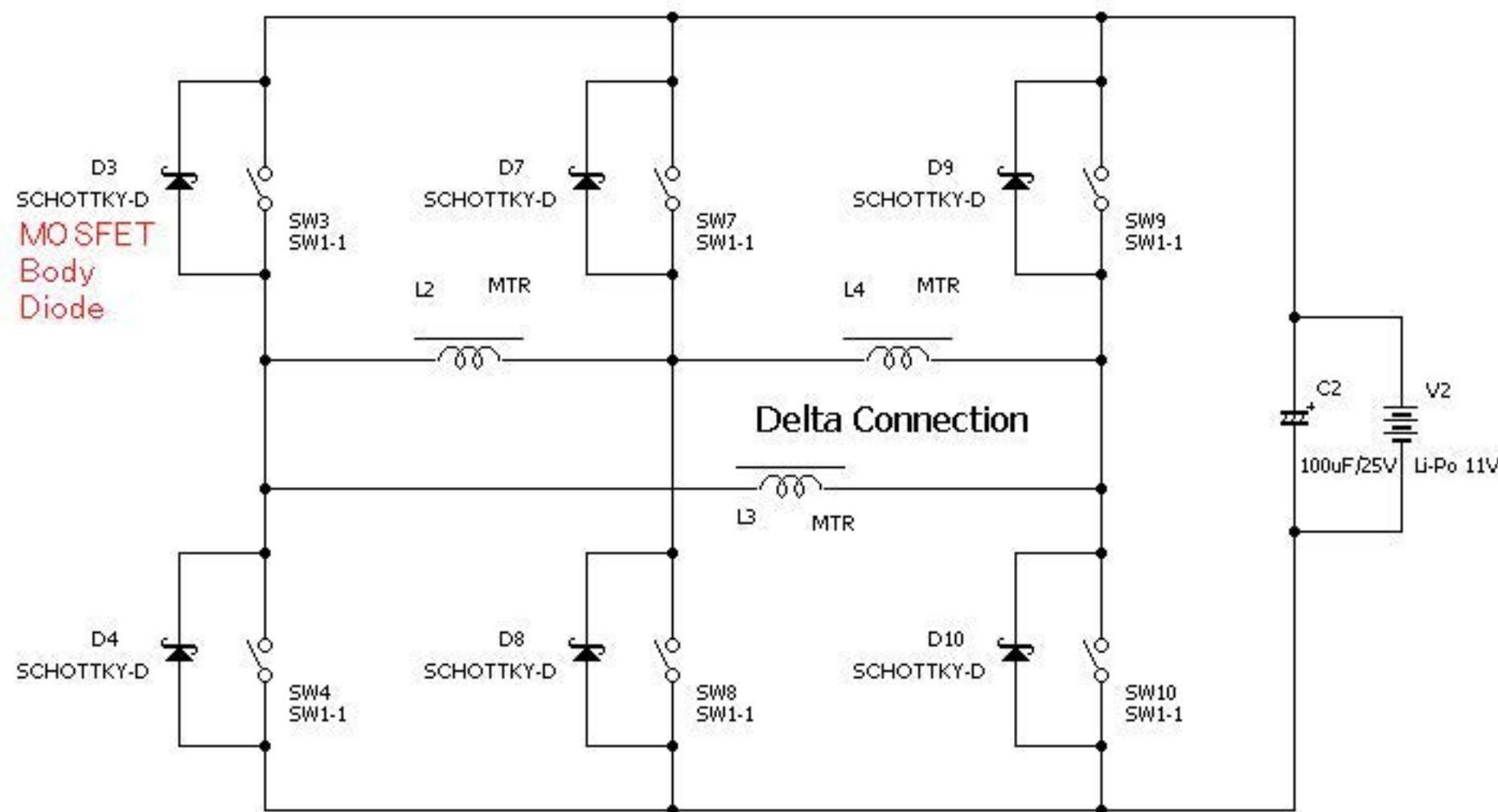
$$\text{Loss(W)} = 0.6V \times \text{Kick current}$$





Murata CSTCR4M0G53-B0

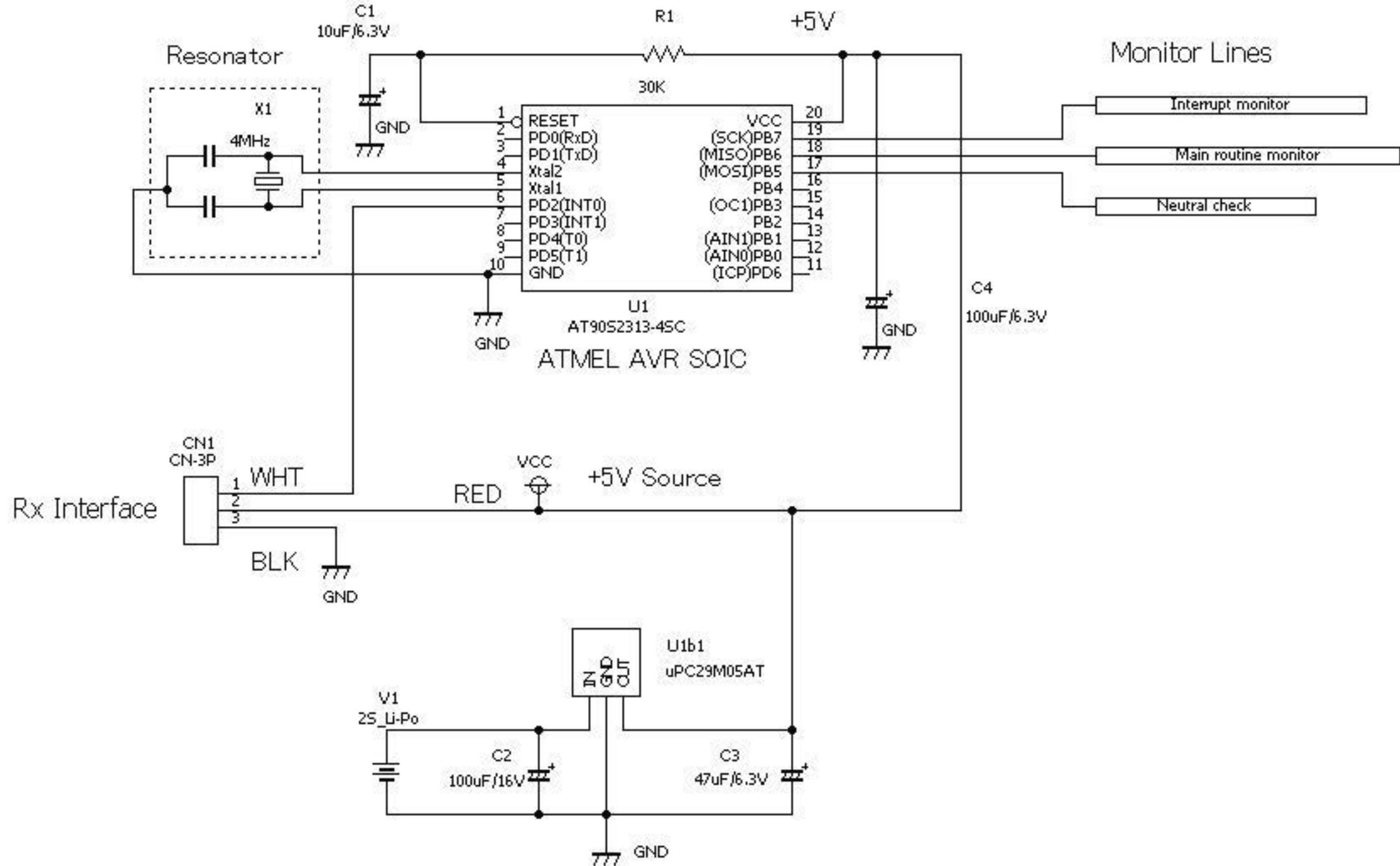


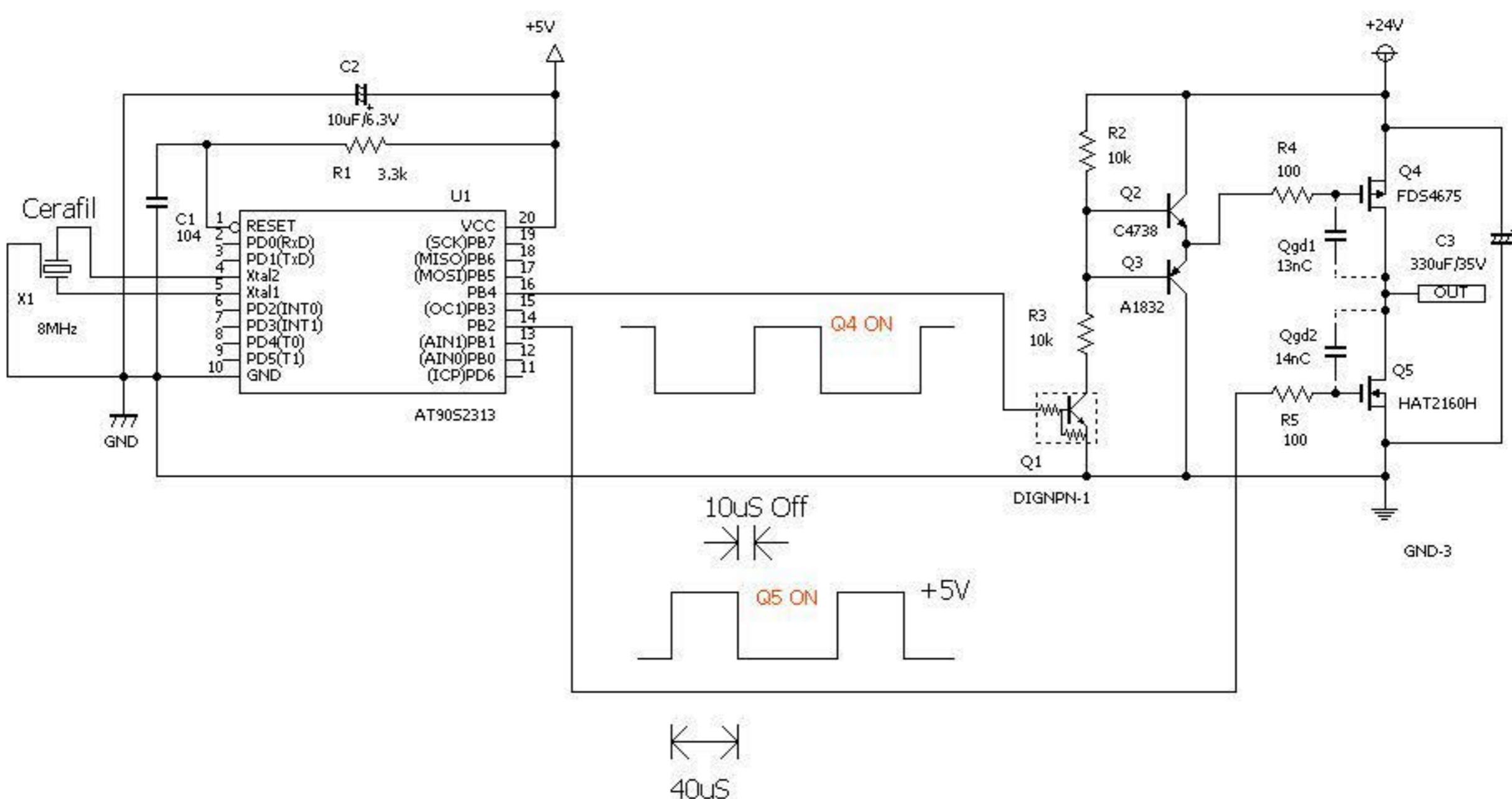

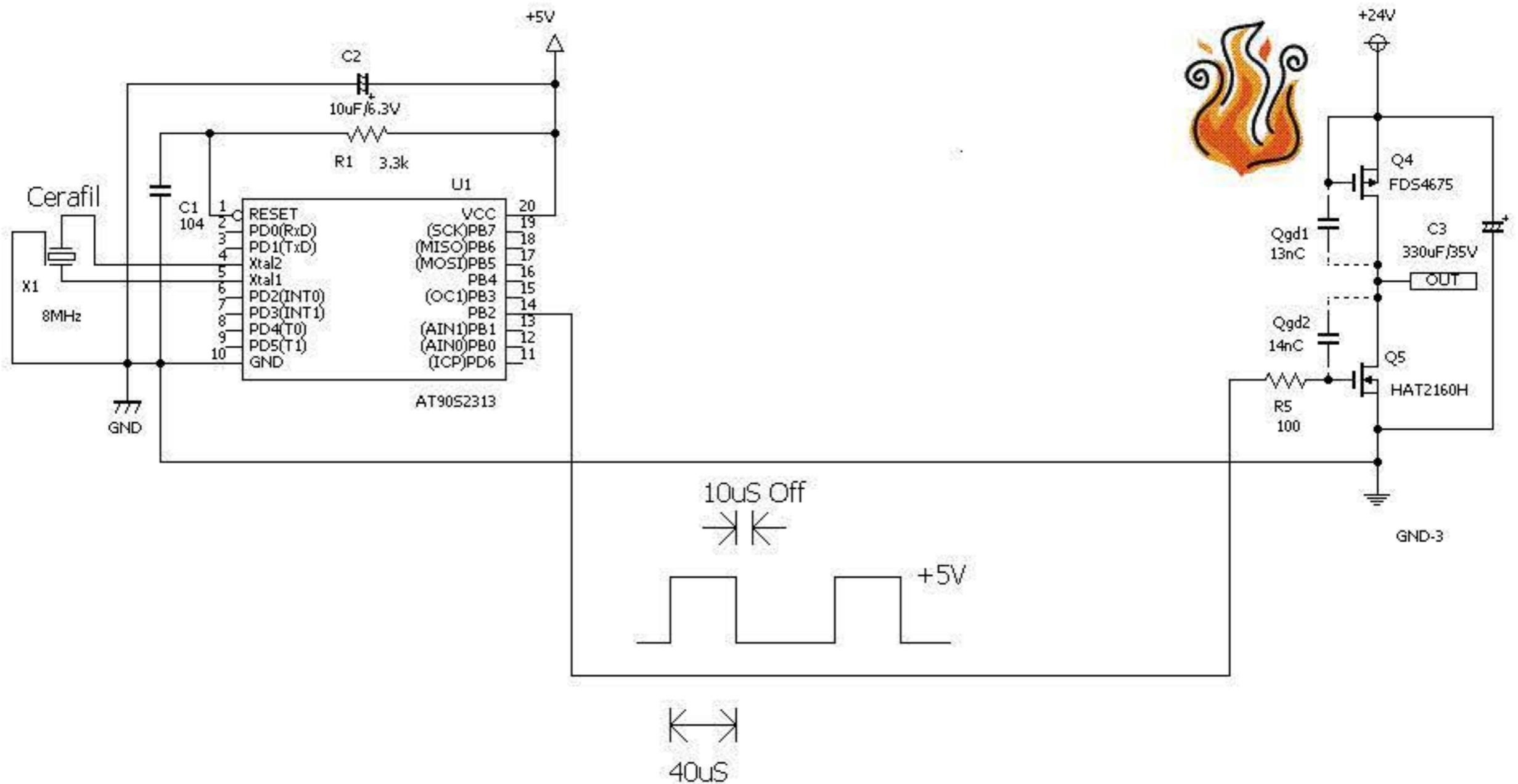

C3: Very Low ESR Cap.

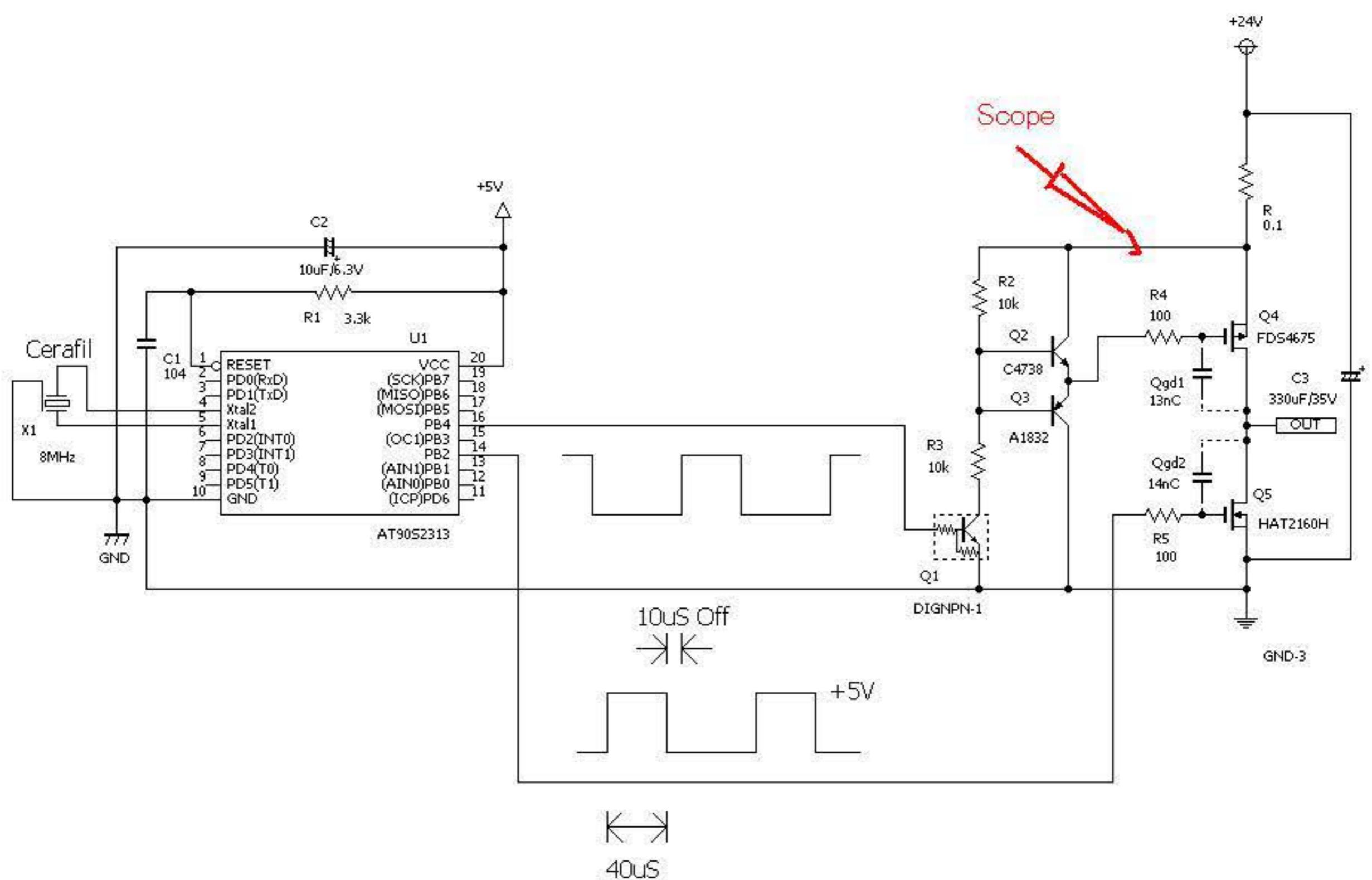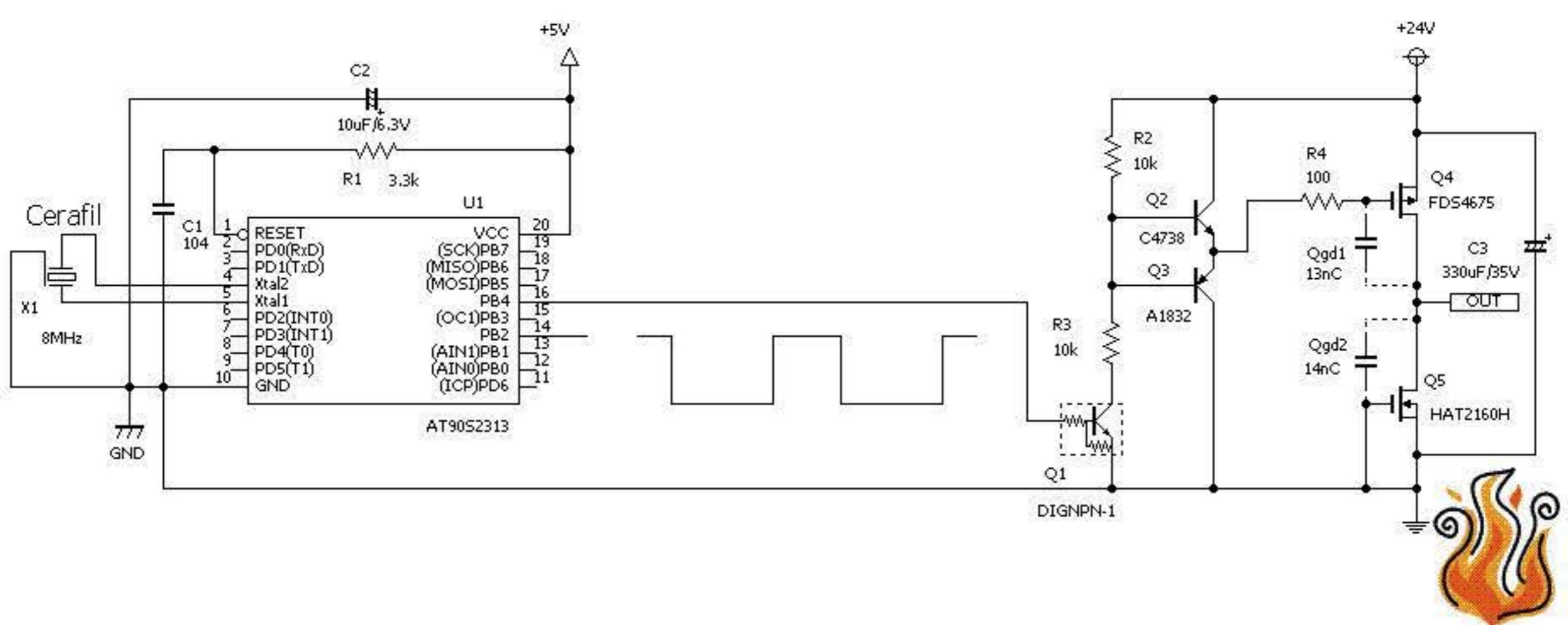

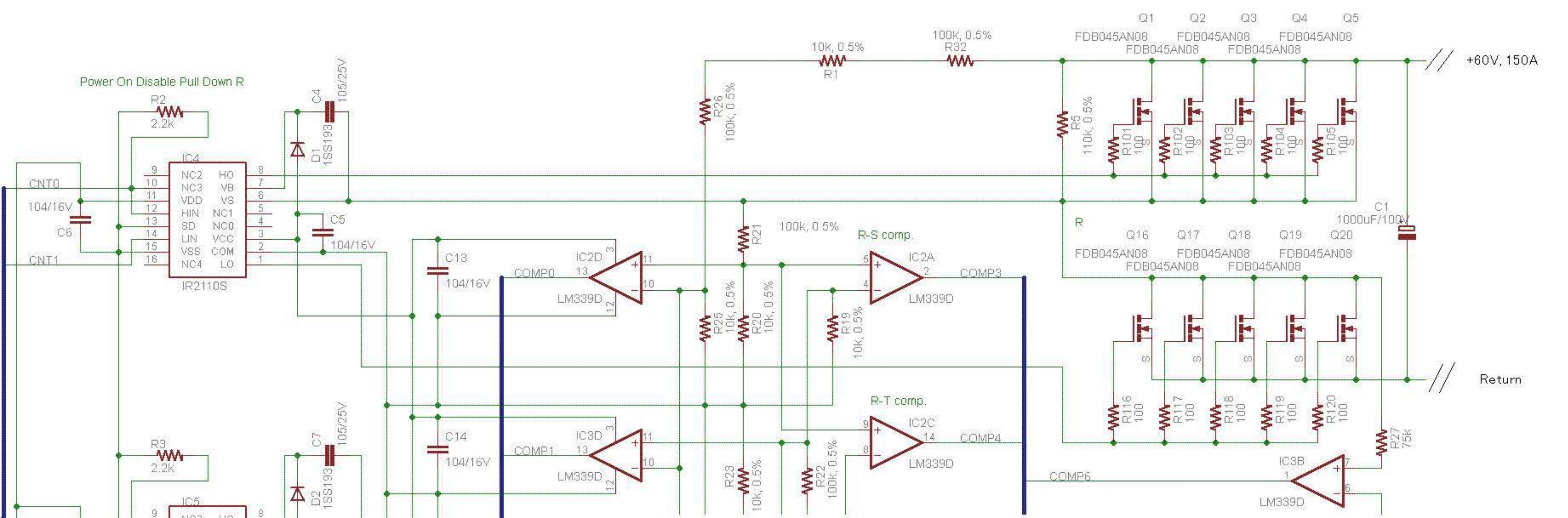

Tek

fl.

● Stop

M Pos: 0.000s

CH1

Coupling

DC

BW Limit

Off

100MHz

Volts/Div

Coarse

Probe

10X

Invert

Off


CH1 5.00V


M 250 μ s


CH1 / 1.20V

8-Oct-08 22:10


<10Hz

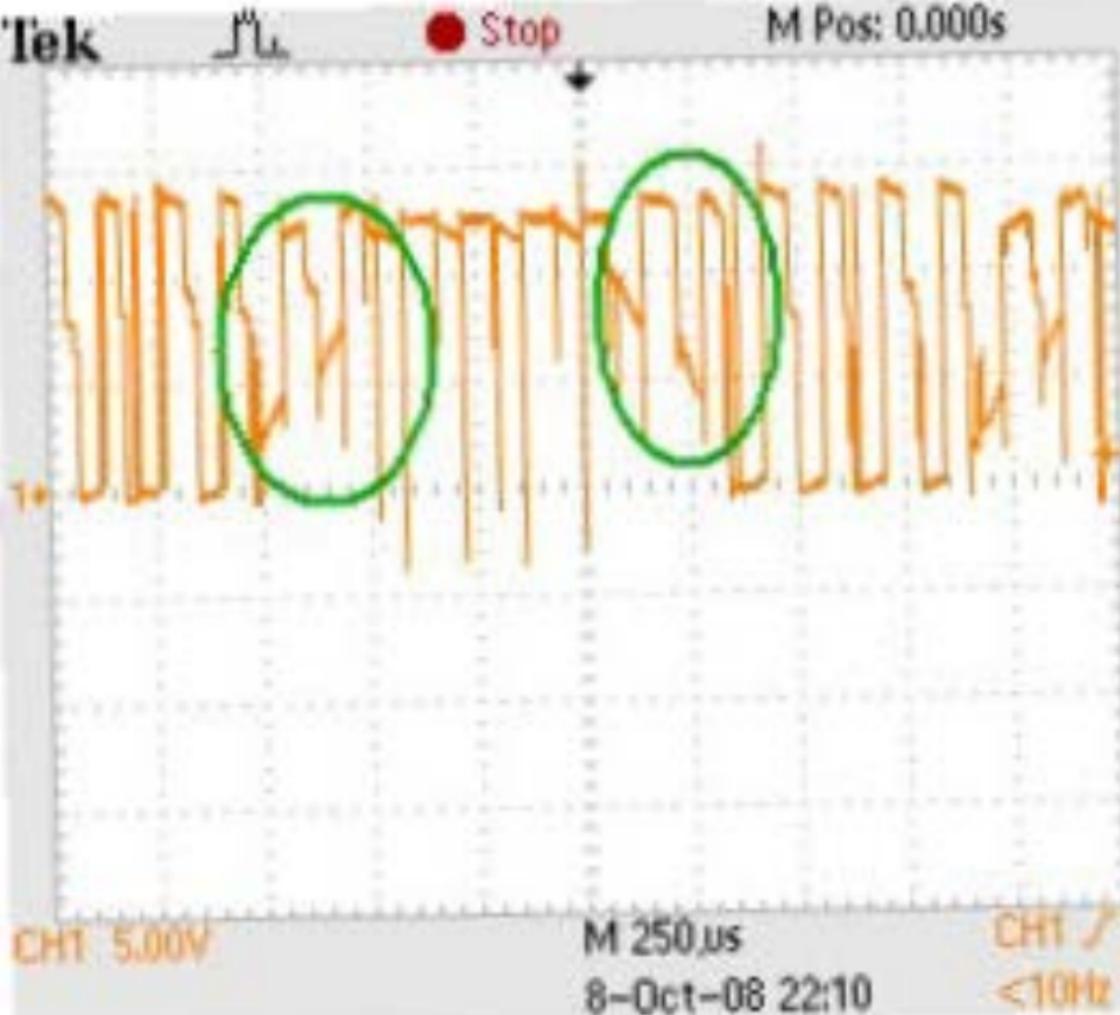


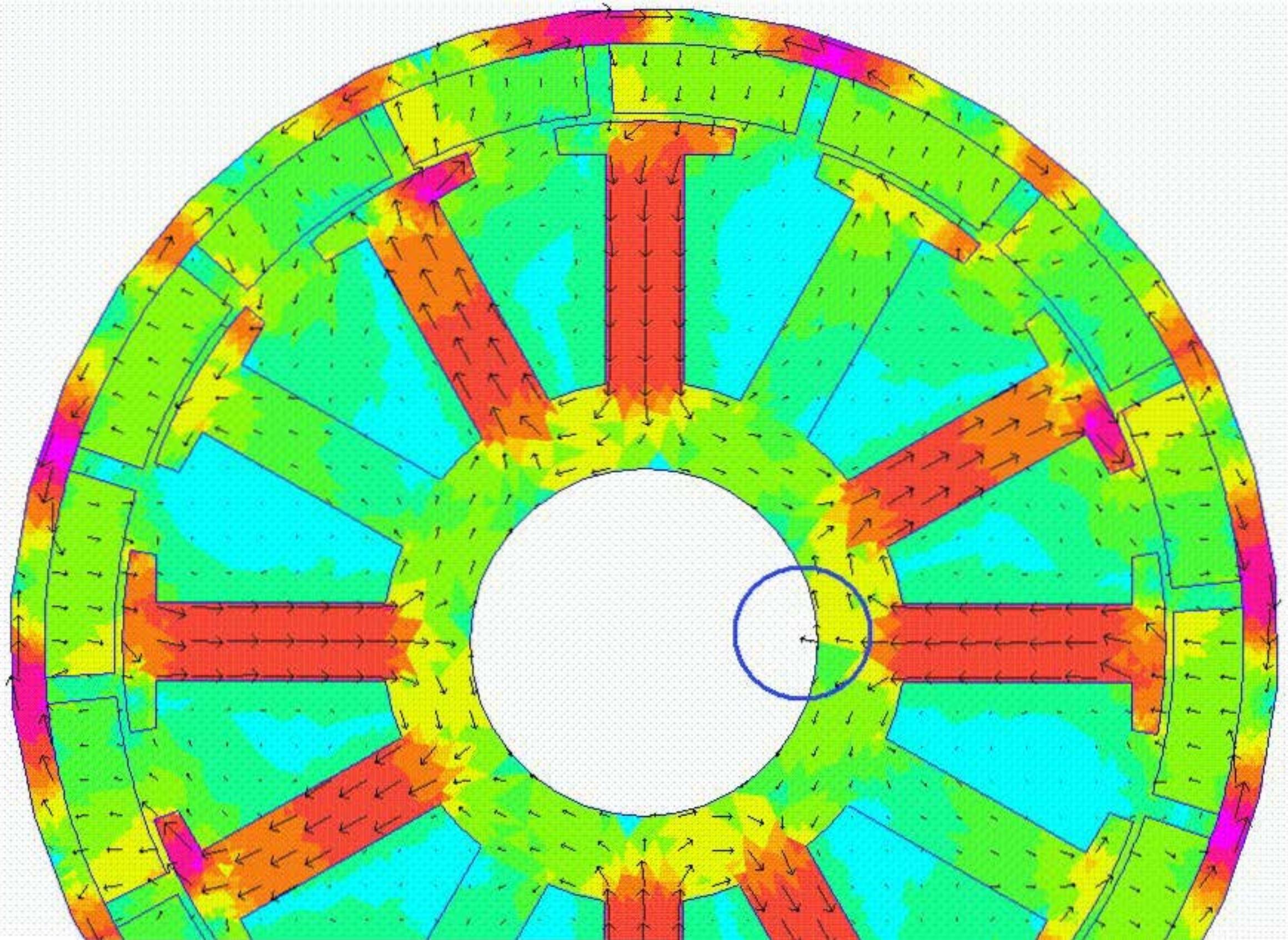

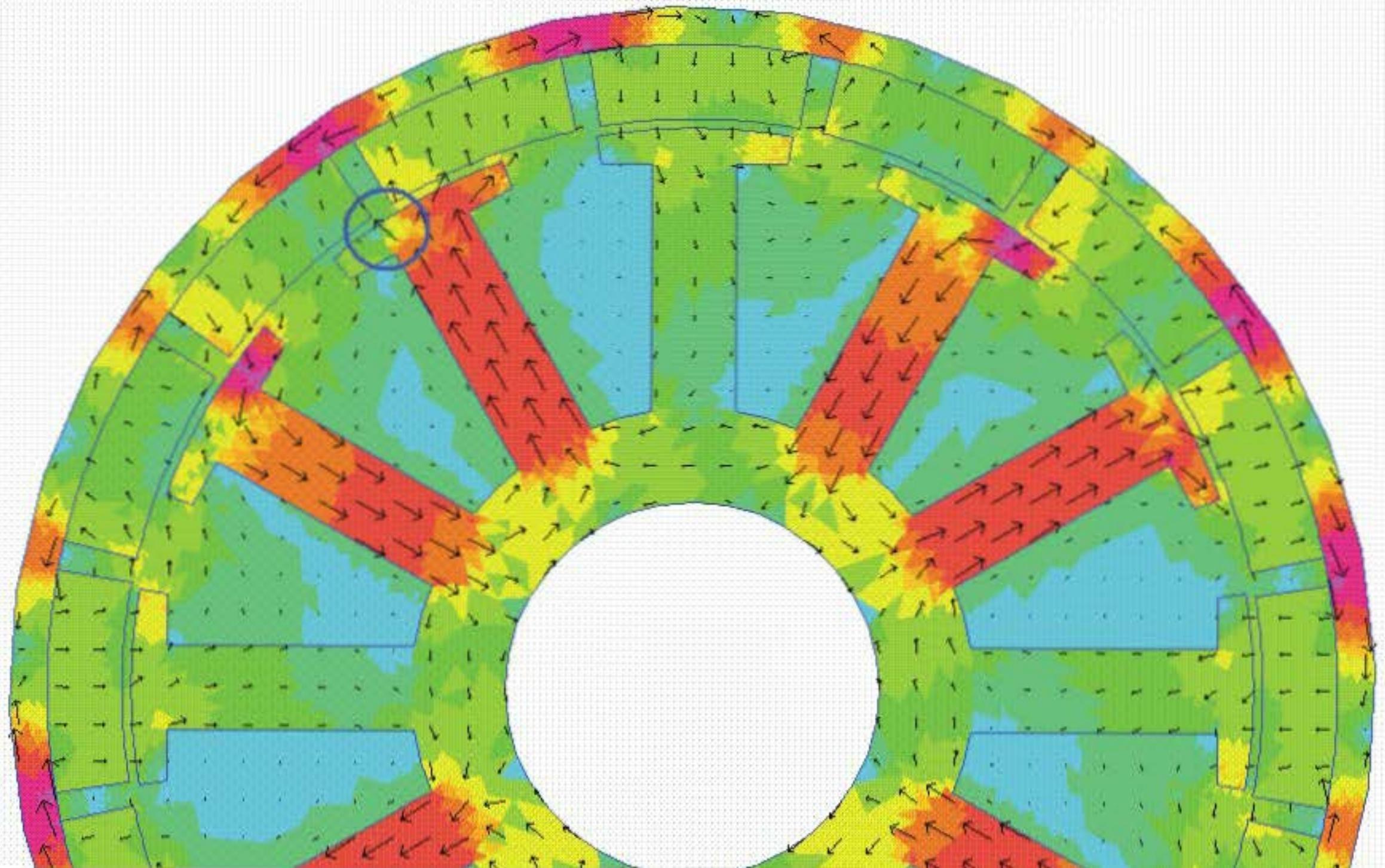

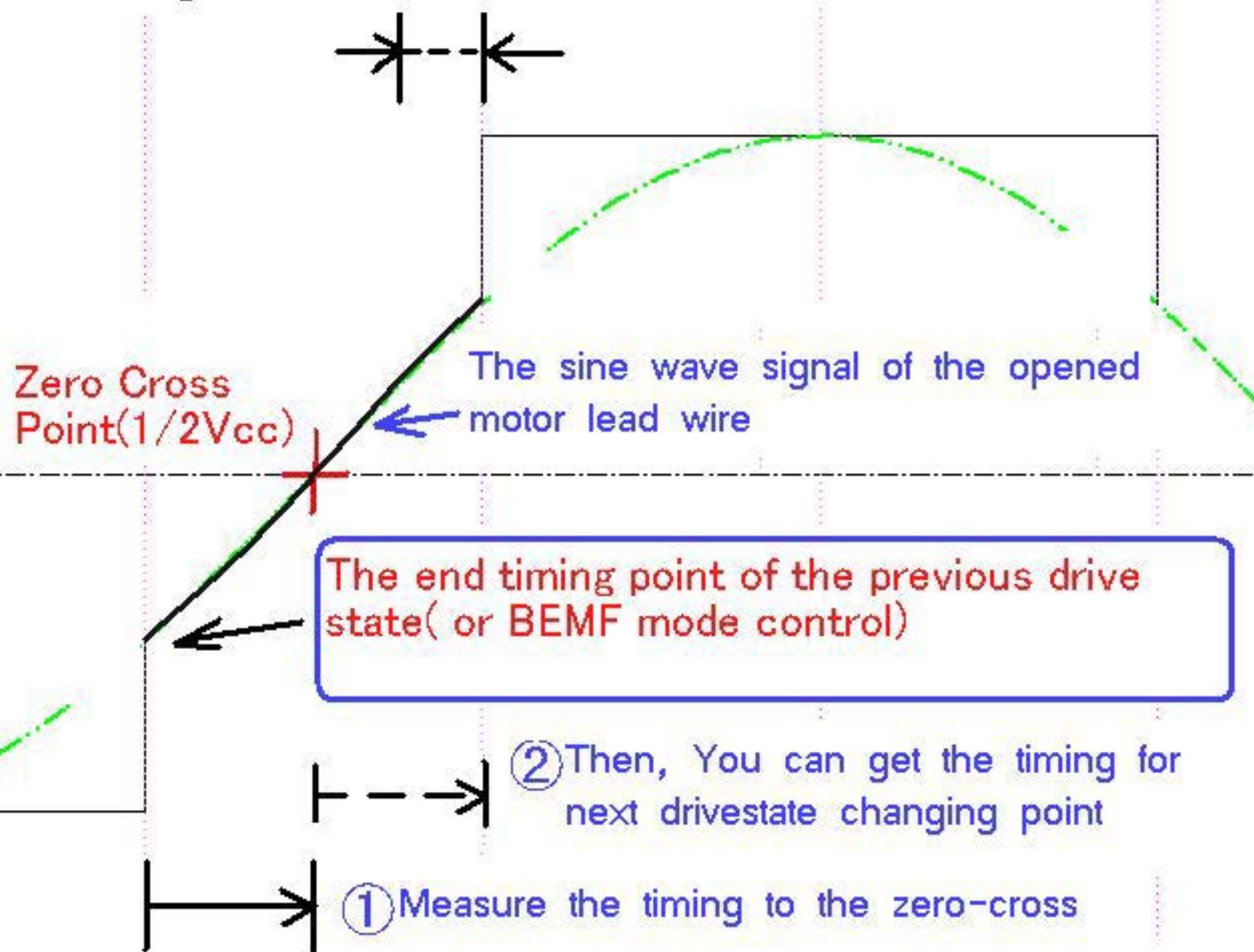
Reduce the timing by software for the timing advance



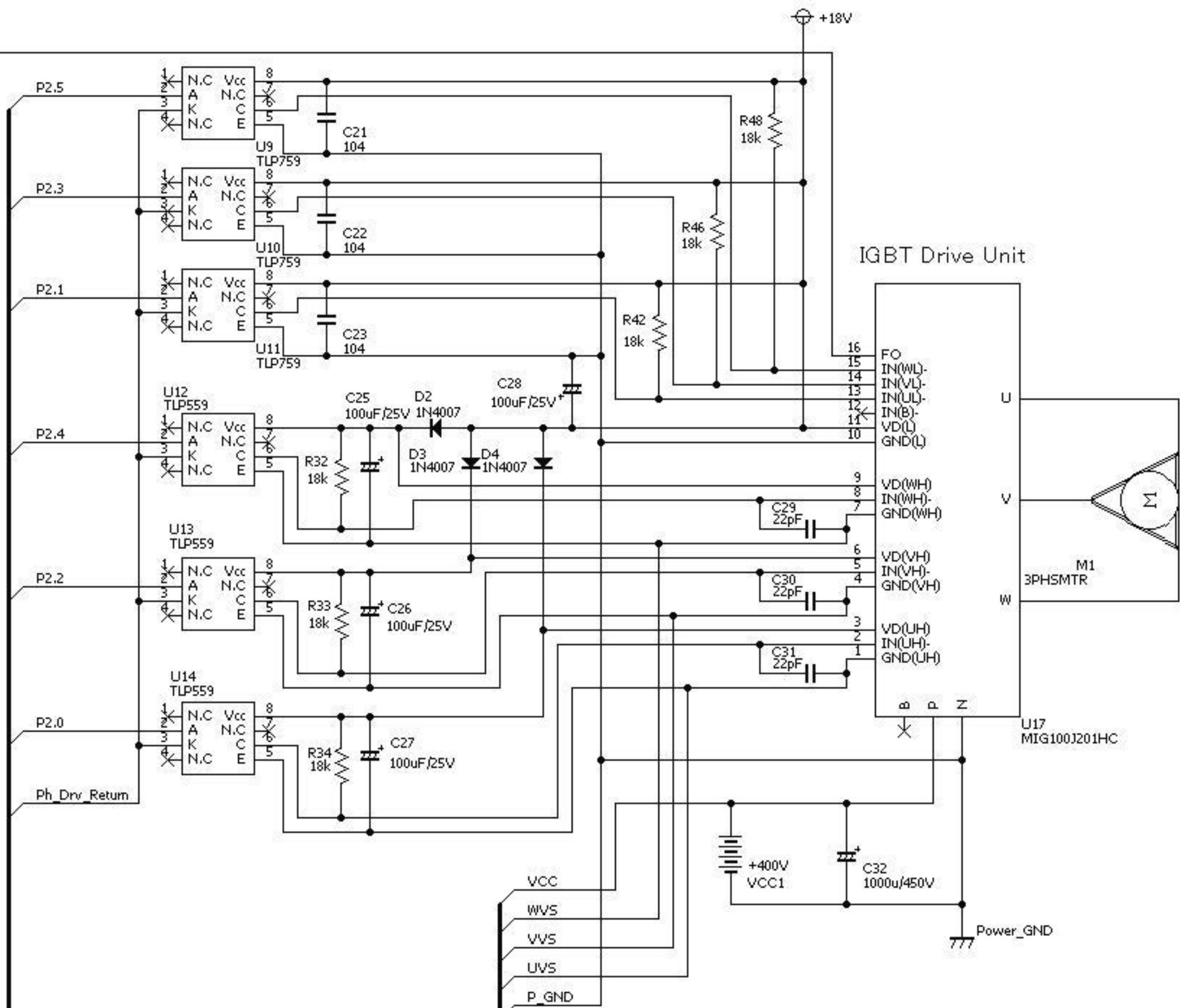

High Voltage Lines

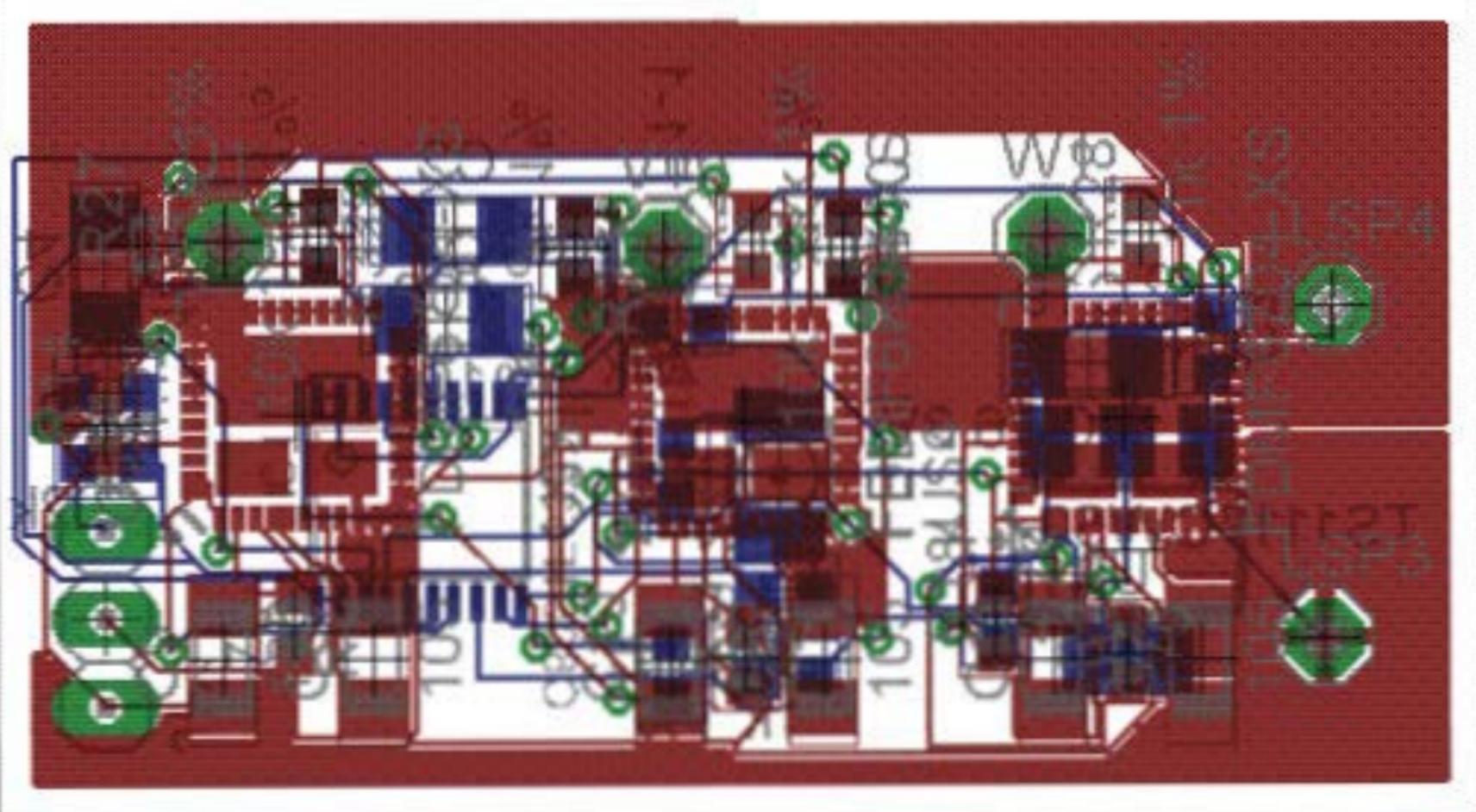Caution! the PCB isolation for BEMF sensing




Tek

In

T Trig'd

M Pos: 0.000s

CH1

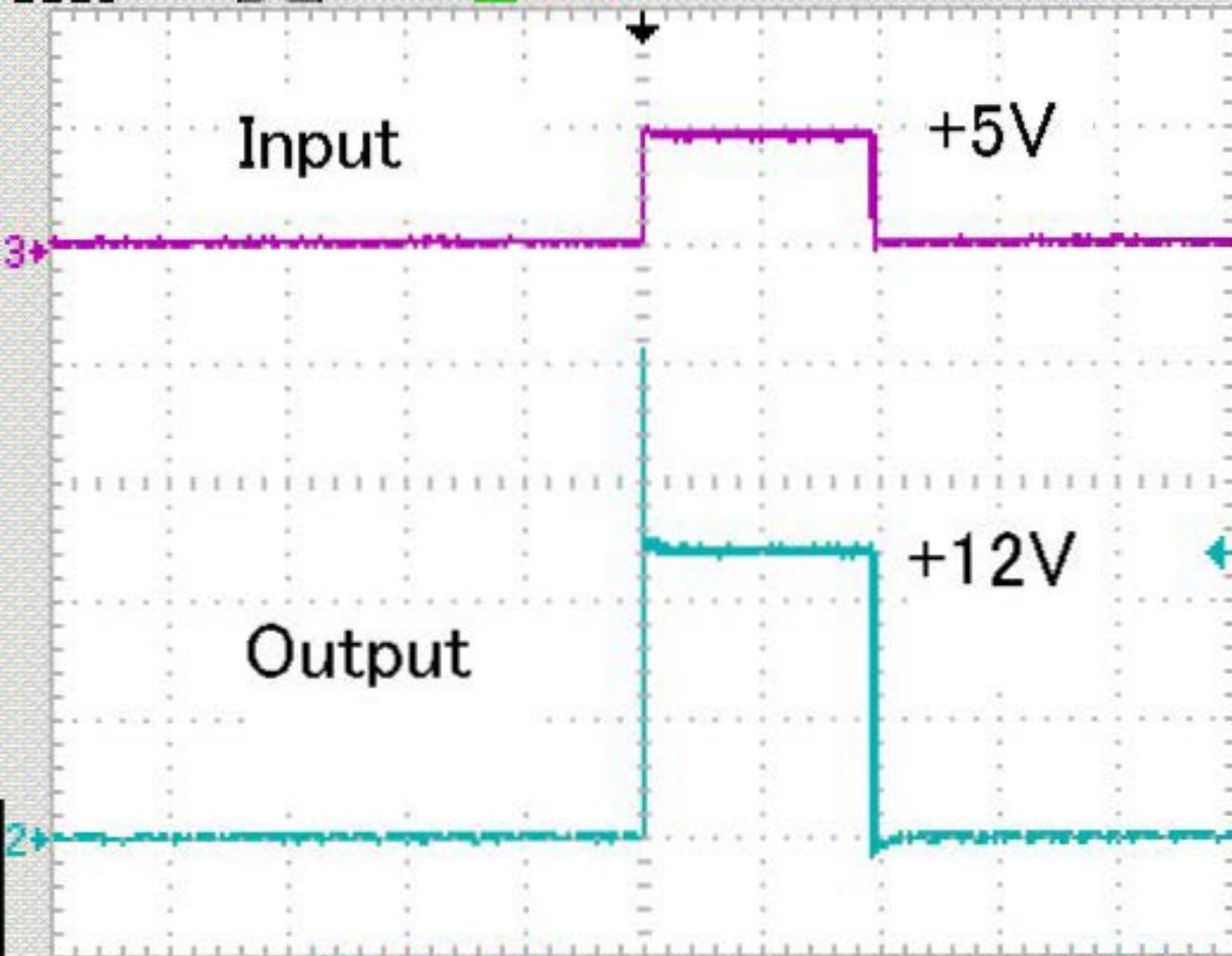

Coupling

DC

BW Limit

Off

100MHz

Volts/Div

Coarse

Probe

10X

Invert


Off

CH2 5.00VBW M 1.00ms

CH2 / 12.0V

CH3 vertical position 1.96 divs (9.80V)

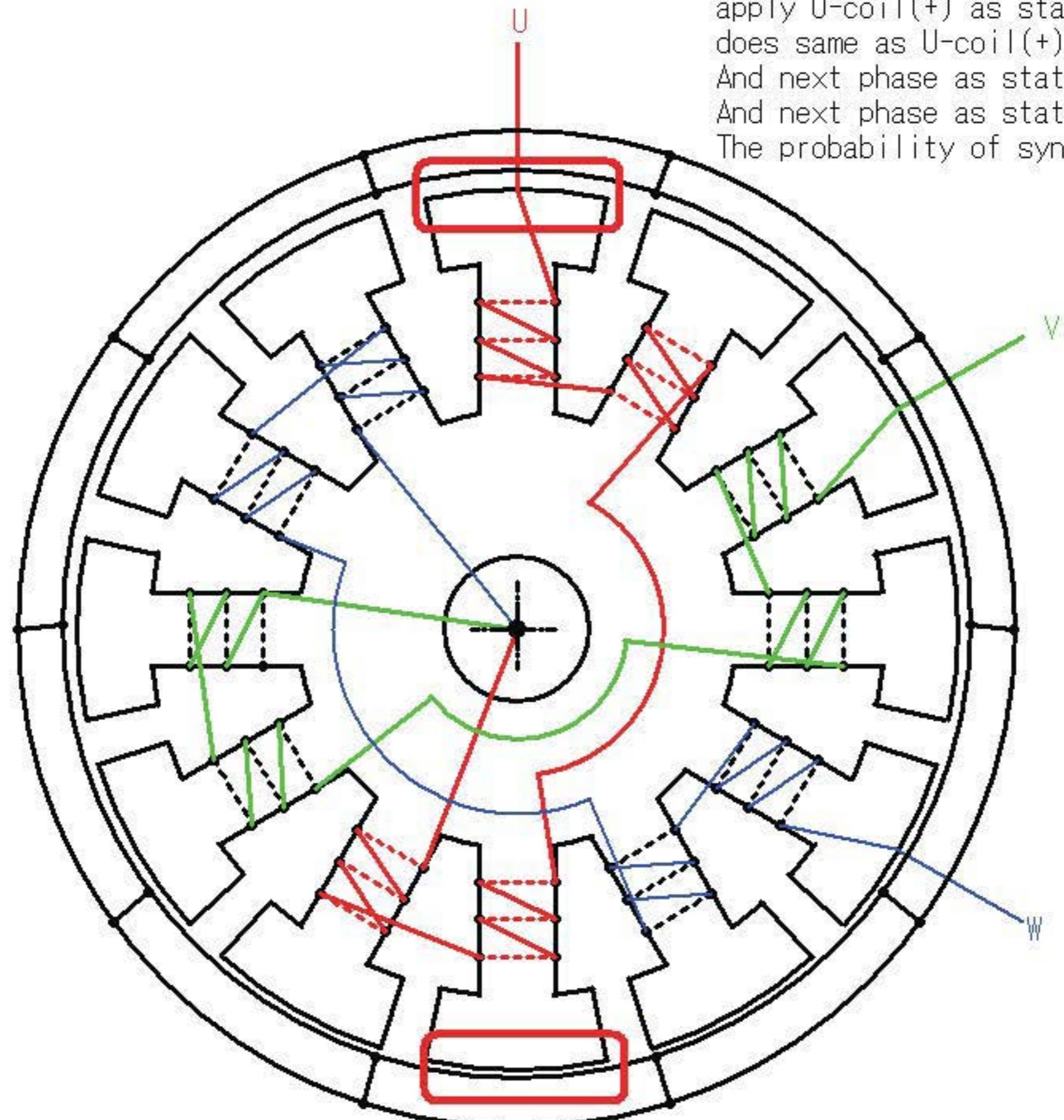To suck-in the red part of magnet, ex.
apply U-coil(+) as state1, and state2
does same as U-coil(+).
And next phase as state3,4 V-coil(+)
And next phase as state5,6 W-coil(+).
The probability of sync. is $\times 2$ better.



1

2

3

4


5

6


U

V

W

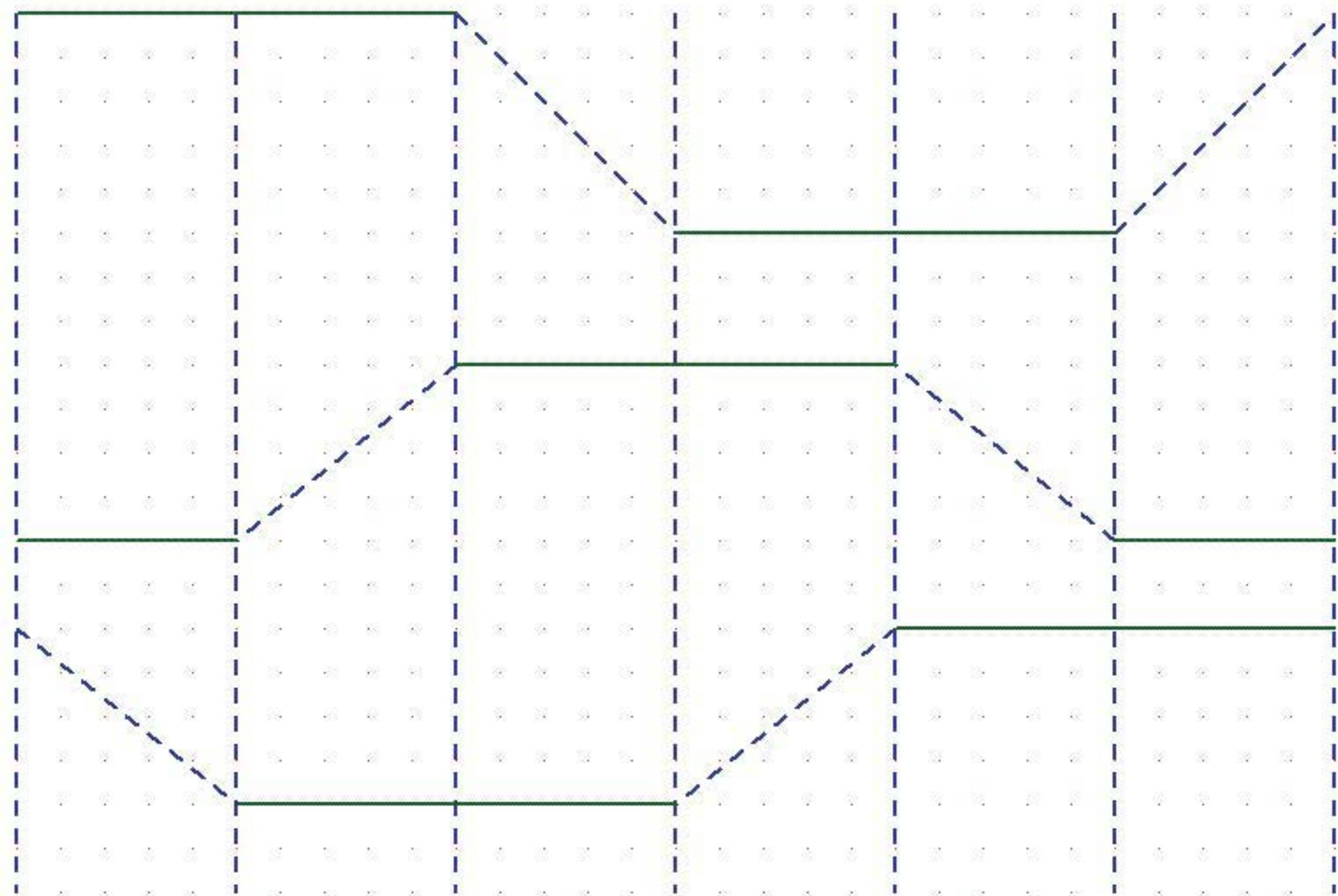

Stick Position

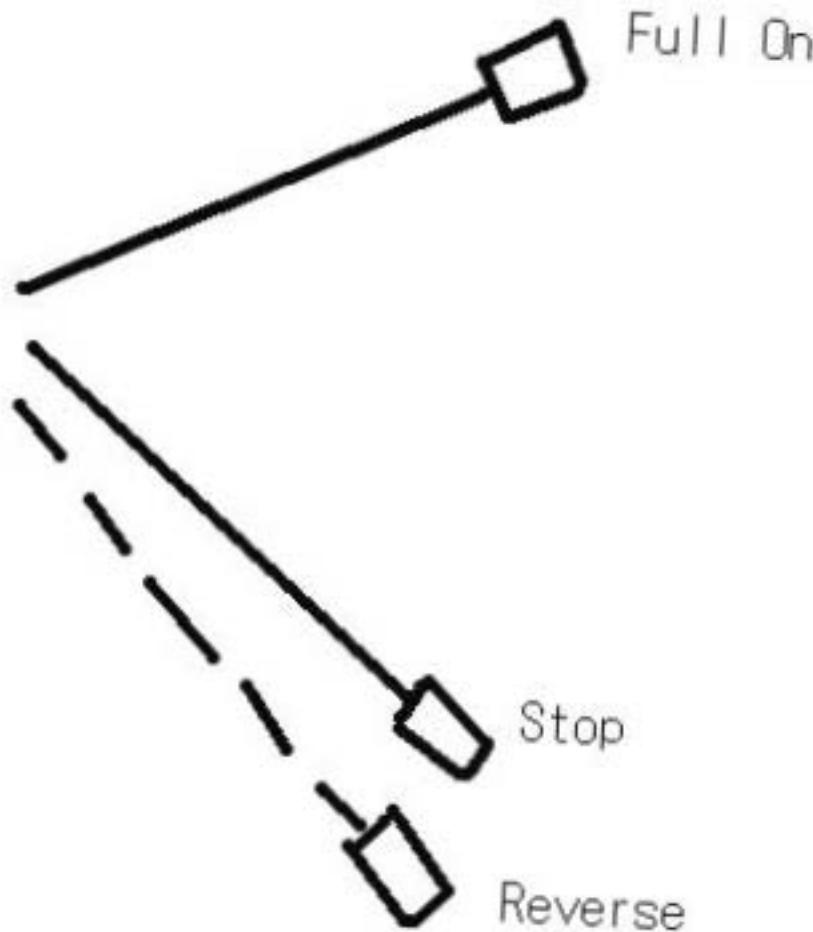

1 2 3 4 5 6

U


V


W




CCW

CW

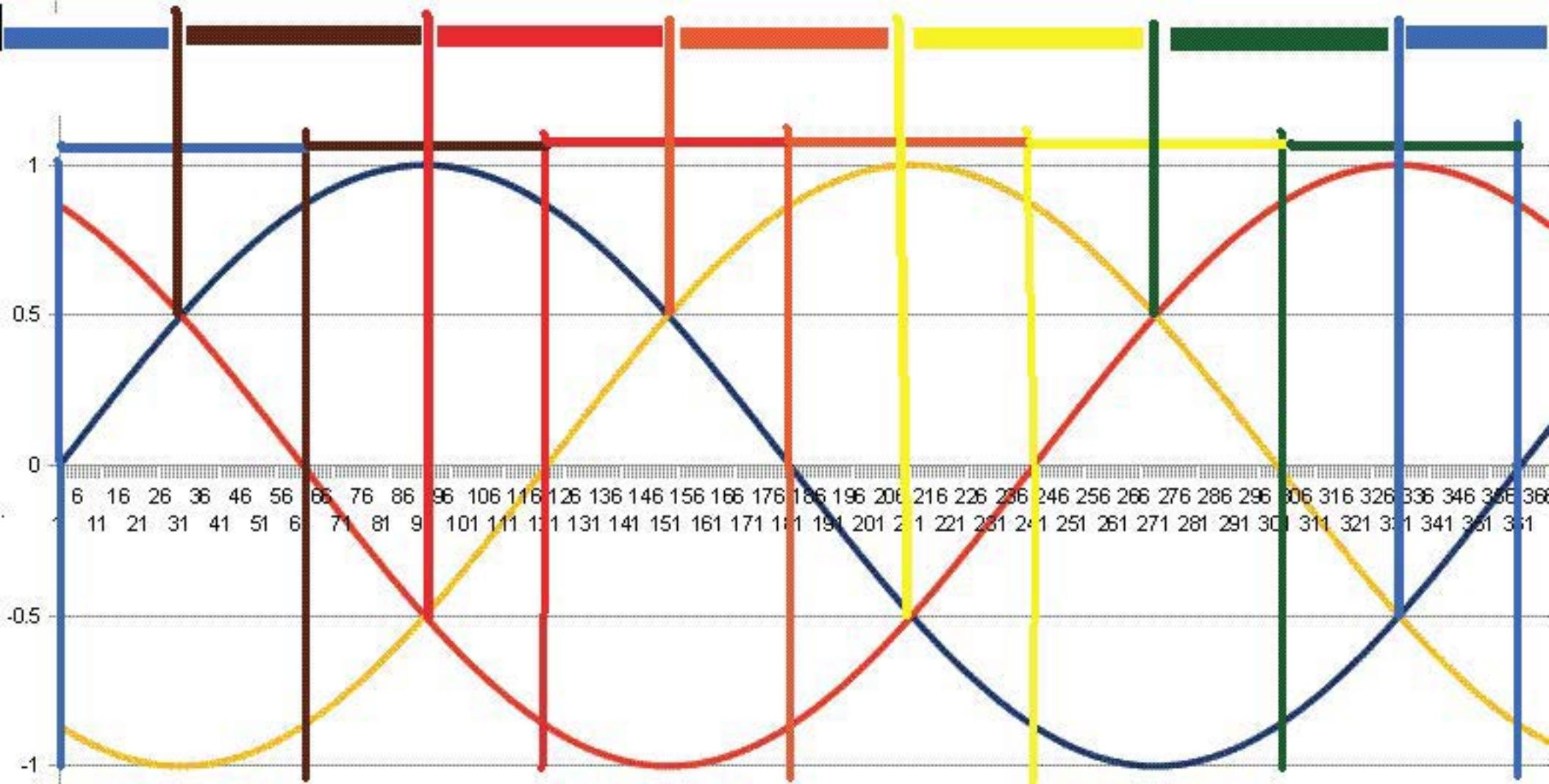

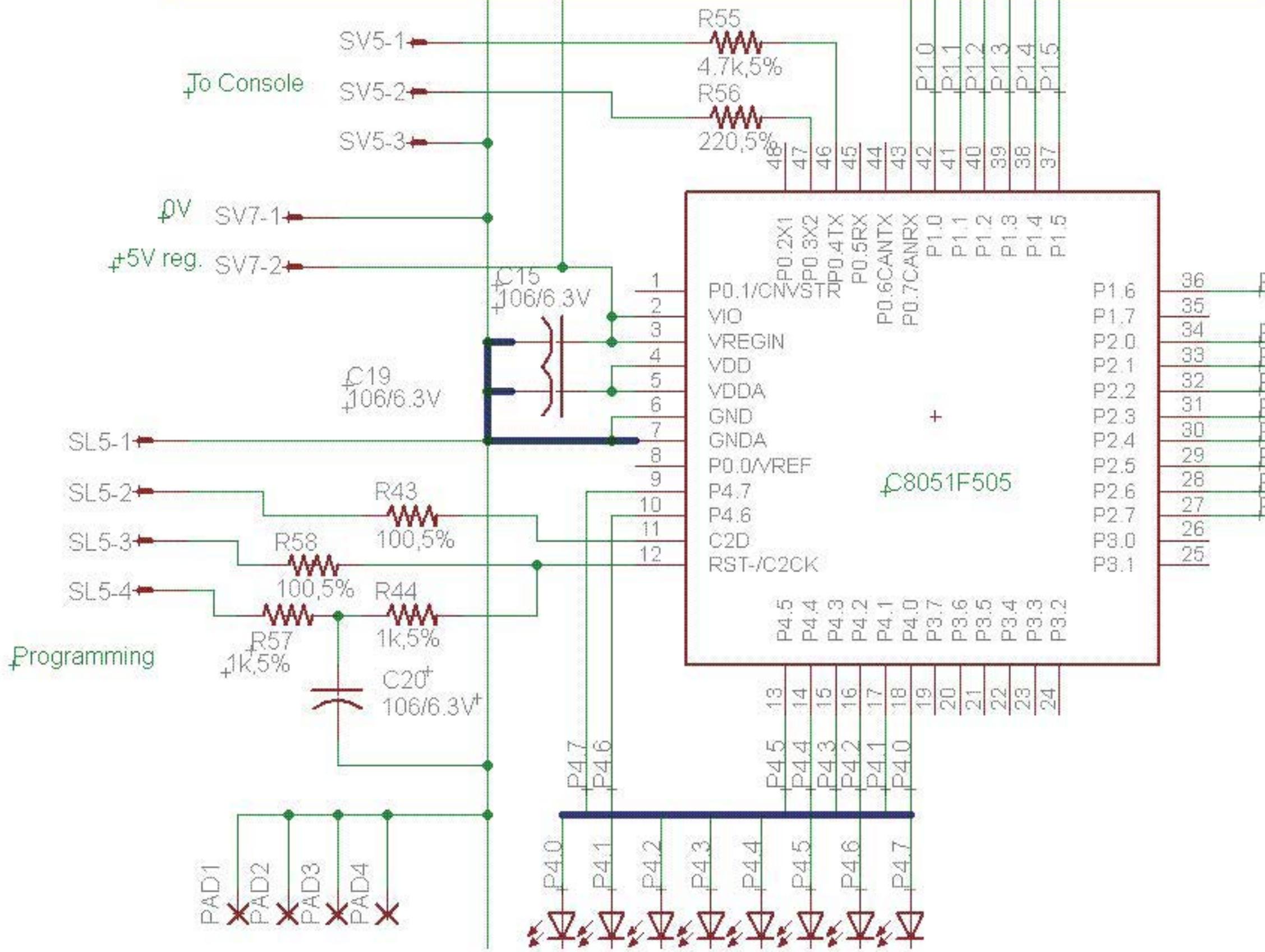

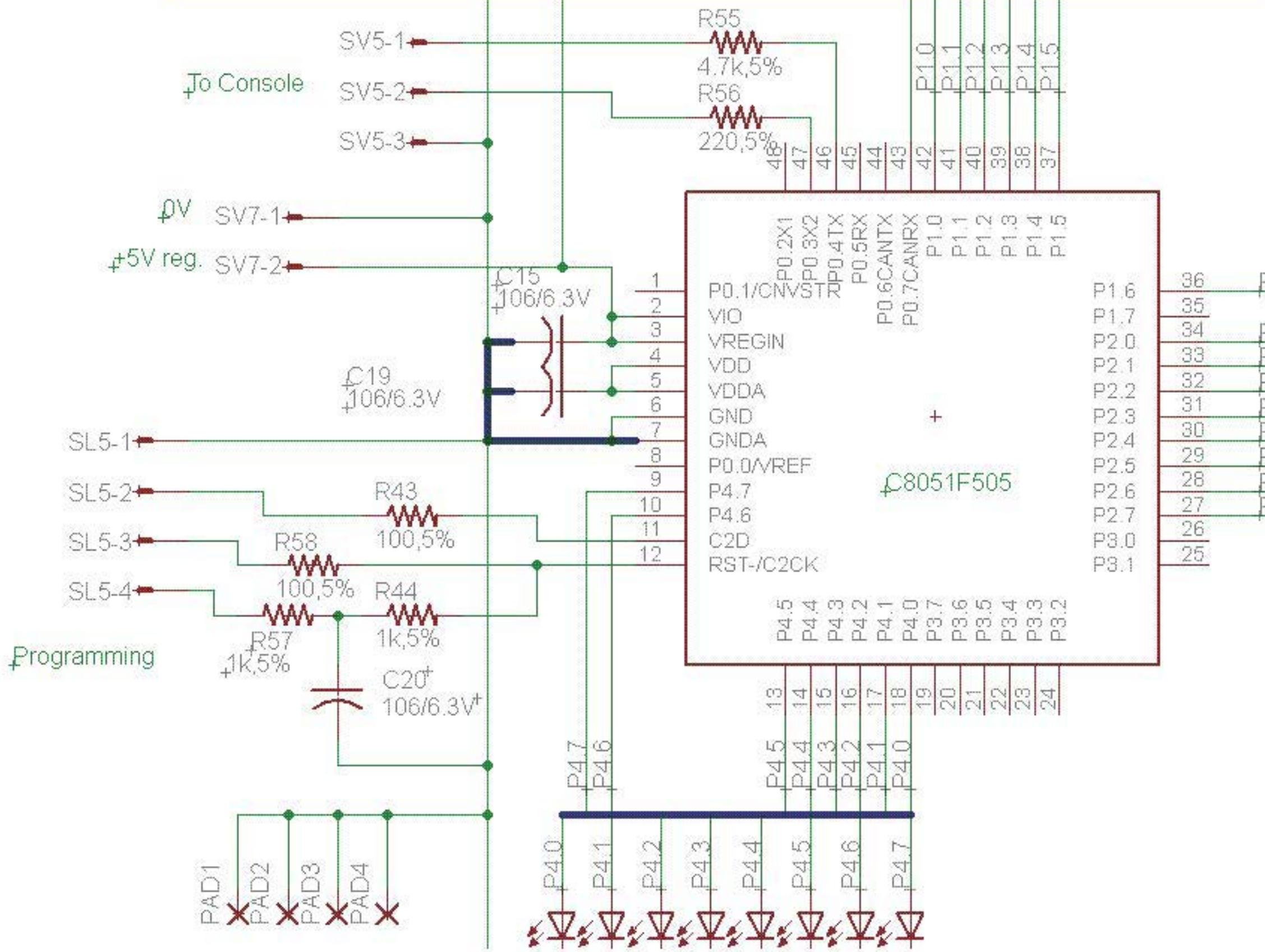

Tek

fl.

Stop

M Pos: 0.000s

TRIGGER

Type
Edge


Source
Ext

Slope
Rising

Mode
Normal

Coupling
DC

summing junction
level

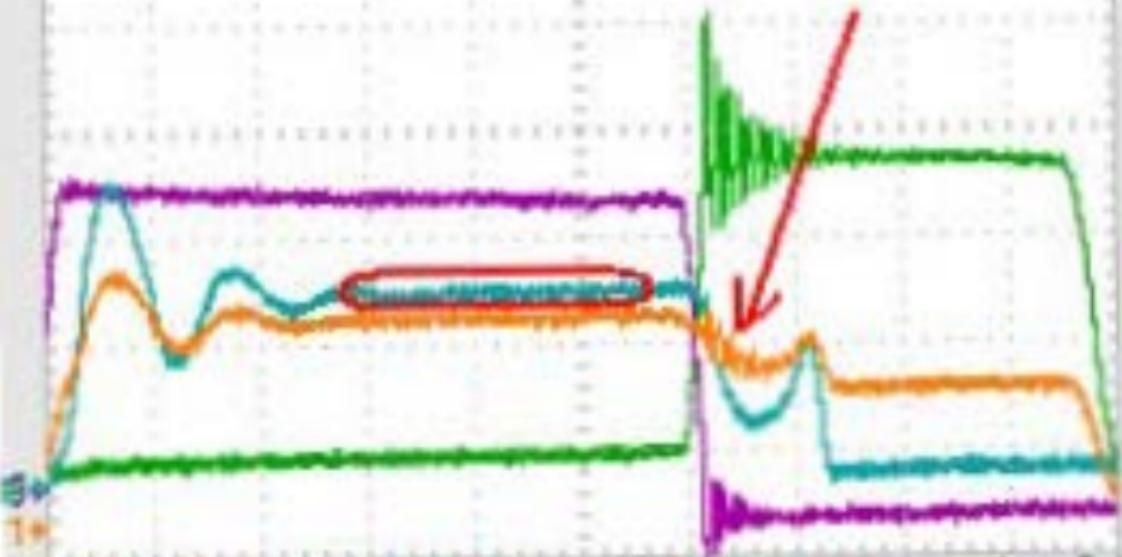

CH1 2.80V

CH2 5.00Vb/s

M 2.50 μ s

Ext / 1.60V

CH3 5.00V

CH4 50.0V

11-Mar-10 11:20

1.30460kHz

Tek

fls.

Stop

M Pos: 0.000s

THRU/H

Type
Edge


Source
Ext

Slope
Rising

Mode
Normal

Coupling
DC

summing junction
level

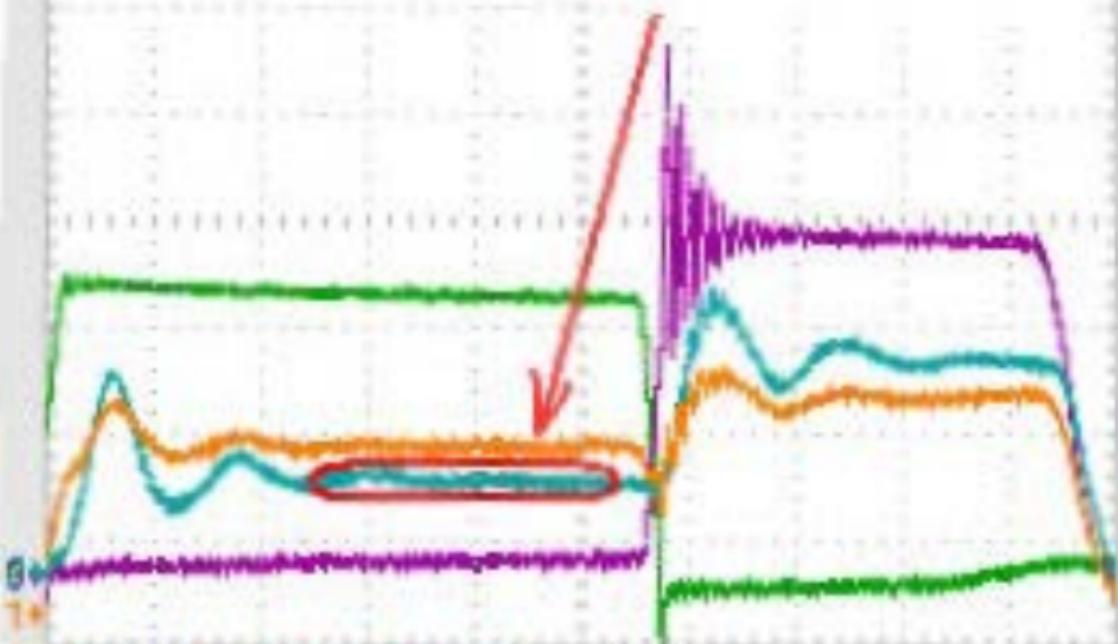

CH1 2.00V

CH3 5.00V

CH2 5.00V



CH4 50.0V

M 2.50 μ s

11-Mar-10 11:21

Ext / 1.60V

1.64022kHz

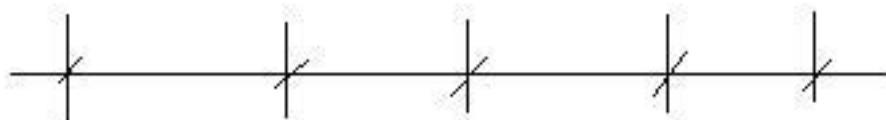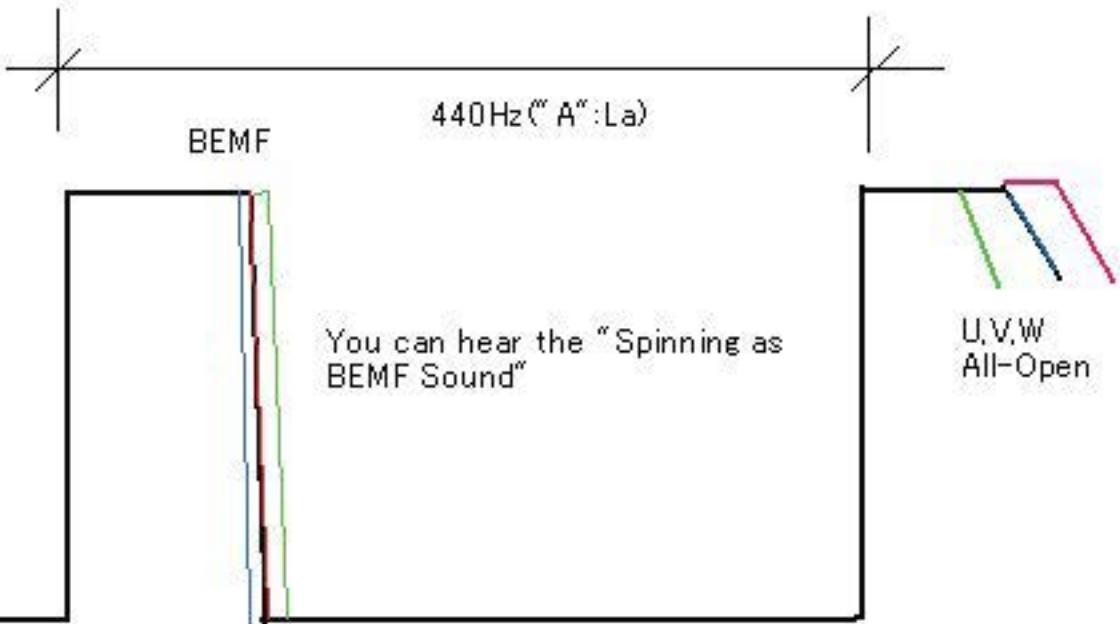

Charge-Up
High-Side
Driver Cap.
of U

Charge-Up
High-Side
Driver Cap.
of V

Charge-Up
High-Side
Driver Cap.
of W

U,V,W turn
On HIGH


Tek


M


Ready

M Pos: -6.600 μ s

CH3

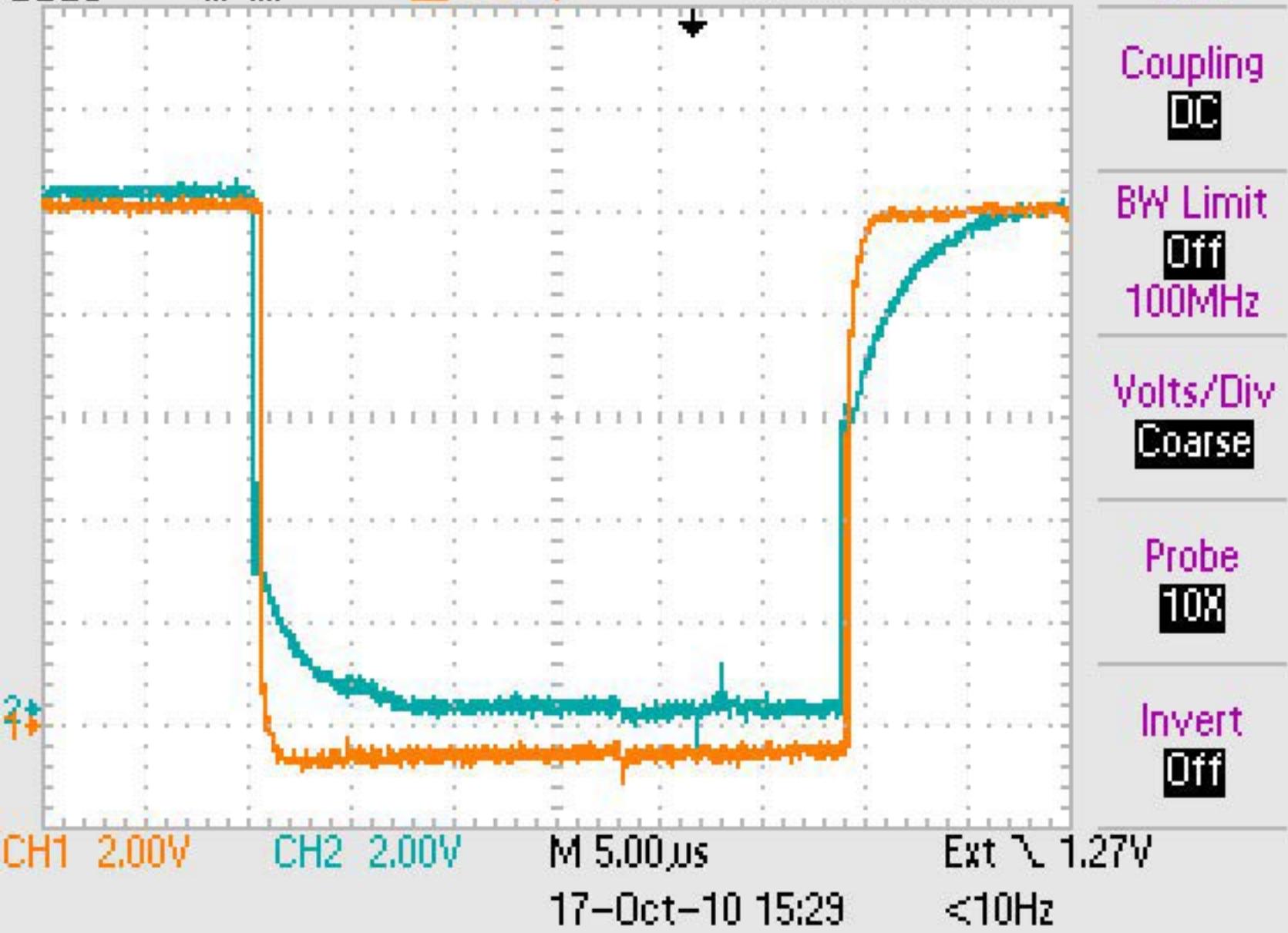

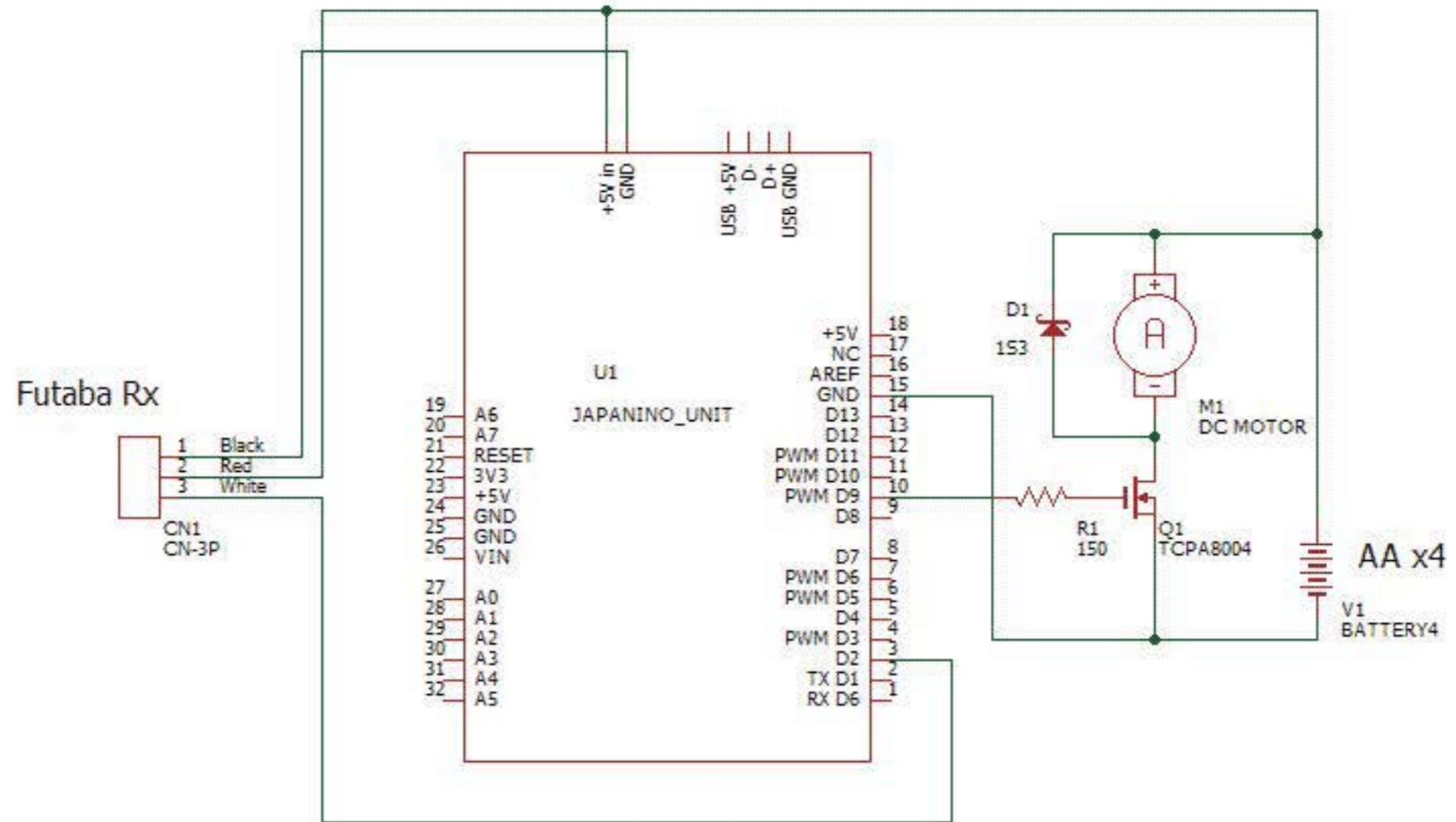

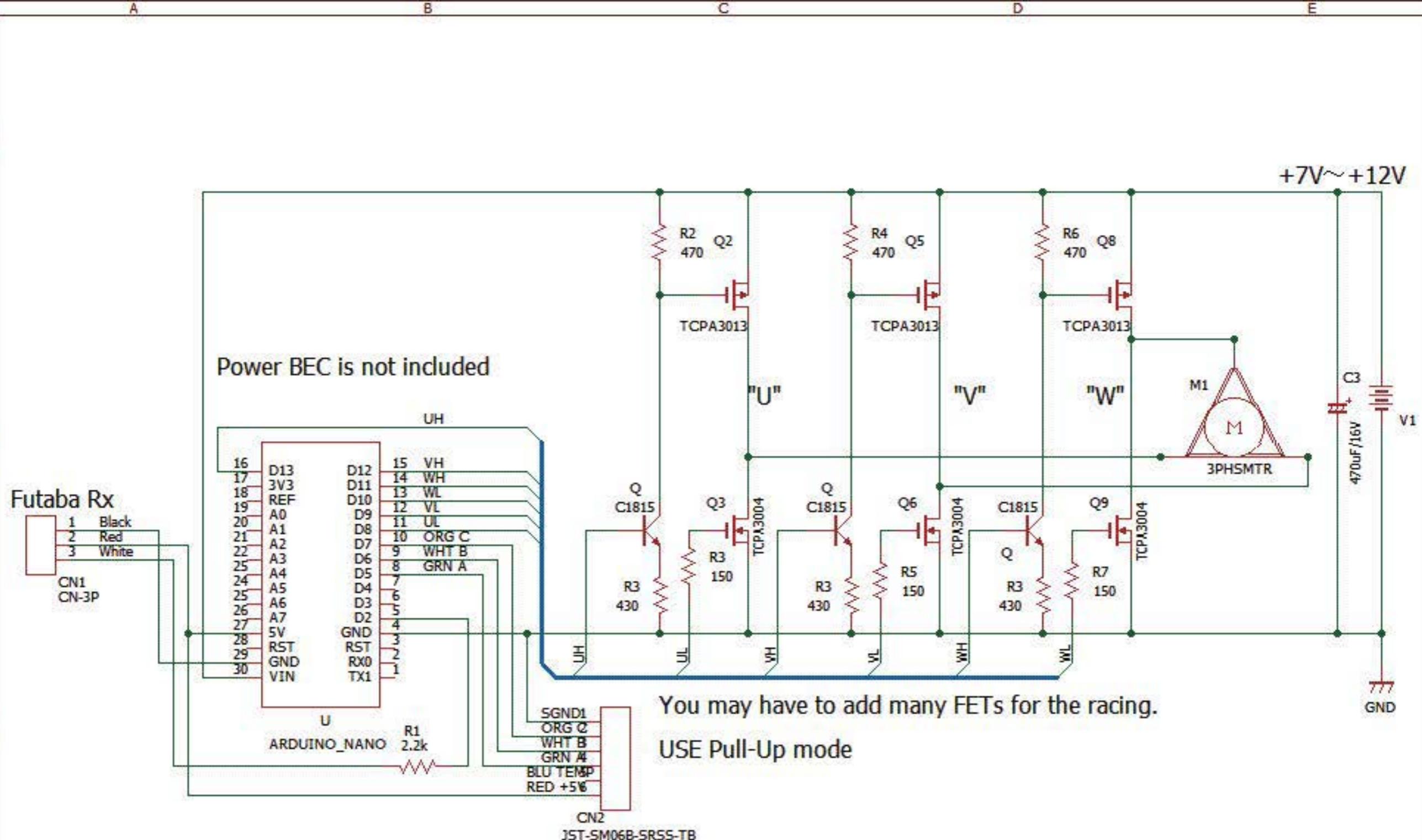

<http://www.rcgroups.com/forums/attachment.php?attachmentid=1244043>
But, the blue line is connected to +5V at Hobby king BL540ST.